


What is IC?

A device consisting of transistors to perform certain task

OpAmp Characteristics

17.01.19

Differential Amplifier

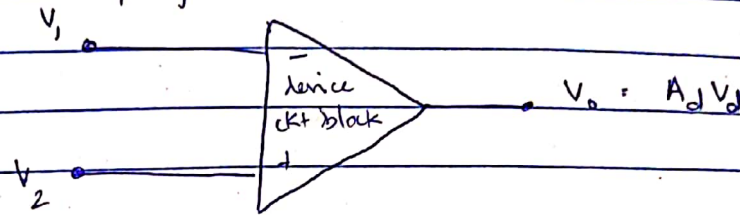


Amplifies the difference in signal.

$$V_d = V_1 - V_2$$

Using BJT and MOS we build a device
i.e. OpAmp

BJT & MOS are non-linear devices

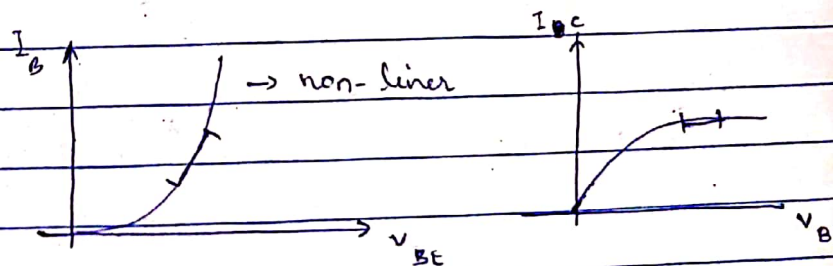

Taking the non-linear device we build OpAmp
& it is linear

As these non-linear device operate as linear
in certain area

The IC is not just amplifying the diff in signal but also the common voltage

$$V_c = \frac{V_1 + V_2}{2}$$

$$V_o = A_d V_d + A_c V_c$$

But we want to just amplify the diff only


$$\text{Common mode reduction ratio} = \frac{A_d}{A_c}$$

Here A_d must be large & $A_c \downarrow$


NOTE: The larger the CMRR, the better the OpAmp.

Terminal Characteristics of OpAmp

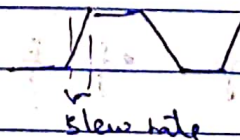- Gain A_d, A_c
- Input impedance $R_i \gg$
- Output impedance $R_o \approx 0$
- Bandwidth
- CMRR
- Slew Rate: The max permissible rate of signal




Amplifier model

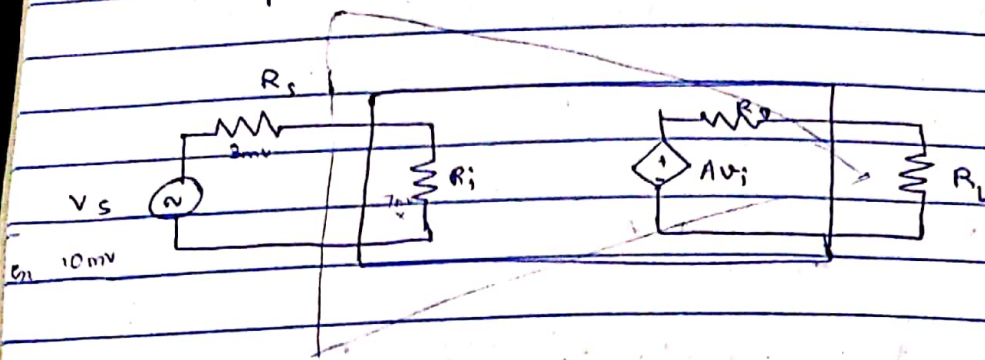


(1) R_i should be very large from R_s because we want the entire voltage to be across R_i

(2) R_o should be $\rightarrow 0$, as max current should come to R_L

(3) Bandwidth

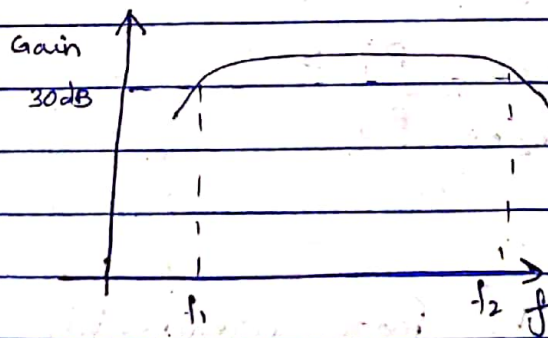

CE amp.

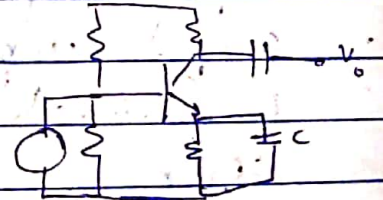

$$BW = f_2 - f_1$$


for what range of freq gain is const.

ideally BW should be very large (As it should amplify all freq)

(4) CMRR : ∞ ideal

practical values are the one built using BJT, MOS
i.e. 10^4 .

(5) Slew rate :

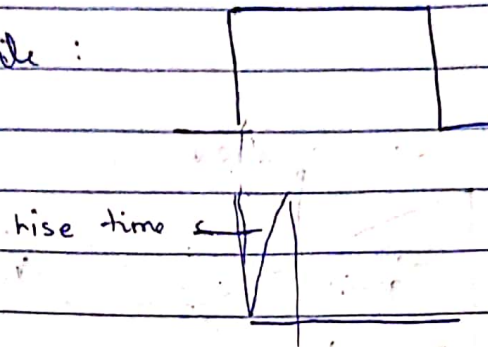


We expect the o/p to come immediately, the
rise time should be very less.

Ideally it should be ∞ , practical $0.5 \text{ V}/\mu\text{s}$

Device :


Linear IC

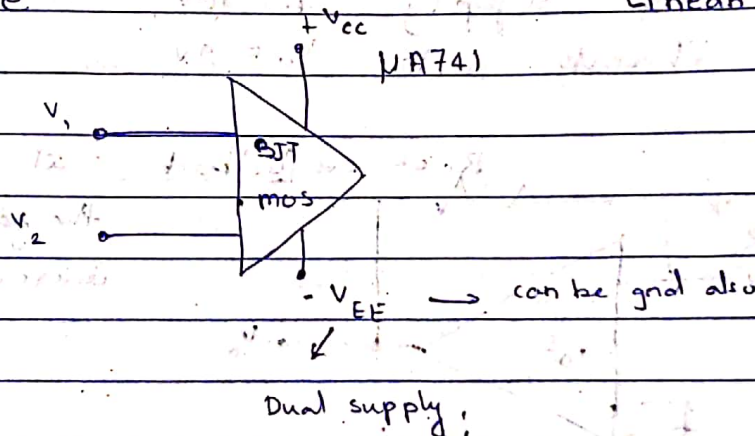


This IC can be used to build

- Inverting Amp
- Non-inverting
- Integrator
- Log
- Add
- Sub
- Differentiation
- Waveform generator
- Filter
- Comparator

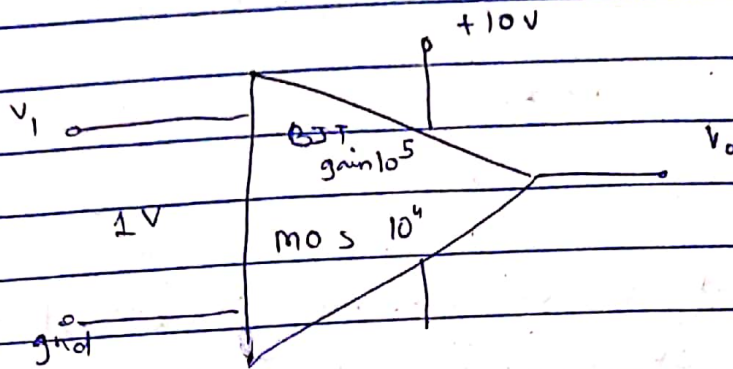linear applications
 ckt ———
 non-linear appli





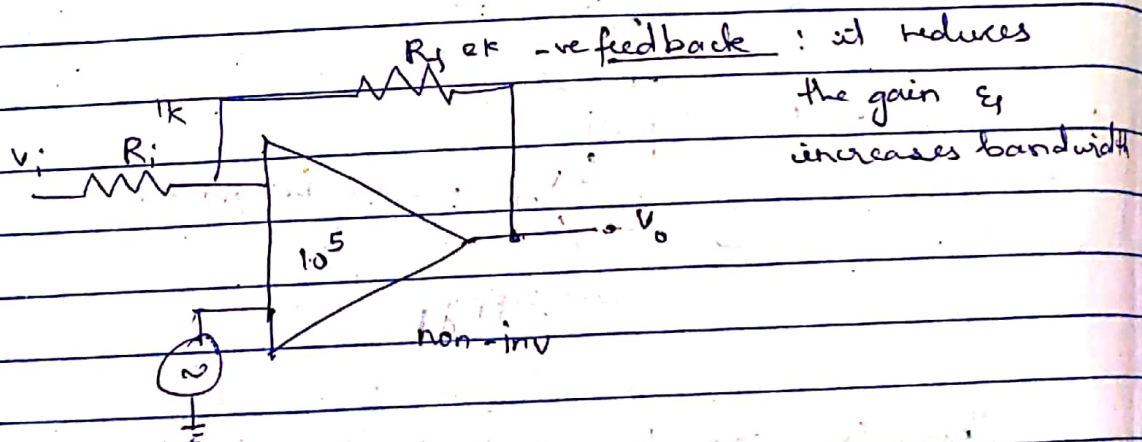
Gain 10^5 , but we can't expect V_o to be 10^4 not possible, as supply is 10V.
 So thumb rule: $V_o \approx 9V$.




$$\text{Gain} = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i} = 3$$

So here we are reducing the gain & $\uparrow$ BW

NOTE : OpAmp rejects ripples

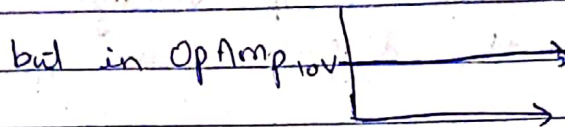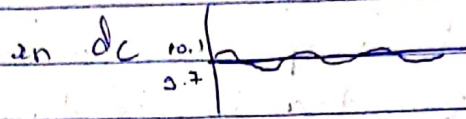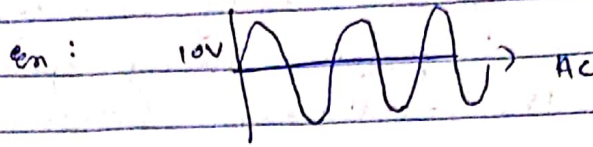

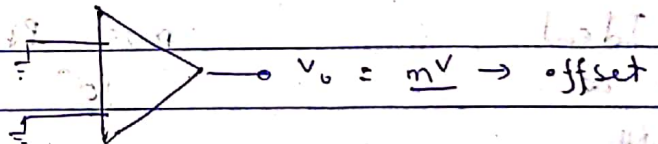NOTE : Offset error/voltage : If we find both V_1 & V_2 0, then V_o is expected to be 0, but practically it is not 0, but has some minute voltage.



Questions :

1. What is OpAmp?
 $\rightarrow$ It is a high gain, low bandwidth amplifier, which amplifies the difference in input voltages.

2. Why name OpAmp?

→ Because it operates only in certain range of frequencies & performs many operations

3. What is the difference between OpAmp and conventional amp?

→ A conventional amp has a single i/p & amplifies the i/p signal while a OpAmp has 2 i/p voltages & it amplifies the difference in i/p signals.

4. When does

a. Discuss the

(i) i/p offset voltage $V_{io} = V_{oo}/A_d$

(ii) $R_i = \infty$ ideally


(iii) CMRR = $\gg \infty$ ideally

(iv) $V_o = A_d V_d$

(v) slew rate : ∞ ideally

	Ideal	mos	Practical BJT
Gain	∞	10^4	10^5
Bandwidth			
R_i	∞		
R_o	0		

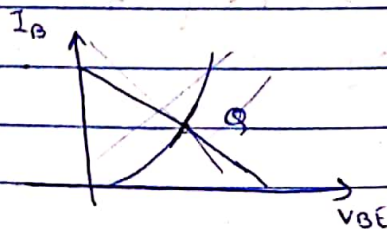4. The OpAmp operates in the linear region of the VI characteristics in cm config.



5. Ideal OpAmp must have.

Gain ∞

$R_i \infty$

$R_o = 0$


slownote 0

Bandwidth $\ll$

4. When two i/p signals are same, then its diff. $V_d = 0$, so it operates ($V_c = 2V$) in CM configuration.

8. In open loop gain OpAmp, the gain is very high (i.e. $10^5, 10^4$) which ideally is not possible to achieve, the OpAmp would reach saturation & V_o is not 10^5 .

Questions.

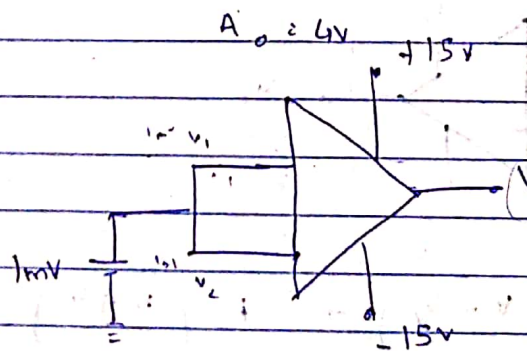

But here offset is there 0


$$V_o = A_d V_d + A_c V_c$$

$$V_o = 10 \times \left(\frac{1m + 1m}{2} \right) + 4$$

$$= 10 \times (1m) + 4$$

$$= 4.01 V //$$

$$A_c = 10$$

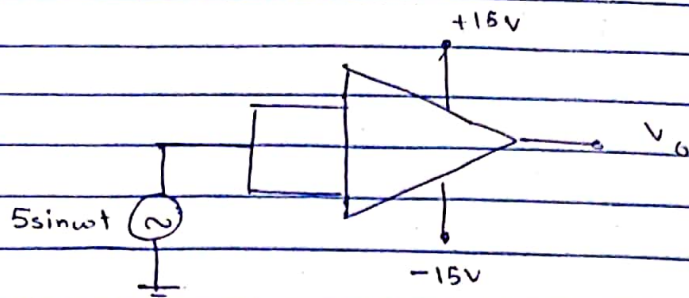

$$V_o = A_d V_d + A_c V_c$$


$$= 0 + 10 \times (5)$$

$= 50V \rightarrow$ not possible

So V_o will be $\approx \underline{15V}$

(a) $A_d = 10^5$
 $A_c = 10$
 $V_{oo} = 4V$

(i) $V_1 = -2m$ $V_2 = 3m$

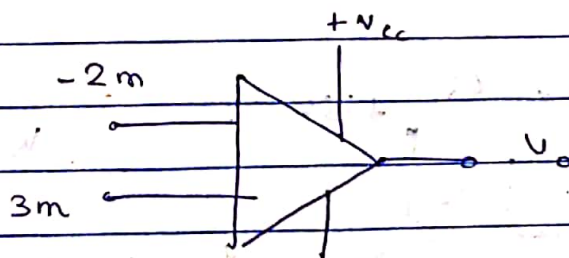

$$V_o = A_d (V_1 - V_2) + A_c \left(\frac{V_1 + V_2}{2} \right)$$

$$= 10^5 (-2 - 3)m + 10 \left(\frac{-2 + 3}{2} \right)m$$


$$= 10^2 (-5) + 10^2 \left(\frac{1}{2} \right)$$

$$= -499.995$$

input offset : the voltage given at i/p to make offset 0V.

② For transfer characteristics of diff amplifier

i) Identify diff regions of operations

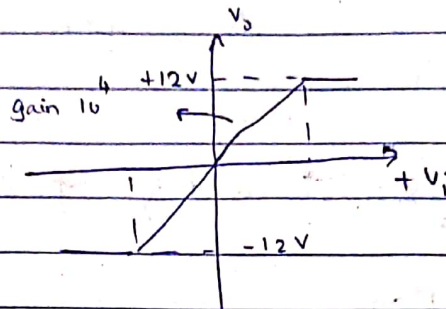


V_o will saturate after 12V.
It operates in linear mode at 12V to -12V.

$$V_o = 12$$

$$V_i$$

$$V_i = \frac{12}{10^4} = 1.2 \text{ mV} //$$

?

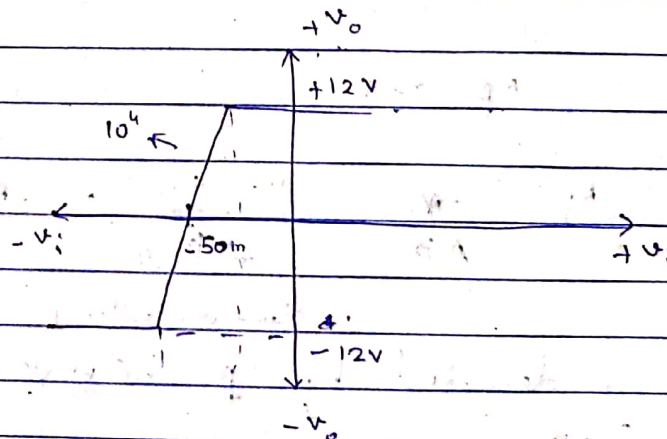

$$V_{io} = -50 \text{ mV}$$

$$V_o = A_d V_i$$

$$-50 \times 10^{-3} = 10^4 \times V_i$$

$$\frac{V_o}{V_i} = 10^4$$

$$V_i = 1.2 \text{ mV}$$

$$V_i = -5 \mu \text{V}$$

Opamp with negative feedback.

- Ideally, opamp has high gain & low bandwidth but due to negative feedback when connected as a circuit, gain decreases & bandwidth increases.
- Also improves the linearity of the system
- Reduces offset voltage
- The gain is reduced by a factor of $(1 + A\beta)$ which is called desensitization of the amp.
- By same factor Bandwidth, linear will ↑ & offset vol ↓

$$A_f = \frac{A}{1 + A\beta} \rightarrow \begin{matrix} \text{order of } 10^5 \\ \text{in } 0.25, 0.33 \end{matrix}$$

$$A\beta \gg 1$$


$$A_f = \frac{A}{A\beta} = \frac{1}{\beta} = \frac{R_1 + R_2}{R_1}$$

(inverse ratio)

Gain is decided by ' β ' network & not by OpAmp

This means gain of opamp can fluctuate
This is called desensitization.

β - network

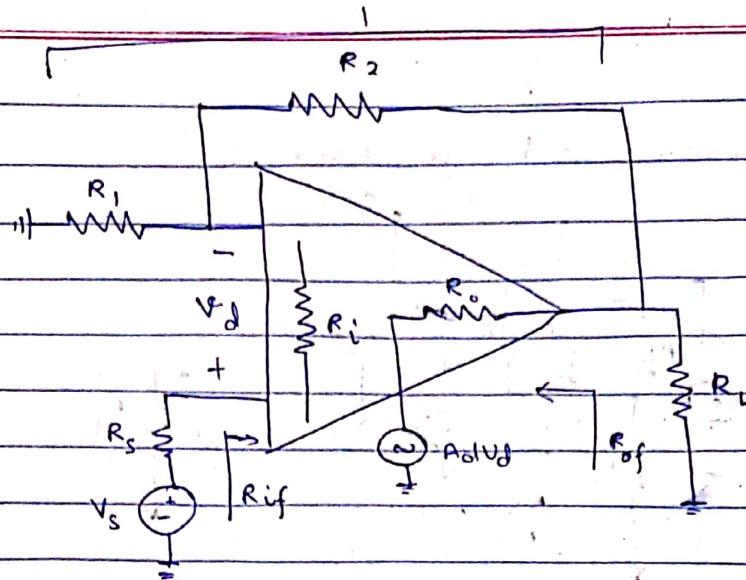

- R_{if} is input impedance of amp as seen by signal source
 R_{if} not same as R_i

$$R_{if} = R_i(1 + A\beta) \rightarrow \text{very large}$$

$\therefore R_{if}$ very large

By virtue of feedback we have achieved input impedance virtually ∞


11th for o/p resistance i.e. R_o is of finite value.

R_{of} is o/p resistance as seen by load resistance R_L .

$$R_{of} = \frac{R_o}{1 + A\beta} \quad R_{of} = \text{very small}$$

The effective value of R_{of} gets reduced

Input resistance with feedback

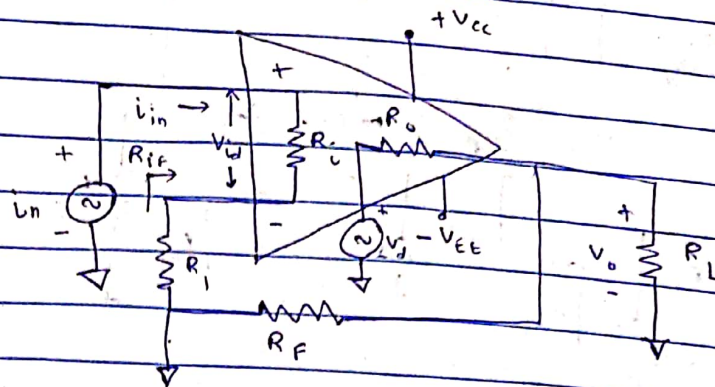

$$R_{if} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{V_d / R_i}$$

$$V_d = \frac{V_o}{A} \quad \text{and} \quad V_o = \frac{A}{1 + A\beta} V_{in}$$


$$R_{if} = \frac{R_i V_{in}}{V_o / A}$$

$$R_{if} = \frac{A R_i V_{in}}{A V_{in} / (1 + A\beta)}$$

$$\boxed{R_{if} = R_i (1 + A\beta)}$$

Output resistance with feedback

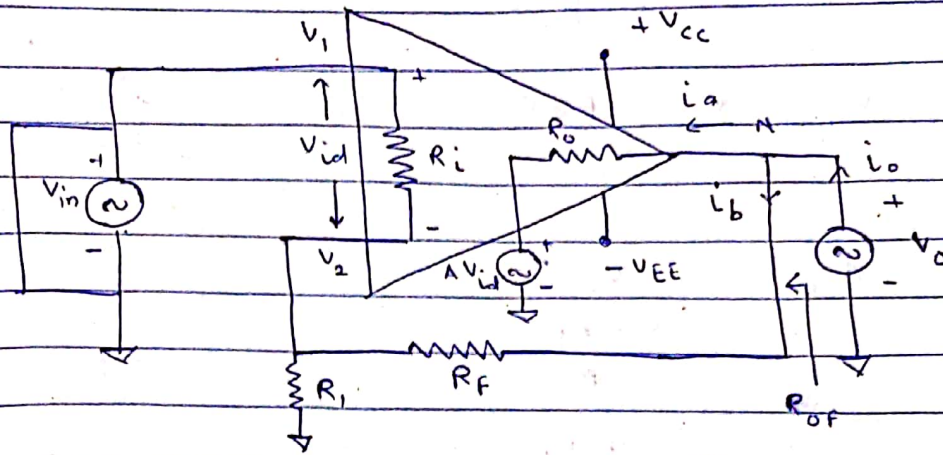Output resistance is the resistance determined looking back into feedback amplifier from output terminal.



It is obtained by using Thevenin's theorem for dependent sources

$$R_{of} = \frac{V_o}{i_o}$$

Writing KVL at output node N

$$i_o = i_a + i_b$$

since $[(R_f + R_i) \parallel R_i] \gg R_o$ & $i_a \gg i_b$

$$i_o \approx i_a$$

Writing KVL for o/p loop,

$$V_o - R_o i_o - A V_{id} = 0$$

$$i_o = \frac{V_o - A V_{id}}{R_o}$$

$$V_{id} = V_1 - V_2$$

$$= 0 - V_f$$

$$V_{id} = -\frac{R_o V_o}{R_i + R_f}$$

$$V_{id} = -\beta V_o$$

$$i_o = \frac{V_o + A\beta V_o}{R_o}$$

$$R_{of} = \frac{V_o}{\frac{V_o + A\beta V_o}{R_o}}$$


$$= \frac{V_o R_o}{V_o (1 + A\beta)}$$

$$R_{of} = \frac{R_o}{1 + A\beta}$$

~~Band~~

24.01.19

Unity gain

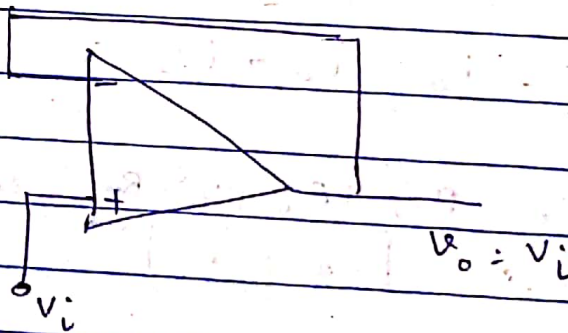


Buffer

$$A = 1 + \frac{R_2}{R_1}$$

$$A = 1$$

$$\frac{V_o}{V_i} = 1$$

Consider

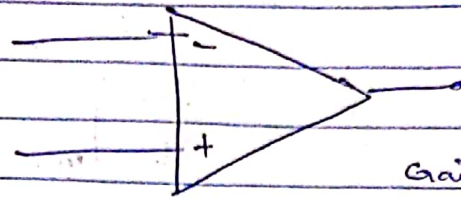


Gain 10^5

$$\omega_1 < \text{UGB}$$

$$\text{BW} = \omega_1$$

(1) opAmp

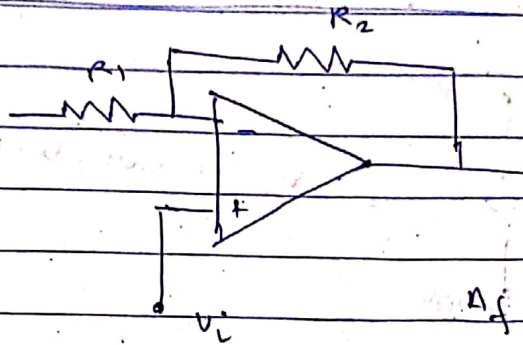

$$A_f = 1 + \frac{R_2}{R_1}$$

(2) Non-inverting amp $\rightarrow$ An amplification built using opAmp

$$\text{BW} = \omega_f$$

$$\omega_{if} > \omega_1$$


$$A_f \ll A$$

$$\text{Here } \text{UGB} \gg \omega_{if}$$

UGB (Unity gain bandwidth) =

$$\text{UG} \times \text{BW}$$

(3) Voltage Follower

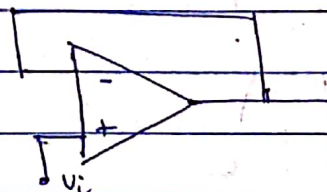

$$v_o = v_i$$

$$A_f = 1 ; \omega_{if} = \text{BW}$$


$$\text{UGB} = \text{UG} \times \text{BW} = \omega_{if}$$

Gain cannot go < 1 , min is 1.

Slew Rate :

By defn. $SR = \left. \frac{dV_o}{dt} \right|_{\min}$

consider an open loop OpAmp

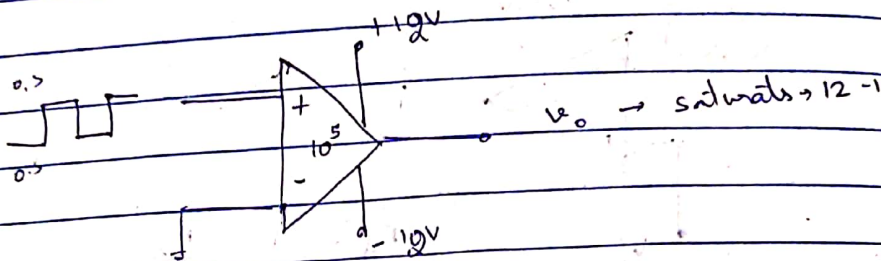

Gain is 10^5 , V_{CC} , V_{EE} is 12V

$$V_d = 1 - 0 = 1$$


$$V_o = A_d V_d$$

$$= 10^5 \times 1$$

$$= 10^5 \text{ V} \rightarrow \text{unexpected}$$

not possible

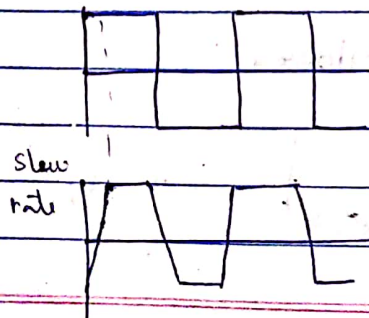KVL says in a loop all volts sum to 0
So it doesn't justify KVL




Slew rate is the max rate of change of the output terminal voltage.

In Case of amplifier,

consider


i/p	o/p
sine wave	sine
1V	2V
1.5V	3V

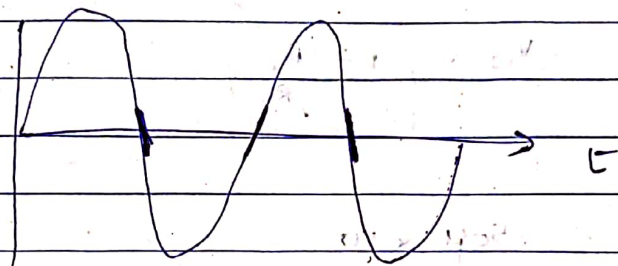

max rate of change occurs at zero crossing

slew rate will put a constraint on bandwidth.

Feedback Affects offset error

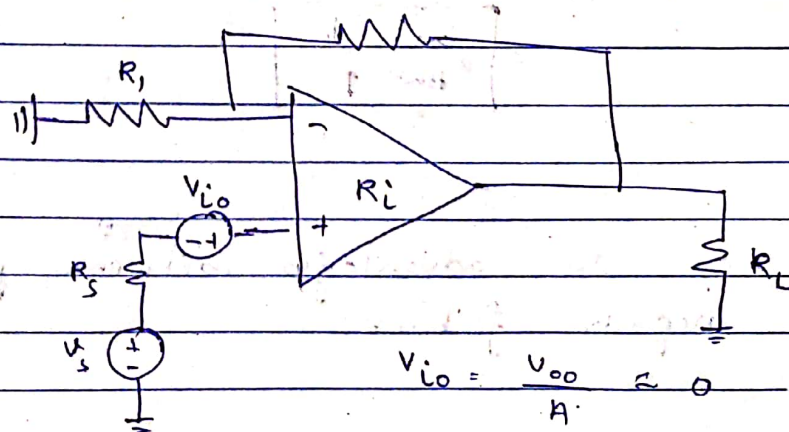

input referred offset voltage

Using Superposition

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_c + \left(1 + \frac{R_2}{R_1}\right) V_{io}$$

Ex: OpAMP

$V_{oo} = 5V$ then $V_{io} = \frac{V_{oo}}{A} = \frac{5}{10^5} = 50 \mu V$

Amplifier effect of V_{io} on the o/p

$$= V_{io} \times \left(1 + \frac{R_2}{R_1}\right)$$

$$= 50 \mu \times 10$$

$$= 0.5 mV \rightarrow \text{still not zero, (DC pedestal)}$$

Conclusion

OpAmp - chcn - not ideal

use feedback

Gain ↓

BW ↑

Applications
of
OpAmp

? What are the advantages between positive and negative feedback?


→ Negative feedback of the amplifier reduces the gain & increases the bandwidth of the OpAmp, it brings the ideal characteristics of the opAmp. In case of +ve feedback gain ↑.

2. How does negative feedback affect on gain, input impedance, output impedance and bandwidth

→ Gain decreases ↓
 input impedance increases ↑
 output impedance decreases ↓
 bandwidth increases ↑

loop gain → desensitivity.

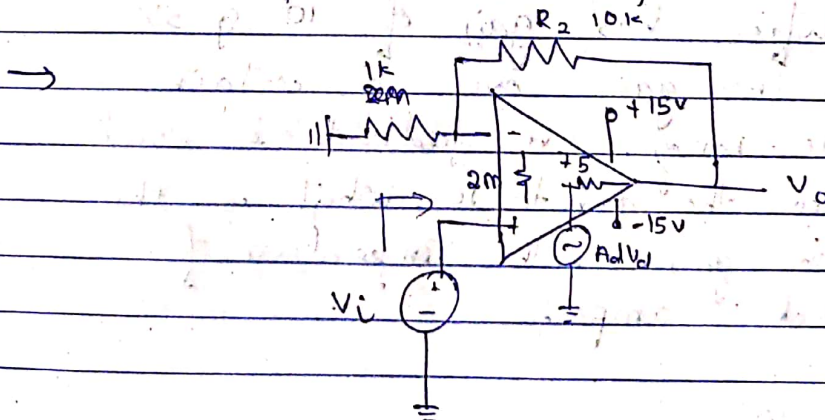1. An Opamp (741C) having parameters
 $A = 2 \times 10^5$, $R_1 = 2 \text{ M}\Omega$, $R_o = 75 \Omega$, $f_o = 5 \text{ Hz}$
 supply voltage = $\pm 15 \text{ V}$, output voltage swing = $\pm 13 \text{ V}$ is connected as a non-inverting amplifier with $R_1 = 1 \text{ k}\Omega$, $R_f = 10 \text{ k}\Omega$ compute A_f , R_{if} , R_{of} , F_f & V_o



$R_{if} =$

$$A_f = 1 + \frac{R_2}{R_1} = 1 + \frac{10\text{k}}{1\text{k}} = 11$$

$$A_f = \frac{A}{1 + A\beta} = \frac{1}{\beta}$$

$$\beta = \frac{R_1}{R_1 + R_2} = \frac{1k}{111k} = \frac{1}{11}$$

$$R_{if} = R_i (1 + A\beta)$$

$$R_{if} = 2M (1 + 2 \times 10^5 \times \frac{1}{11})$$

$$R_{if} = 3.6 \times 10^{10} \Omega$$

$$R_{of} = \frac{R_o}{1 + A\beta} = \frac{75}{1 + (2 \times 10^5)}$$

$$= 4.12 m\Omega$$

$$f_f = f_o (1 + A\beta)$$

$$= 5 (1 + 2 \times 10^5)$$

$$= 90.9 KHz$$

$$V_o = 11 \times V_i$$

? An amplifier has gain of 10^5 & 5% variation in gain over a certain temperature range. -ve feedback is used to reduce the gain to 10. What is the variation in gain with temperature of the feedback amplifier

→

$$A_f = 10$$

$$A = 10^5$$

... $\uparrow$ $1 + a_m \beta$) - (1)

5% variation : $10^5 + \frac{5 \times 10^5}{100}$

$$A_f = 10.5 \times 10^4$$

$$A_f = \frac{A}{1 + A\beta} = \frac{10.5 \times 10^4}{1 + (10.5 \times 10^4) \left(\frac{1}{11} \right)}$$

Given $A_f = 10$,

$$A_f = \frac{A}{1 + A\beta}$$

$$10 = \frac{10^5}{1 + 10^5 \beta}$$

$$10 + 10^6 \beta = 10^5$$

$$\boxed{\beta = \frac{1}{10}}$$

It will not vary.

HW An amplifier has gain of 800. After adding negative feedback the gain is measured as 25. Find feedback factor.

$$\rightarrow A_f = \frac{A_{OL}}{1 + \beta A} \quad 25 = \frac{800}{1 + 800 \beta}$$


wherever there is 0 cross the rate of change of V_o is max.

$$\beta = 0.0388$$

$$\begin{aligned}\text{loop gain} &= 800\beta \\ &= 800 \times 0.0388 \\ &= 31.04\end{aligned}$$


Slew Rate

29.1.19

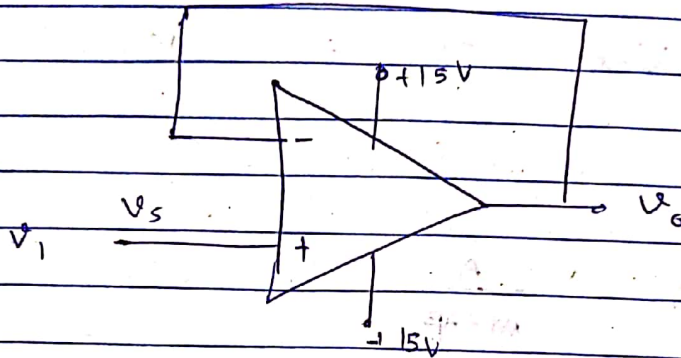

$$\begin{aligned}\text{Slew rate} &= 0.5 \text{ V}/\mu\text{s} \\ \text{Gain} &= 1\end{aligned}$$

$V_o = ?$ at what time

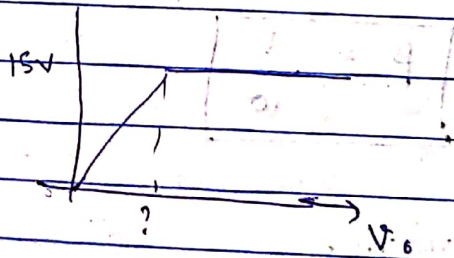

$$\frac{15}{0.5} = \underline{\underline{30 \mu\text{s}}}$$

(ii) input is $V_s = V_m \sin \omega t$

$$V_o = V_m \sin \omega t = V_s$$

what is maximum freq of i/p signal that this amp can handle without distortion

$$SR = \left. \frac{dV_o}{dt} \right|_{\max}$$

$$V_o = V_m \sin \omega t$$

$$\frac{dV_o}{dt} = \omega V_m \cos \omega t$$

It is max when $\cos \omega t = 1$

$$\omega t = 0$$

$$\left. \frac{dV_o}{dt} \right|_{\max} = \omega V_m$$

$$0.5 \text{ V} / \mu\text{s} = 2\pi f V_m$$

$$f = \frac{0.5 \times 10^6}{2\pi V_m}$$

NOTE: If $V_m = 1 \text{ V}$

$$f = 79.5 \text{ kHz} //$$


$$V_m = 15 \text{ V}$$

$$f = 5.3 \text{ kHz} //$$

Non-linear (harmonic) distortions :-


OpAmp is a linear IC built using non-linear (MOS, BJT).

Characteristic of MOS

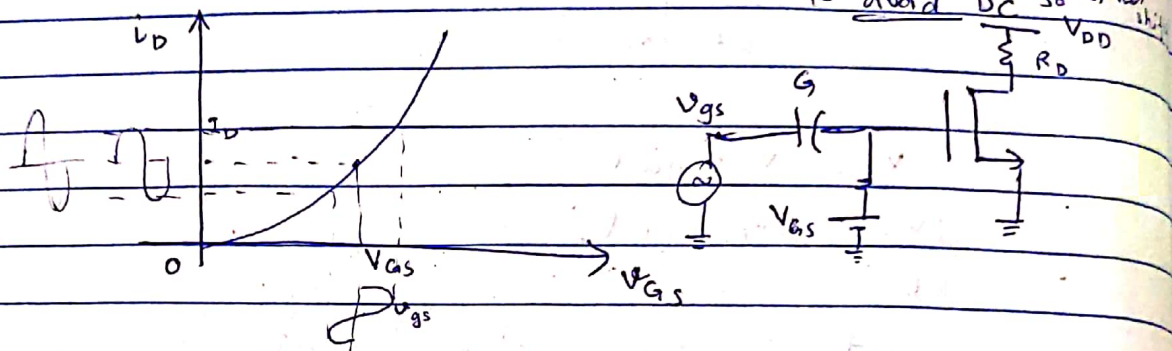

NOTE:


v_{gs}	- small signal
V_{GS}	- DC
V_{GS}	- Total instantaneous
V_{gs}	- RMS

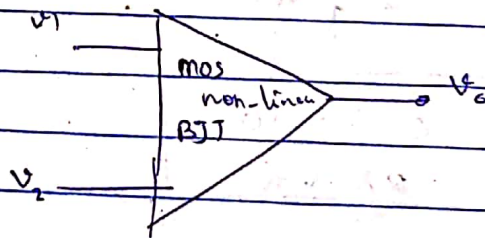

So opAmp also non-linear working in linear mode only in certain region. Along with dominant -ve feedback.

$$V_a / (1 + g_m r_{ds})$$

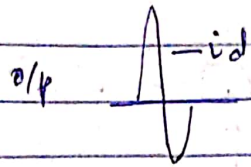Mathematically, Fourier analysis says that all the non-linear distortions are getting added to o/p



fundamental (i/p)

$$i_d = i_{1m} \sin \omega t + i_{2m} \sin 2\omega t + i_{3m} \sin 3\omega t + \dots$$


non-linear

harmonics

The distortion due to the non-linearity of device.

OpAmp model -

cannot ignore

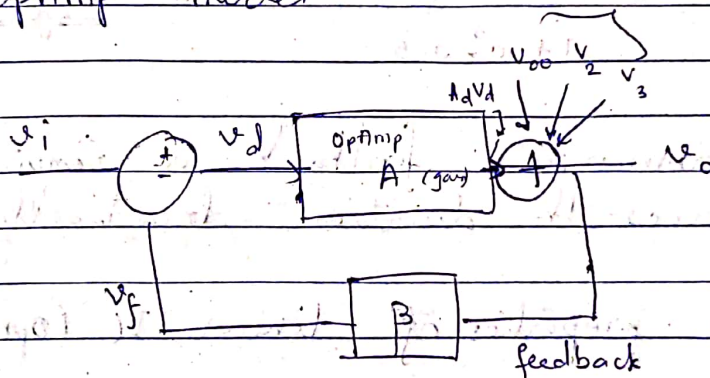


This is not a SISO (due to V_{00}, V_2, V_3) it is MISO.

Now finding V_o , we use superposition

(i) consider V_i & nullify V_{00}, V_2, V_3

$$V_o = \frac{A}{1 + A\beta} V_i +$$

(ii) consider V_{00}

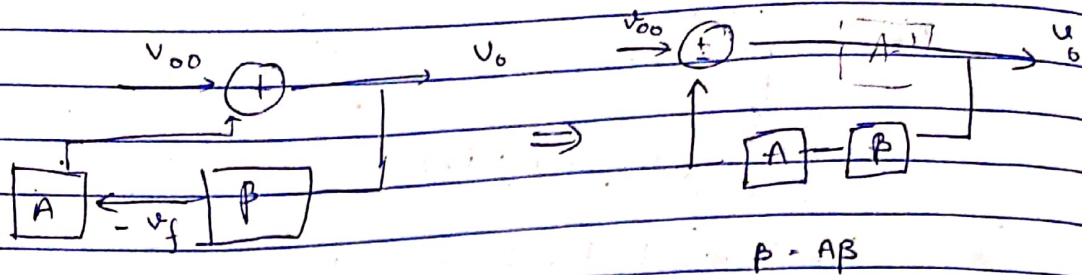

$$\frac{V_o}{V_{oo}} = \frac{1}{1 + 1 \times AB} = \frac{1}{1 + AB}$$


Ex take $V_{oo} = 2V$
 $A = 10^5$

$$V_o = \frac{2}{1 + 10^5 \times 0.5} = 4 \times 10^{-4} \text{ very small}$$

So a dominant feedback is required
 so reduces the distortion drastically.

Two imp properties of linear IC (opAmp)

- Followers
- Inversion

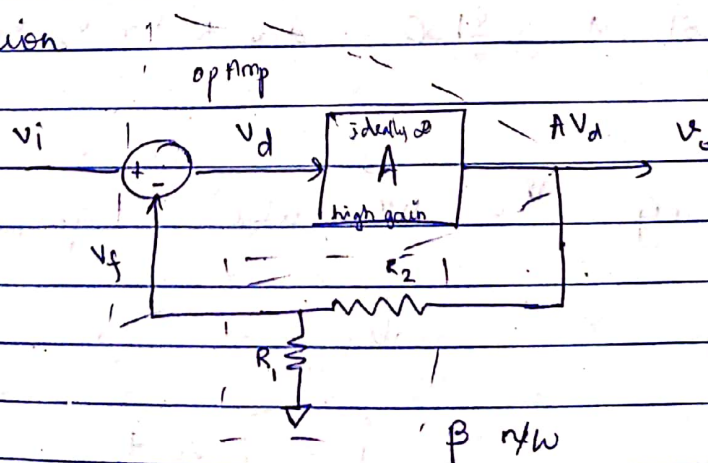


(1) follower

if OpAmp is unsaturated

$$v_d = v_i - v_f$$

$$v_o = A v_d$$

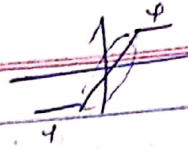

$$v_d = \frac{v_o}{A} = \frac{v_o}{10^5} = \frac{v_o}{\infty} \approx \frac{v_o}{10^5}$$

$$v_d \approx 0$$

$$v_i - v_f = 0$$

$$v_i = v_f$$

This is called as voltage follower property
 v_f follows v_i .

(2) Inversion property :

$$\frac{v_o}{v_i} = \frac{A}{1 + A\beta}$$

A - very large ($\infty \approx 10^5$)

$$\frac{v_o}{v_i} = \frac{1}{\beta}$$

→ inversion relation

v_o is independent of opAmp, depends on β & R/W .

$$\frac{v_o}{v_i} = \frac{1}{\beta}$$

(in denominator, so called inversion)

Because of these 2 properties, called linear IC.

1. Why OpAmp is called linear IC?

→ OpAmp is a linear device, built using non linear devices. Due to its dominant negative feedback it acts as a linear device.

2. What do you mean by harmonic distortion?


→ Along with the linear component, the non linear components adding up to the output of signal is known as harmonic distortion.

3. What is loop gain, improvement factor.

→ loop gain = $A\beta$

improvement factor = $1 + A\beta$

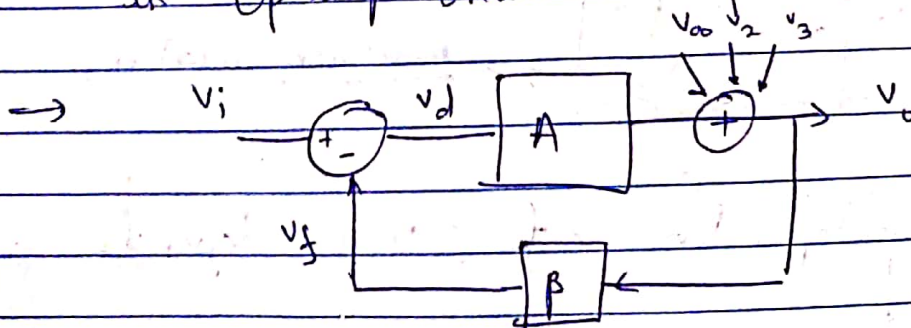4. Explain the process of amplification taken in Op-amp under -ve feedback condition



5. State the condition for Op-amp to operate in linear mode of operation.

→ Op-amp must have a dominant -ve feedback so that the output is unsaturated.

6. What is meant by follower property and inversion property.

→ When the Opamp is operating under linear mode.


- The input follows the feedback voltage. This property is known as follower property.
- Inversion property is

$$V_o = \frac{V_i}{\beta}$$

$$\frac{V_o}{V_i} = \frac{1}{\beta}$$

The gain is independent of opamp A it only depends on β n/w.

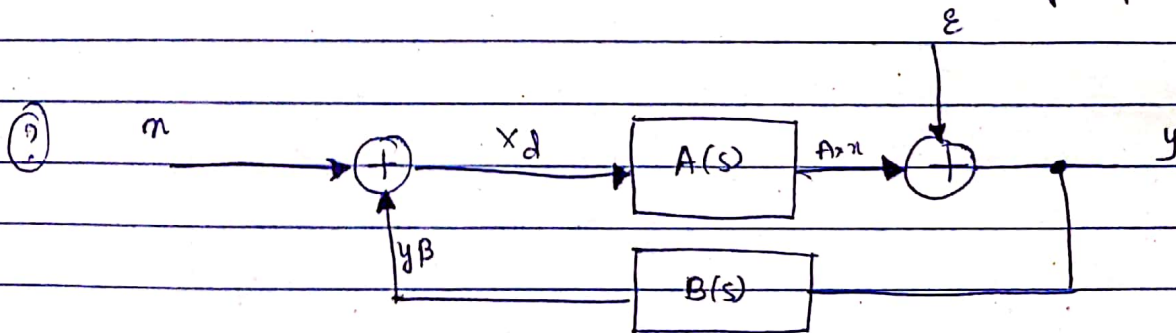Since gain is dependent on inverse of β , it is known as inversion property.



$$y = \frac{Ax + E}{1 + AB}$$

$$\frac{A}{1 + AB}$$

$$X_d = X + yB \quad y = AX_d$$

$$y = Ax_d = A(x + yB)$$

$$y(1 - AB) = Ax$$


$$\boxed{\frac{y}{x} = \frac{A}{1 - AB}}$$

NOTE: if $AB < 1 \rightarrow$ negative feedback

$AB > 1 \rightarrow$ oscillations

$$AB = -1 \quad \text{+ve}$$


polar plot

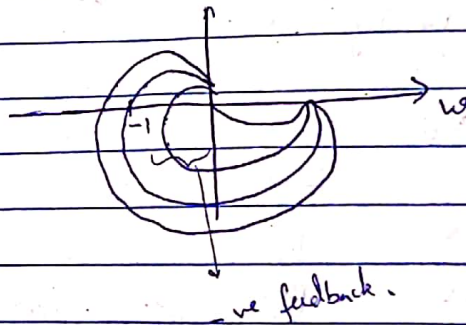

Linear Symmetric Networks

For a linear system, it has to obey


- Homogenous
- Superposition principle

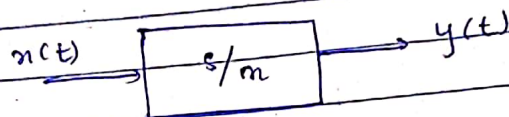

$$\alpha x_1(t) + \beta x_2(t) \longrightarrow \alpha y_1(t) + \beta y_2(t)$$

- Each component is independent of each other

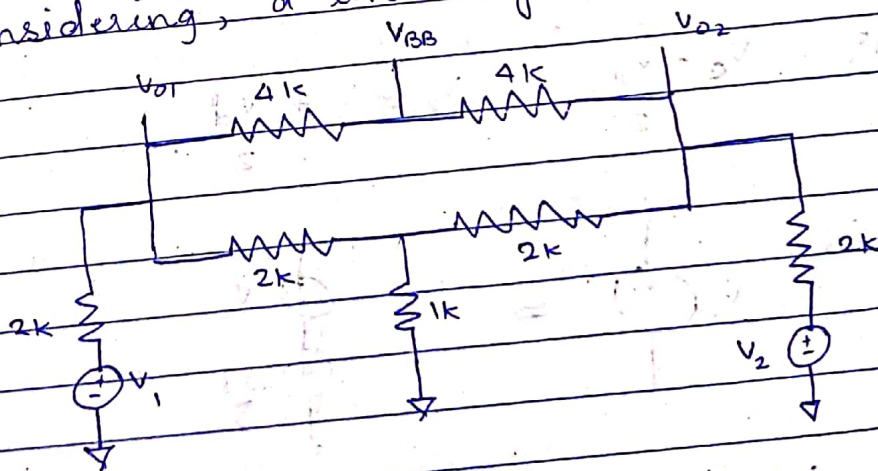Considering, a linear symmetric circuit -



$$V_{cm} = \frac{V_1 + V_2}{2}$$


$$V_d = V_1 - V_2$$

$$V_1 = -\frac{V_d}{2} + V_{cm}$$

odd component

$$V_2 = +\frac{V_d}{2} + V_{cm}$$

Because of symmetric of network

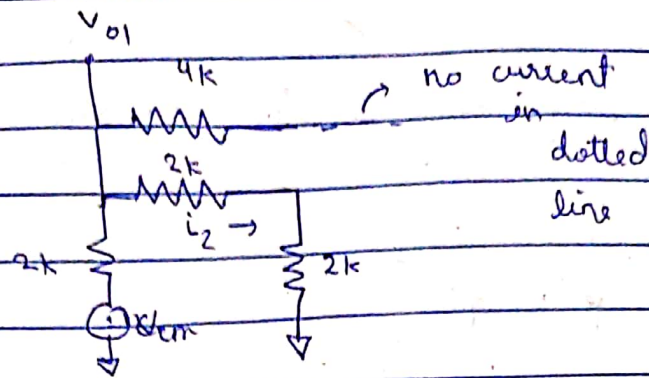

Here $V_{01} = V_{02}$

Symmetric


ckt

even

$$\frac{0.20}{\pm 0.01} = 2$$

$$V_1 = \frac{V_e - V_d}{2}$$

$$V_2 = V_c + \frac{V_d}{2}$$

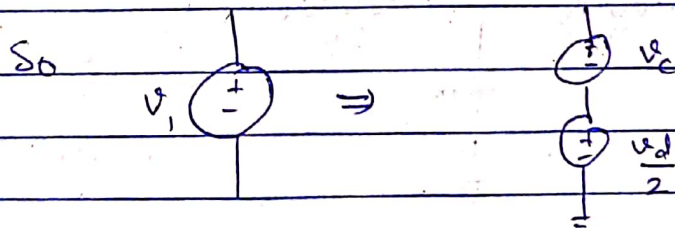

splitting v_1 & $v_2 \rightarrow$ in this form.

Once we consider V_C then $\frac{V_D}{2}$ then the DC bias V_{BB} .


Diagram illustrating a three-output buffer configuration:

The diagram shows an input i/p connected to a three-output buffer. The three outputs are labeled:

- $v_{o1} (v_c) = v_{o2}$
- $v_{o2} (v_{d/2}) = v_{o2}$
- $v_{o3} (v_{BB}) = v_{o2}$

We can calculate v_1, v_2 with KVL or KCL but it tedious.

So we do -

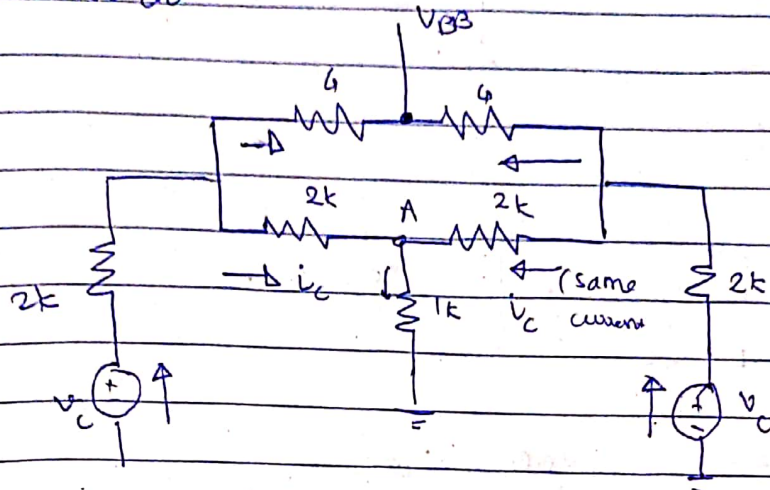


At node A, the summation of both current pass i.e. $2i_c$


$$2i_c \times 1k = 2i_c kV$$

$$i_c \times 2k = 2i_c kV$$


Meaning,

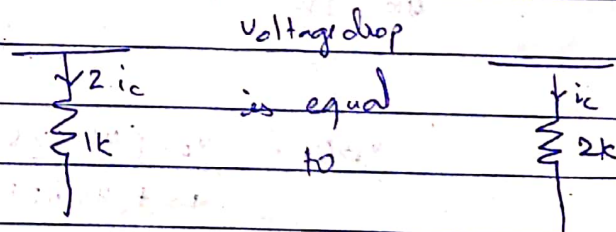

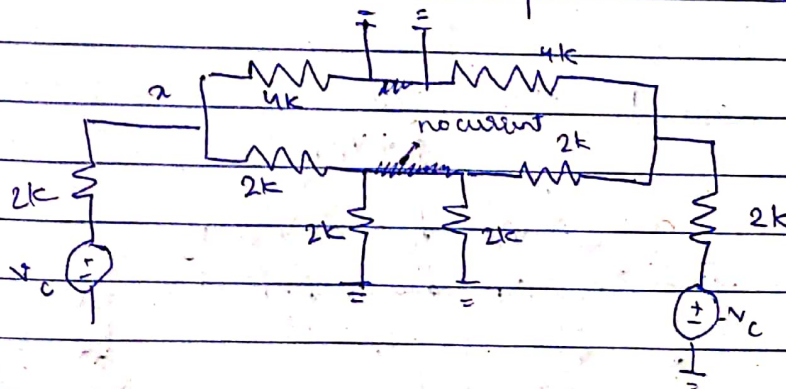So that we can split the circuit in 2 parts




The effective ckt

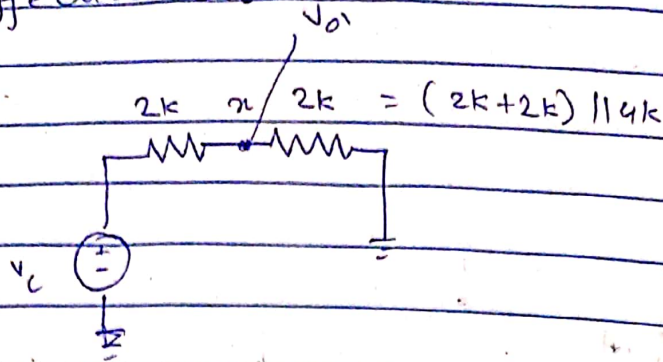


$$V_{O1} = \frac{V_C}{2} = V_{O2}$$

② Now for V_{BB}

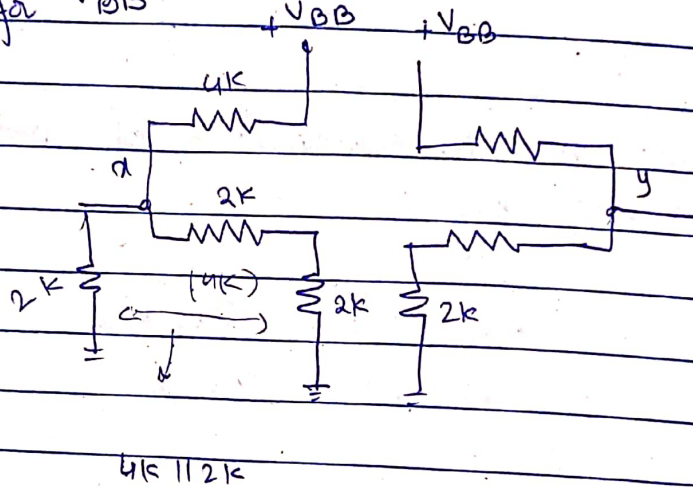

$$V_{BB} = \frac{V_{O1} (4k \parallel 2k)}{4k + (4k \parallel 2k)} = \frac{V_{O2} (4k \parallel 2k)}{4k + (4k \parallel 2k)}$$

③ With respect to $V_d/2$

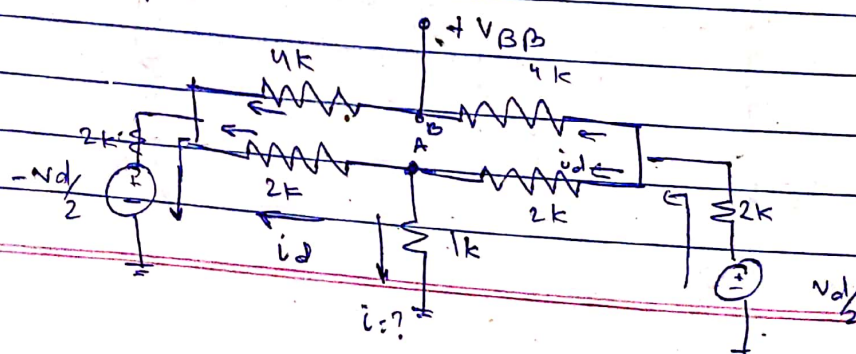


Here it is 0 as same current i_d flows from $2k$ to $2k$.

$$V_n \left(\frac{1}{r_{ds}} + g_m \right) = \frac{V_n}{1 + g_m r_{ds}} \quad (2)$$


So voltage at A is '0V'
 i.e. for 'B' node

So the entire line becomes '0' potential

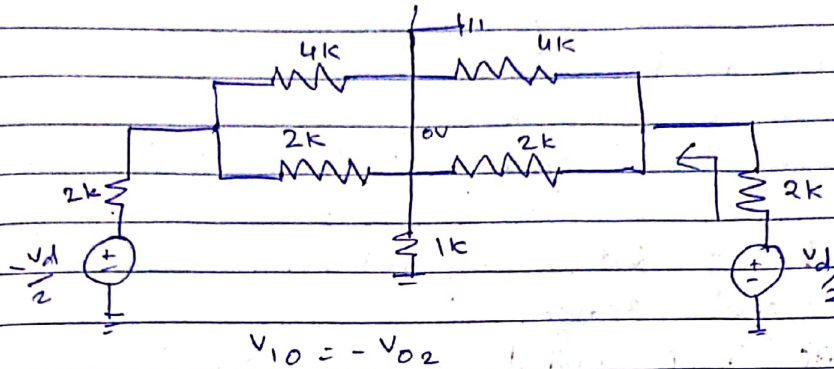


So whenever we have a symmetric network, we try to solve by superposition.

Differential Amplifier

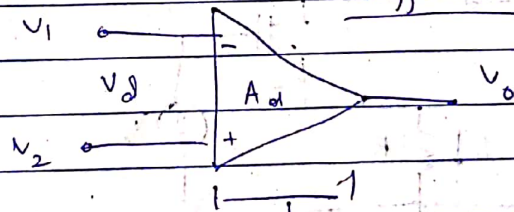

Amplifier the diff. in signal

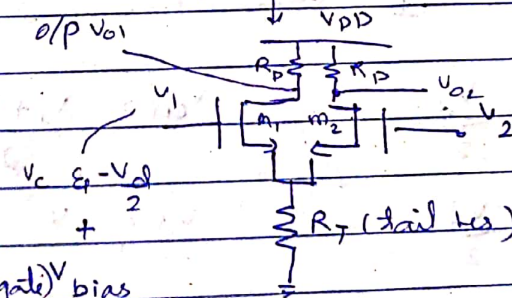

Basic differential amp.

R_D is the load for ckt.


(To provide at gate) V bias voltage)

Differential Amplifier Basics

- Basic differential amplifier
- common mode signals
- difference mode gain
- common mode gain
- difference mode gain

To make it better by reducing common mode signal range

The diff mode signal

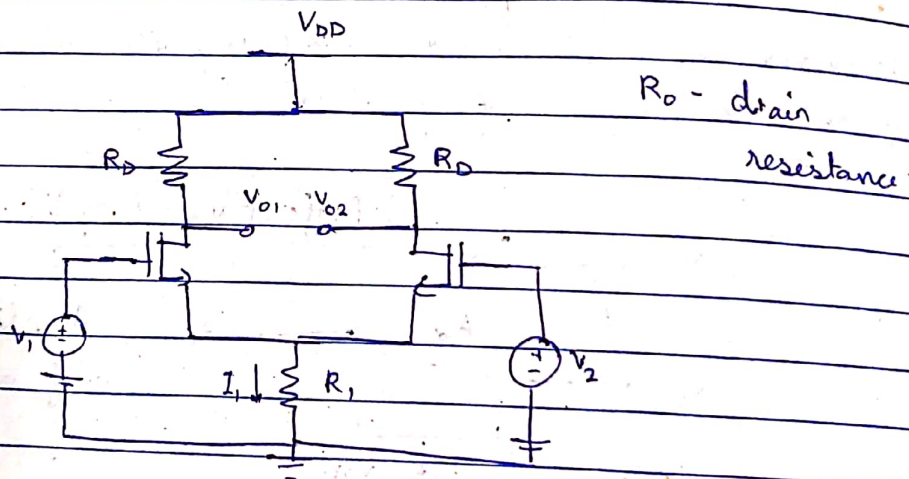

$$V_1 = V_c + \frac{V_d}{2}$$

$$V_{cm} = \frac{V_1 + V_2}{2}$$

$$V_2 = V_c - \frac{V_d}{2}$$

$$V_d = V_1 - V_2$$


The differential amplifier is biased and operated in the 'small signal' range

The amplifier is considered a linear system

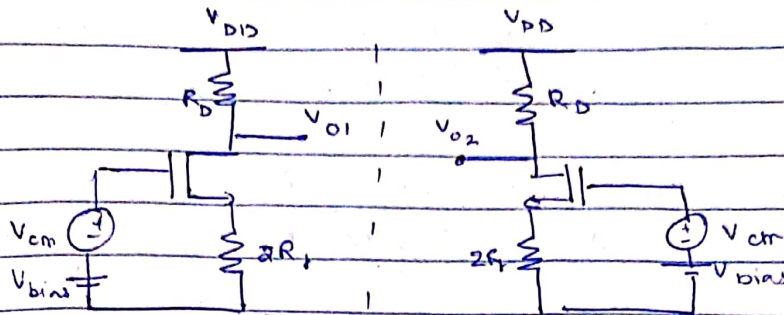1.1 / 1 + a ... etc

V_{bias} is voltage req. by device to work in saturation.

difference mode signal $+\frac{V_d}{2}$ & $-\frac{V_d}{2}$




$$V_{O1} = V_{O2} = \frac{-\mu R_D V_{cm}}{R_D + R_D + (1+\mu)2R_s}$$

$$A_c \approx \frac{-\mu R_D}{(1+\mu)2R_s} \approx \frac{-R_D}{2R_s}$$

Single ended o/p common mode gain

$$A_c = \frac{-R_D}{2R_s}$$

Difference mode analysis

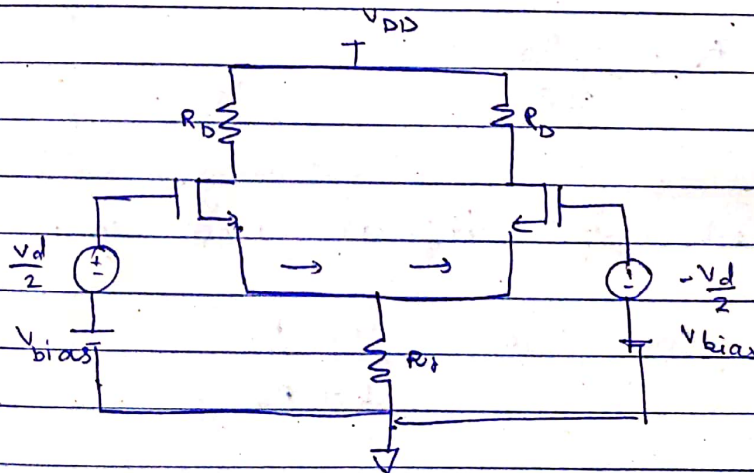


$$V_1 = V_c + \frac{V_d}{2}$$

$$V_2 = V_c - \frac{V_d}{2}$$

$$A_{d1} = \frac{V_{o1}}{V_d} = - \frac{g_m}{2} \frac{r_{ds} R_D}{(R_D + r_{ds})}$$

$$A_{d2} = \frac{V_{o2}}{V_d} = \frac{g_m}{2} \frac{r_{ds} R_D}{(r_{ds} + R_D)}$$
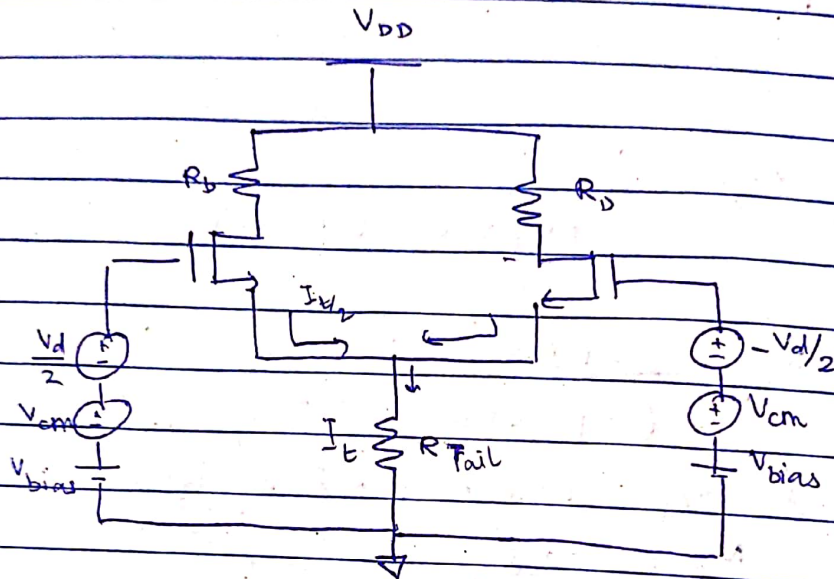
$$A_{d2} - A_{d1} = \frac{V_{o2} - V_{o1}}{V_d} = \frac{g_m}{2} \frac{r_{ds} R_D}{(r_{ds} + R_D)}$$



Single ended output common mode gain

$$A_c = - \frac{R_D}{2R_{T1}}$$

Single ended output difference mode gain


$$A_{d2} = \frac{g_m}{2} = \frac{r_{ds} \cdot R_D}{r_{ds} + R_D}$$

$$CMRR = \rho = \frac{A_{d2}}{A_c} = \frac{g_m}{2} \frac{r_{ds} R_D}{r_{ds} + R_D}$$







this signal means the range is not in saturation
'linear ranged' region.

3.1.19

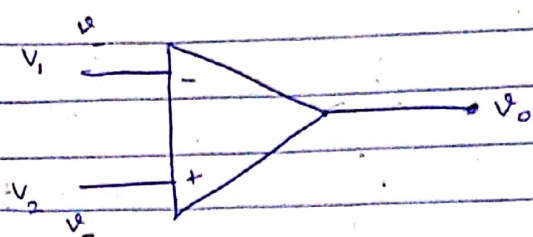


$$V_d = V_+ - V_-$$

$$V_c = \frac{V_1 + V_2}{2}$$

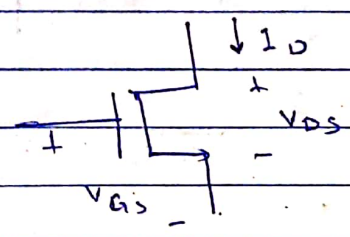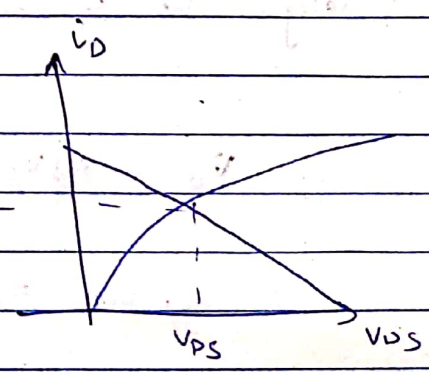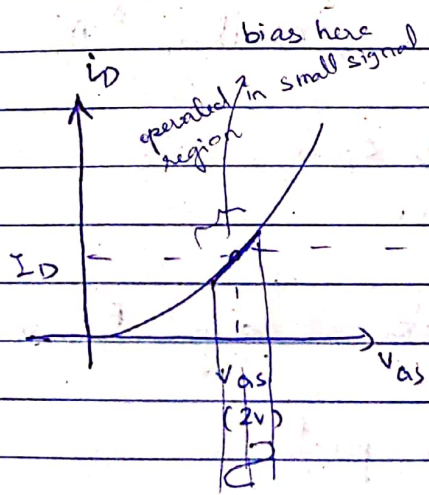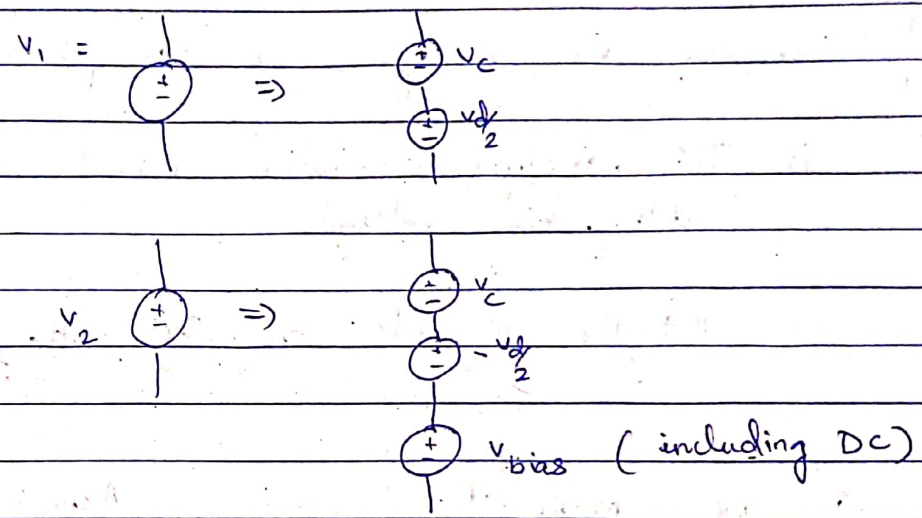

when we say signal, the terminals go off.

CS amplifier with "source degeneration"

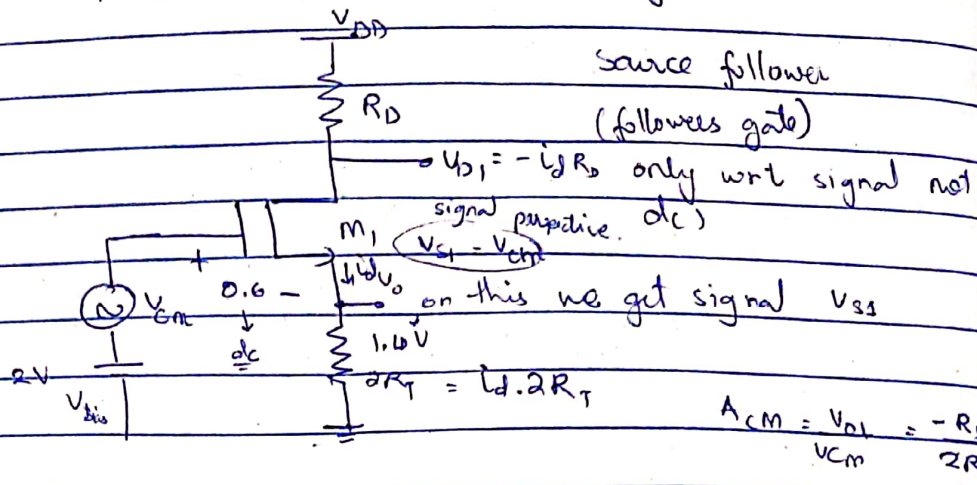

Whenever we analyse a amplifier,

(i) DC analysis: Device must conduct with bias voltage

(ii) Put the signals on DC voltage.


If we make $R_T = \infty$ $A_{cm} \approx 0$
larger the value of R_T , smaller A_{cm}

$$V_o = A_d V_d + A_{cm} V_{cm}$$

To remove A_{cm} , take a large R_T value
then voltage at that point

$$Ex, \quad I = \frac{1.4}{100m} = \text{very small}$$

$$V_{in} / (1 + g_m R_D)$$

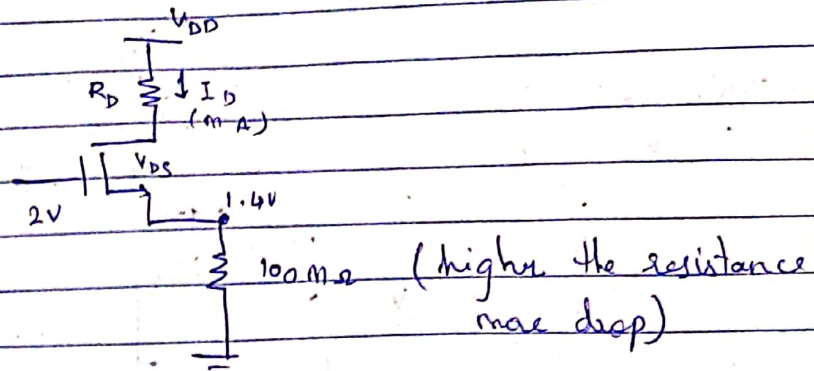


To make $A_{cm} \approx 0$,


$$R_T = \text{large } I_D$$

But signal current should not get disturbed

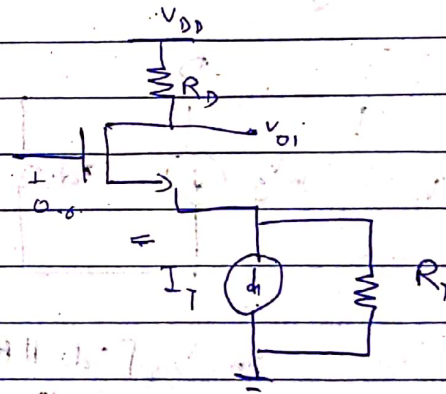
But changing R_T will not fix it
So we connect a current source



Difference mode Analysis

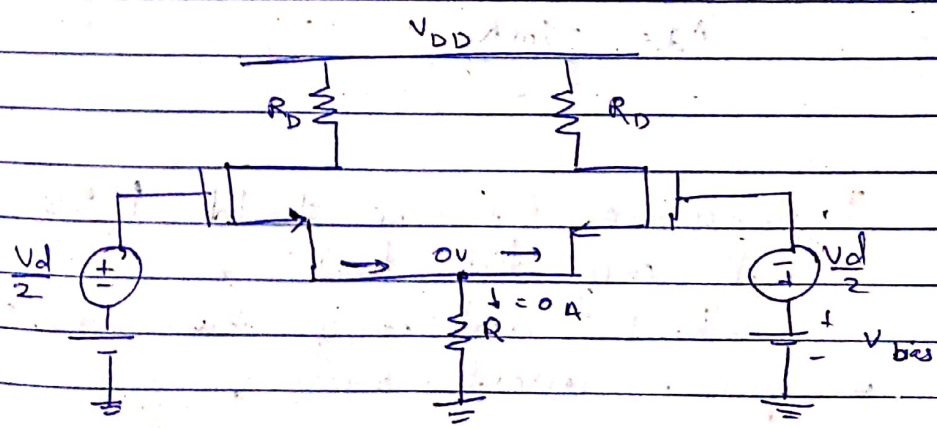


equivalent
1/2 ckt $\Rightarrow$

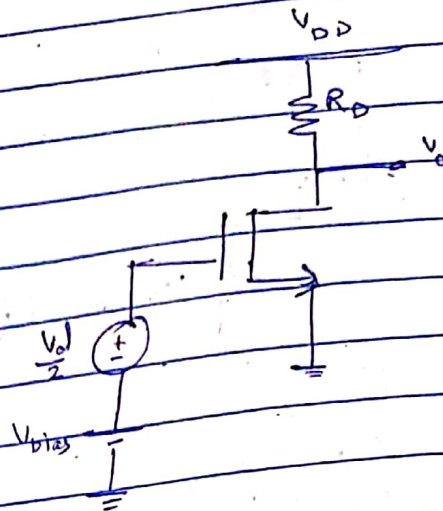

$$V_O = \frac{V_d}{2} - R_D i_D$$

Small signal model

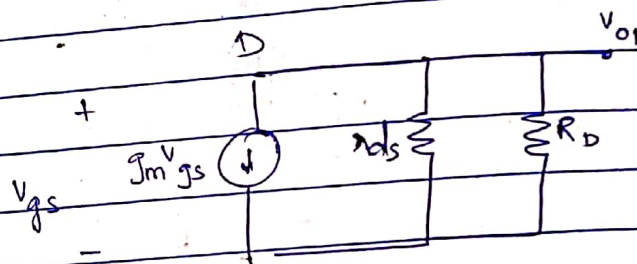

$$V_{O1} = -g_m V_{gs} [r_{ds} \parallel R_D]$$


V_{O1}	$= -g_m R_D$
V_d	2

$V_{gs} = \frac{V_d}{2}$

$$A_d = \frac{-g_m R_D}{2}$$

To increase A_d , we should $\uparrow R_D$
 not only till saturation,
 So without disturbing bias condition
 we put a current source.

 double o/p (in this case $A_{cm} = 0$)

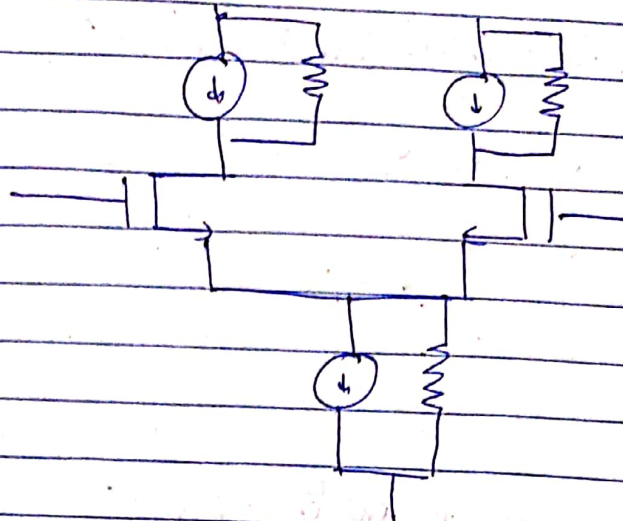

Single ended
o/p

Differential
o/p

V_{cm}

V_{o1}

$$= \frac{-R_D \cdot V_{cm}}{2R_T} = V_{o2}$$

$$V_{o2} - V_{o1} = 0$$

$$A_{cm} = \frac{-R_D}{2R_T}$$

$$V_{o2} = -V_{o1}$$

$$V_{o1} = -\frac{g_m R_D V_d}{2}$$

$$= \frac{g_m R_D V_d}{2}$$

$$V_{o2} - V_{o1} = g_m R_D V_d$$

$$A_d = -\frac{g_m R_D}{2}$$

$$A_d = g_m R_D$$

$$\text{Common mode rejection ratio} = \frac{A_d}{A_{cm}} = \frac{-g_m R_D}{\frac{-R_D}{2R_T}} = 2R_T$$

(ideally ∞)

$$= g_m R_T //$$

1. what is a differential signal?

→


$$v_d = v_1 - v_2$$



2. What is common mode signal?

→

$$v_{cm} = \frac{v_1 + v_2}{2}$$

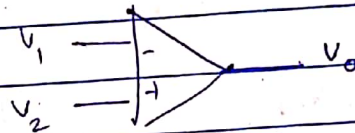

3) How do we amplify a differential signal

→ By using a differential amplifier we amplify a differential signal.

4) What is a differential amplifier?

→ A amplifier which amplifies the difference in input signals.

5) What is the purpose of differential amplifier?

→ To increase the bandwidth & reduce gain

6) What is the o/p if same signal is given to both inputs to differential amplifier?

→ there will be a small component of A_{cm} which will appear across N_0

$$V_o = A_d V_d + A_{cm} V_{cm}$$

↓
0

7] How does the gain of differential amplifier differ from common source stage

→ In case of diff. amp


$$A_d = -g_m R_D$$

while in case of C.S

$$A_d = g_m R_D$$

there is inversion in case of diff. amp.

8] What happens if $V_{cm} = 0$

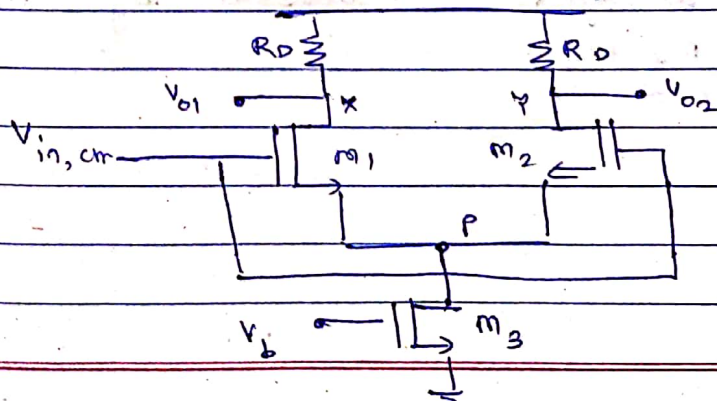


$V_{in, cm}$ i.e. dc is 0, it is not biased, so $V_{o1} \& V_{o2} = V_{DD}$

HW

Differential Amp

7.2.19

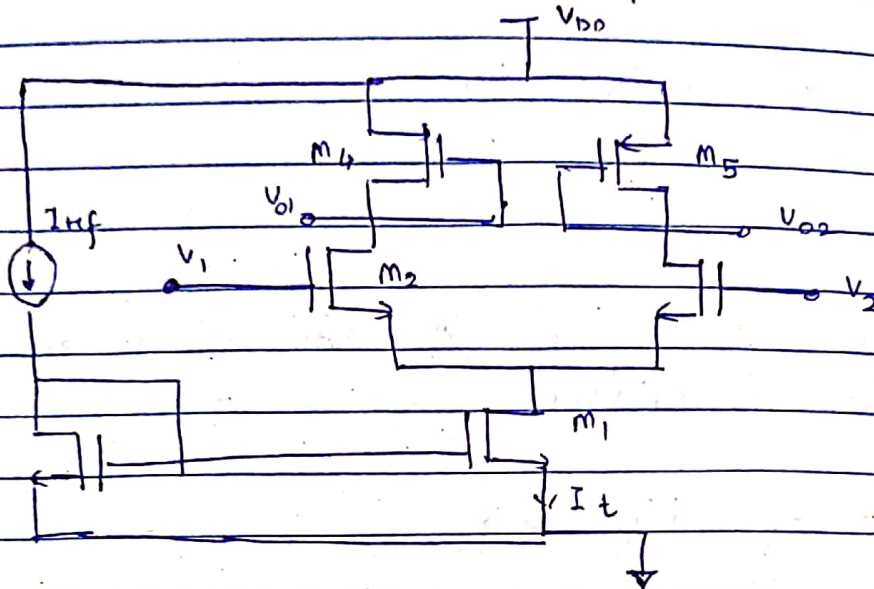

$$A_{d1} = \frac{V_{o1}}{V_d} = \frac{-g_{m2}}{2} \left[\frac{r_{ds2}}{1 + g_{m2} r_{ds2}} \right] = -0.5$$

low gain, high bandwidth



Active load Amplifier

It improves CMRR

differential gain is boosted by active loads (M_4, M_5)

Basic Differential Amplifier

7.2.19

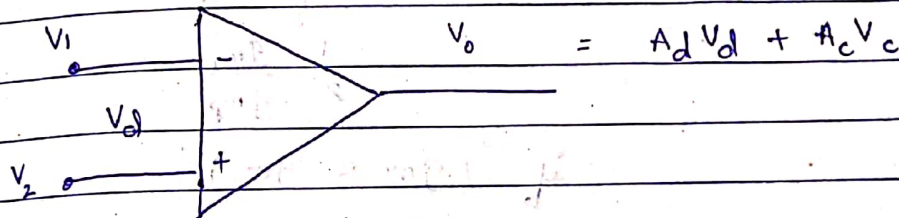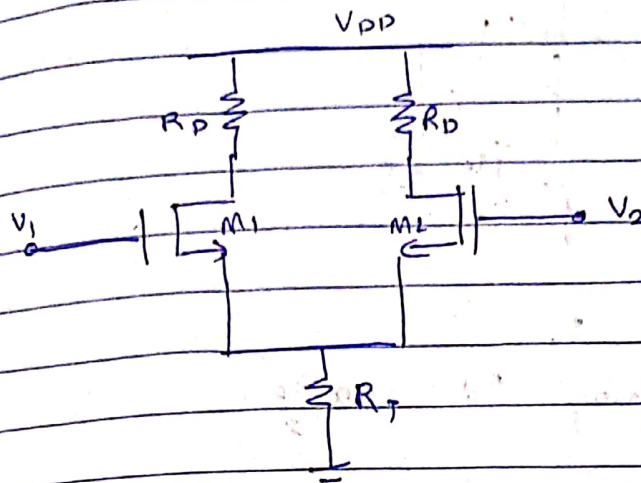

$$A_d = -g_m R_D \rightarrow \infty$$

$$A_c = -\frac{R_D}{2R_T} = 0$$

To increase A_d , $R_D \uparrow$

How to increase R_D ?

10 K, 100 K, 1 M, 100 M...

$\Rightarrow$ not possible $\because$ (it can make M_2 in triode region)

Replace R_D —
 — mos Diode
 — mos device (active load)


coz of the voltage it has to sustain

①

Resistance load.

Diff amp with diode load

So

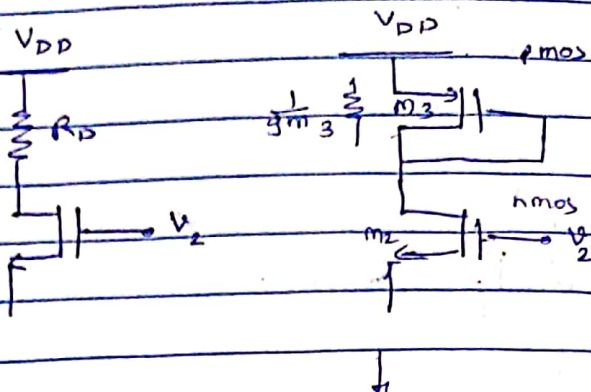

Replacing $A_d = -\frac{g_m R_D}{2}$

by $A_d = -\frac{g_{mn}}{2} \times \frac{1}{g_{mp}}$

$= -\frac{1}{2} \frac{g_{mn}}{g_{mp}}$

if $(g_{mn} \approx g_{mp})$


$= -\frac{1}{2} //$

So we conclude that we don't want to change R_D value as m_2 goes to triode region. replace R_D by MOS device then the gain is around -0.5 (doesn't act as amp but it is good ckt as everywhere we have saturation)

One more condition we look is,

we say $A_c = -\frac{R_D}{2 R_T}$ (ideally 0 or lowest)

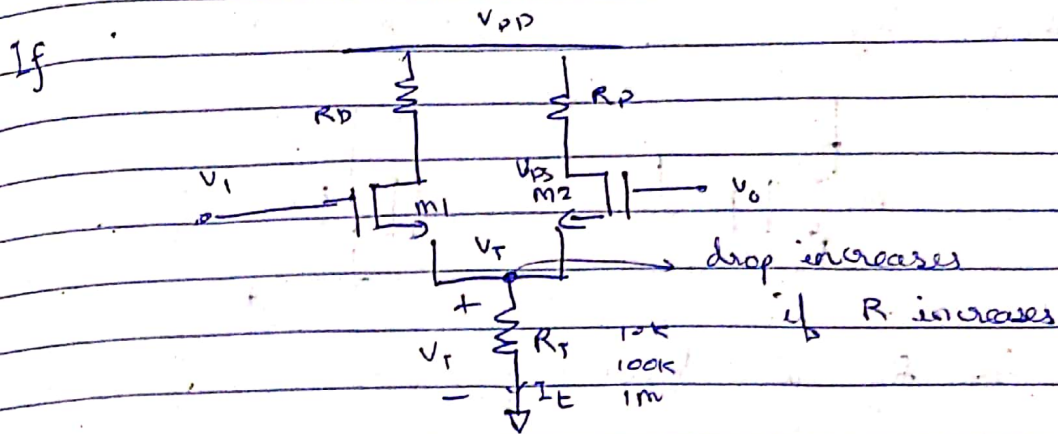To have $A_c \approx 0$, $R_T \rightarrow \infty$ (large value of R_T)




if $V_T \uparrow$, $V_{DS} \downarrow$


so M_2 can go into triode region

I_t - changing

I_t can go on reducing & into triode


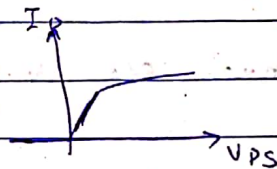


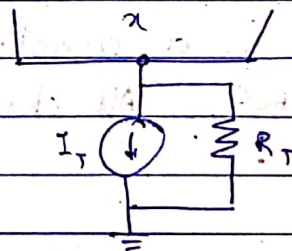So, a soln for this is replace R_T by current source.




we want current to be fin & R_T to change.

So we replace R_D by nmos

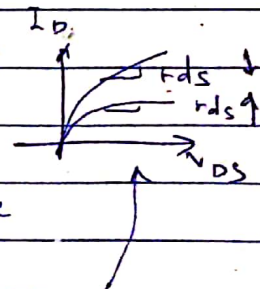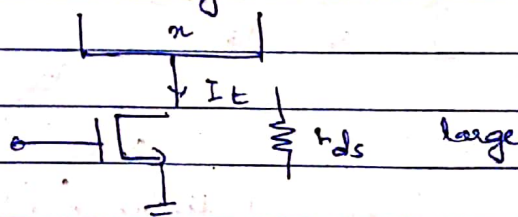


larger the r_{DS}
flatter the I_D curve


Then why do we need m_0 ?

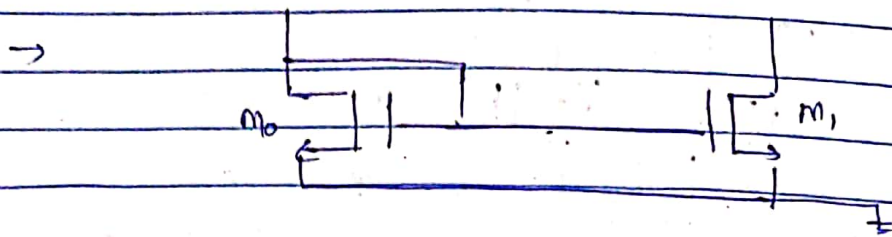

In fig, we have

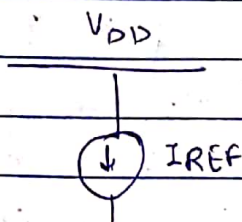


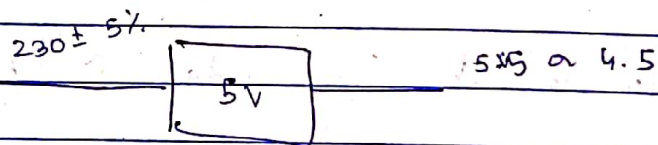In reality, there are variations in ^{supply} voltages



so we need to have a const. current / voltage

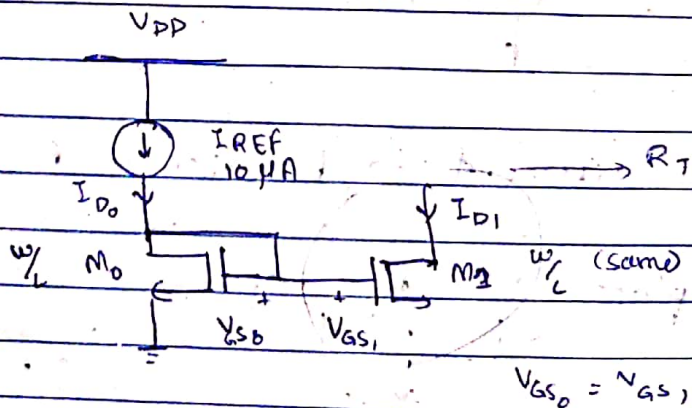So we have I_{ref} . (All ckt must have I_{ref})



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \text{ (fixed)} (V_{GS} - V_{th})^2$$

$$I_D = (f_{nd}) \times V_{GS}$$

$$I_{D0} = I_{REF} = 10 \mu A$$


$$I_{D1} = I_{D0}$$

So to bias M_1 , we take M_0 , to make V_{GS} same for same current (I_{D0} & I_{D1}) to flow. If we want different current then we change W/L .

So we wanted to make $A_{d1} = -g_{m1}R_{D1}/2$

$$A_{c1} = -R_{D1}/2R_{T1}$$

is achieved by putting diodes.

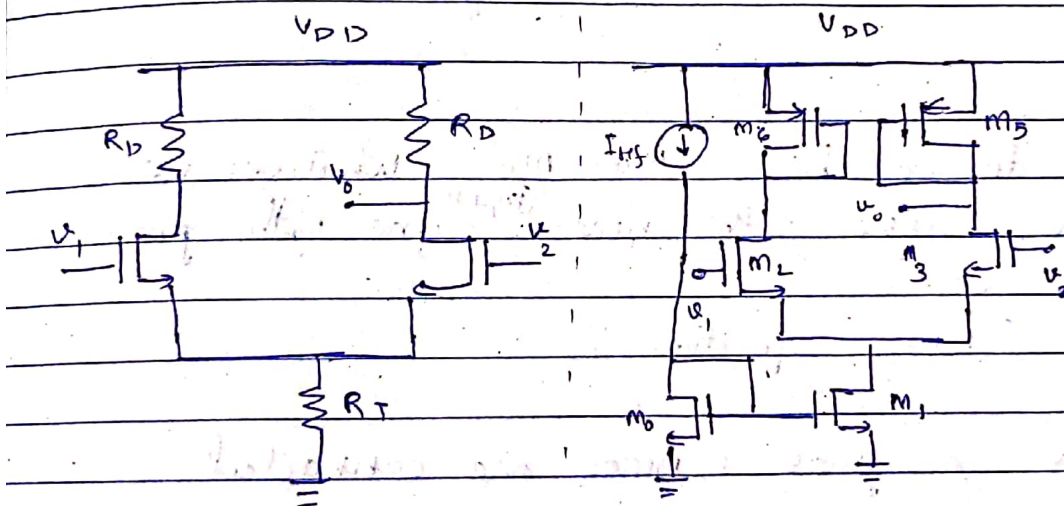


$$A_{d1} = \frac{V_{O1}}{V_d} = \frac{-g_{m2}}{2} \left[\frac{r_{ds2}}{1 + g_{m4}r_{ds2}} \right]$$

$$= -0.5$$

$$= -A_{d2}$$

② Differential Amplifier with Active load

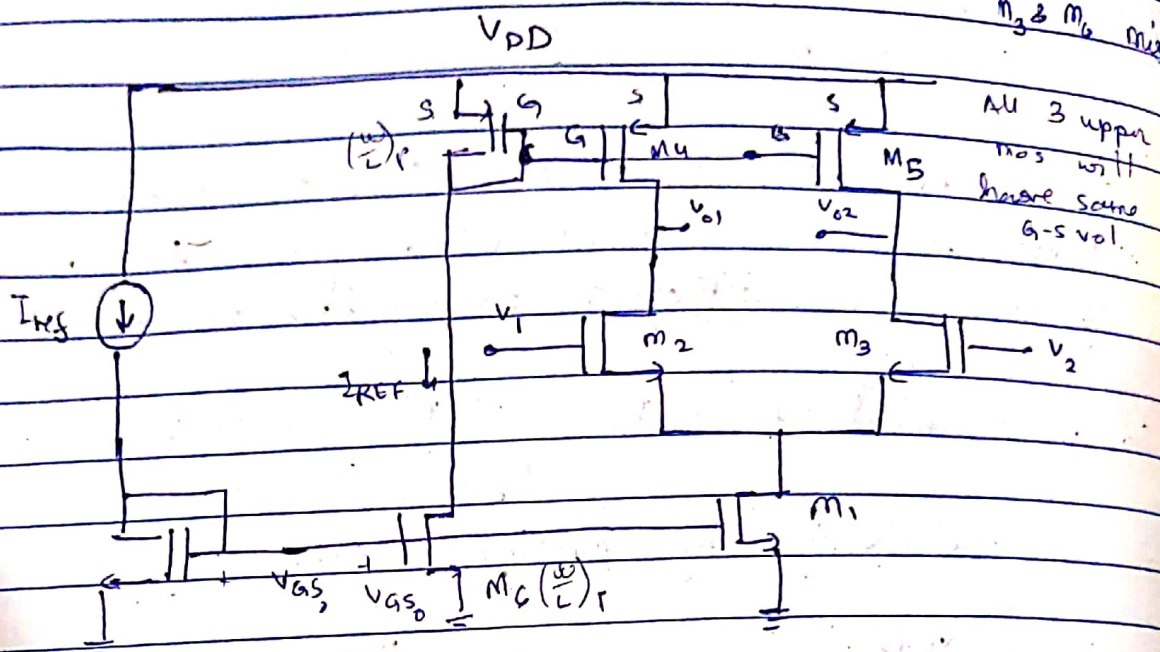
Another topology to increase ΔI & $A_c \downarrow$.




Now do we bias m_4 m_5 whatever we have done with nmos, same with pmos

But a basic question is


when a pmos & nmos are connected

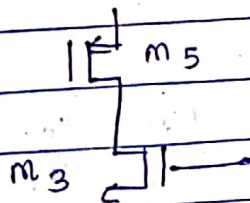


Ideally

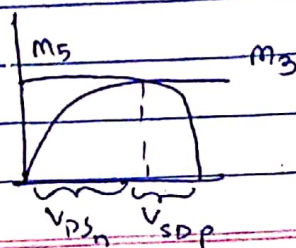

Reality

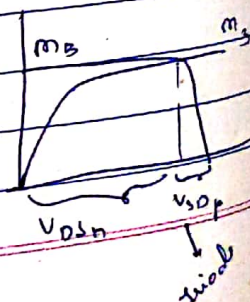


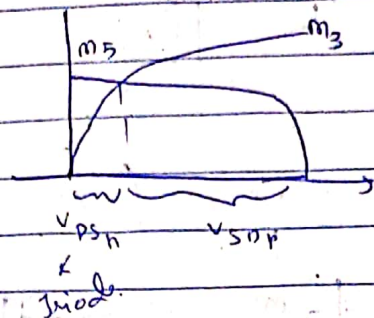There is a mis-match b/n m_5 & m_3
 always one of the device will go in triode.



So we can't connect $nmos$ & $pmos$.

Case: Feedback

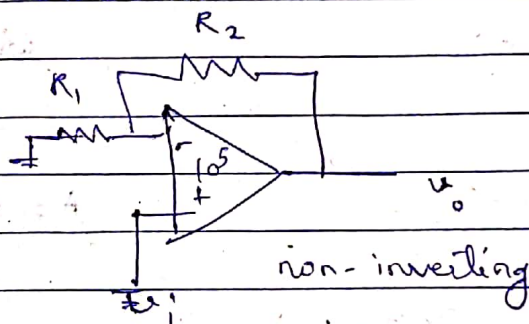


$$A = 1 + \frac{R_2 (1k)}{R_1 (1k)} = 2$$

So here also we try to build a feedback
 to keep ckt linear.

$V_{DD} = 5V$

($V_2 \approx V_O \approx 180$ phase)

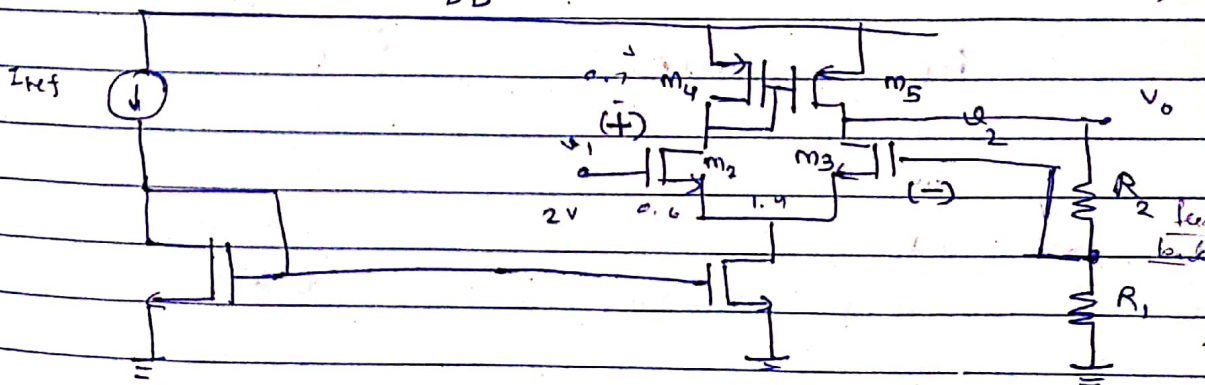


③ 5 - pack differential amp

2-stage OpAmp.

L.N Gd CMOS
a Batist

7 pack differential amplifier

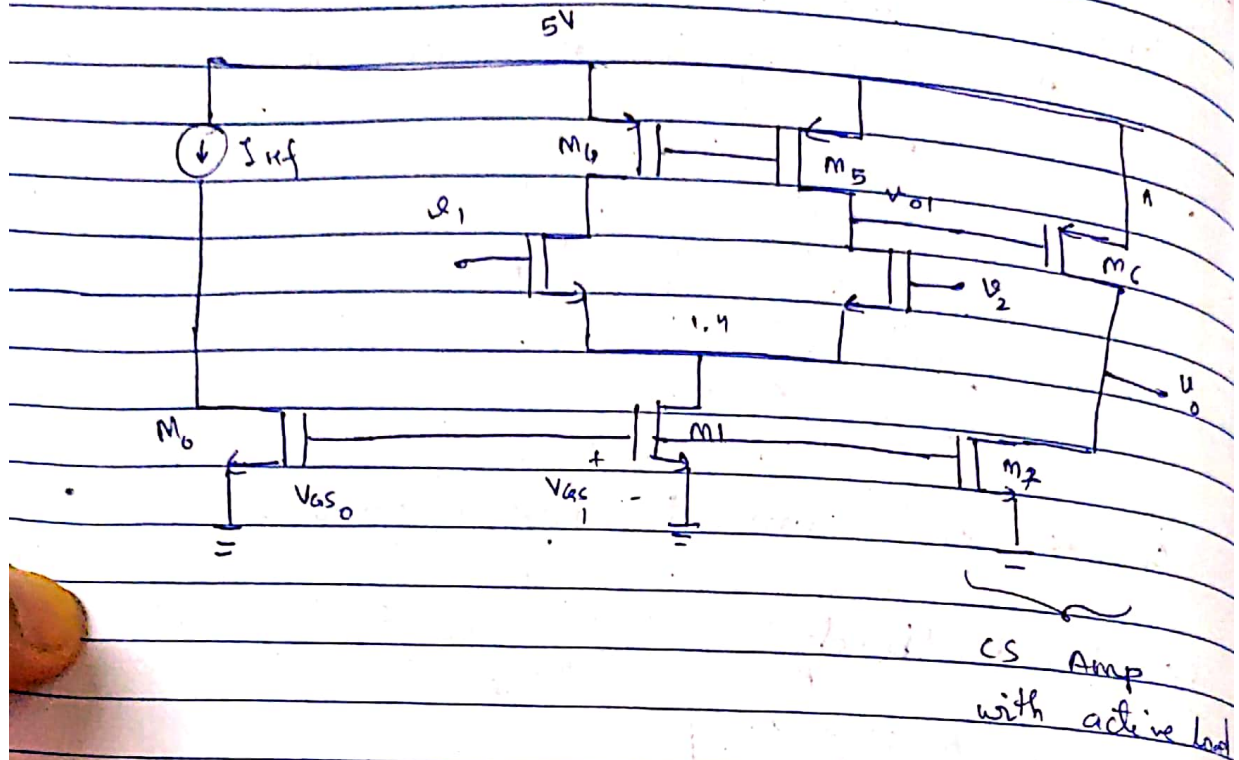

Post test

$$A = 5$$

$$V_0 =$$

$$R_2 = 30k$$

$$R_1 = 10k$$

$$\frac{V_0}{V_i}$$

$$20 \log 106$$

To design a OpAmp

- MOS structure

* CS

- $I_D \sim \frac{V_{GS}^2}{V_{DS}}$

CG

g_m


CD

r_{ds}

CMRR

- Temp variation

DA

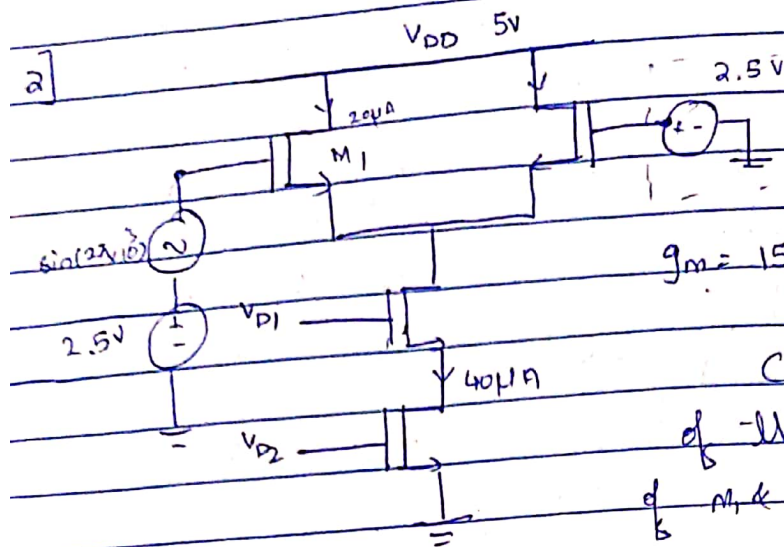


Calculate AC content of the drain current of M_1 & M_2 if $V_{i1} = 2.5V + 1 \times 10^{-3} \sin 2\pi \times 10^3 t$

$$i_D = I_D + i_d$$

$$= 20\mu A + i_d$$

To find i_d
eq. model

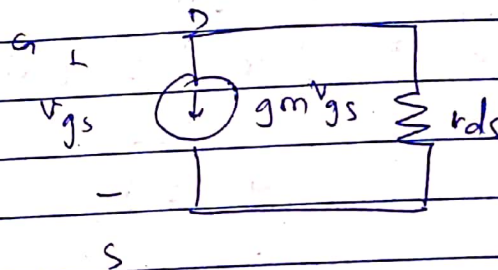

$$i_d = g_m v_{gs}$$

$$v_{gs1} \text{ \& } v_{gs2} =$$

$$i_d = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{gs} - V_t)^2$$

$$20\mu A =$$

$$-V_{gs2} + V_{gs2} - 1mV = 0$$

M_1 & M_2 are matched

$$V_{gs1} = -V_{gs2}$$

$$V_{gs1} = 0.5mV$$


$$i_{d1} = 150\mu A \times 0.5m$$

$$= 75nA$$


$$i_{d2} = -75nA$$

$$V_{i1} = 1m \sin 2\pi \times 10^3 t$$

$$V_{i2} = 0$$

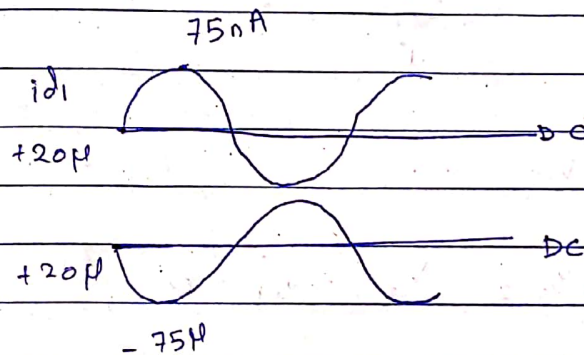

②

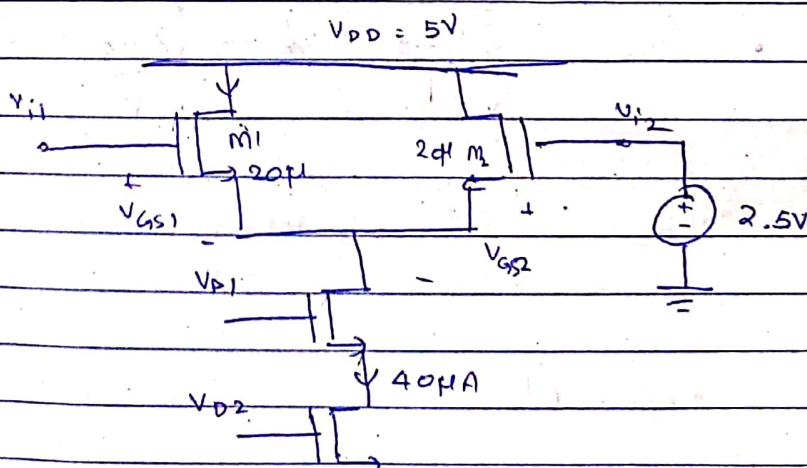

Cal. the min & max vol. in the gate of M_1 that ensures neither M_1 nor M_2 shut off

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$(V_{GS} - V_t)^2 = \frac{2 I_D}{\mu_n C_{ox} W/L}$$

$$V_{GS} = \sqrt{\frac{2 I_D}{\beta}} + V_t$$

$$V_{GS1} = \sqrt{\frac{2 I_{D1}}{\beta}} + V_t$$

$$V_{GS2} = \sqrt{\frac{2 I_{D2}}{\beta}} + V_t$$

KVL from V_{i2} to V_{i1}

$$+V_{i2} - V_{GS2} + V_{GS1} - V_{i1} = 0$$

$$V_{i2} - V_{i1} = V_{GS2} - V_{GS1}$$

$$V_{i2} - V_{i1} = \sqrt{\frac{2 I_{D2}}{\beta}} + V_t - \sqrt{\frac{2 I_{D1}}{\beta}} + V_t$$

$$V_{i2} - V_{i1} = \sqrt{\frac{2 (I_{D2} - I_{D1})}{\beta}}$$

$$\mu_n C_{ox} = 120 \mu A/V^2$$

$$\frac{W}{L} = \frac{10}{2}$$


$$v_{i2} = 0 \Rightarrow I_{D1} = 40 \mu A, I_{D2} = 0$$

$$\begin{aligned} +v_{i1} &= -\sqrt{\frac{2}{\beta}} \sqrt{I_{D1}} \\ \text{max } v_{o1} &= -0.365 V // \end{aligned}$$

$$\text{max} = 2.5 + 0.365 V = 2.865 V$$

$$\text{min} = 2.5 - 0.365 = 2.135 V$$

(9)

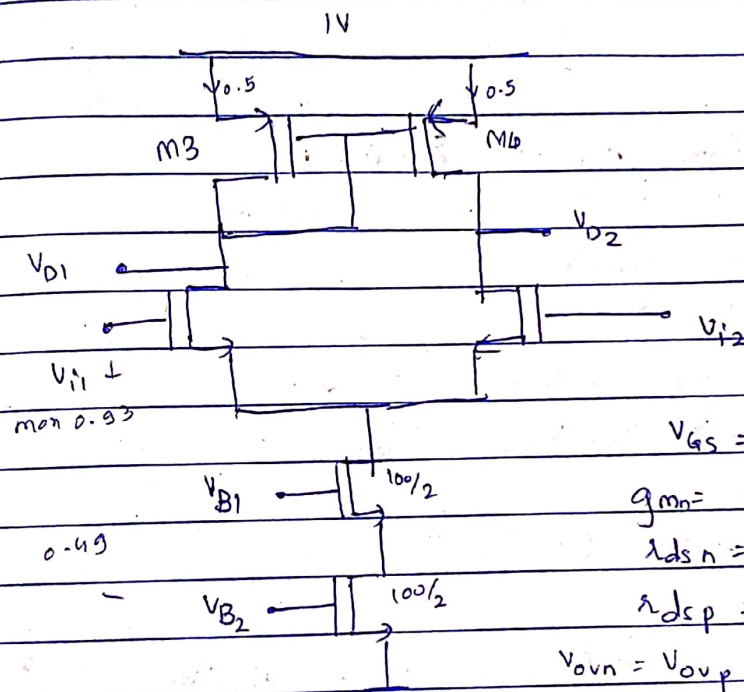

$$V_{GS} = V_{SG} = 350 \text{ mV}$$

$$g_{mn} = g_{mp} = 150 \mu A/V$$

$$r_{dsn} = 167 \text{ k}\Omega$$

$$r_{dsp} = 333 \text{ k}\Omega$$

$$V_{ovn} = V_{ovp} = 70 \text{ mV}$$

Determine the small signal gain & the i/p (cmr)
common mode rejection ratio

$$V_{DS(sat)} = V_{SD(sat)} = 50 \text{ mV}$$

$$\rightarrow A_d = \frac{v_o}{v_{in}} = 16.7$$


diff gain

$$\frac{v_{o2} - v_{o1}}{v_d} = ?$$

$$\text{CM (max)} V = 0.93 V$$

$$\text{min} = 0.49 V$$

DA Basics.

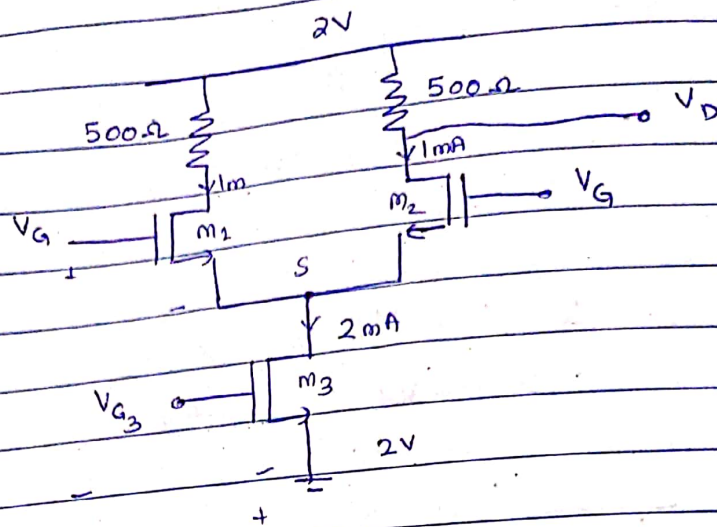

$$\mu_n C_{ox} \left(\frac{W}{L} \right) = 8 \text{ mA/V}^2$$

$$V_T = 0.5 \text{ V}$$

$$\lambda = 0$$

$$V_{OV3} = 0.5 \text{ V}$$

Compute V_S , V_D , V_{DS} & V_{GS} .

(i) $V_G = 0$ (2) $V_G = 1$

$$\rightarrow I_D = 1 \text{ mA} = \frac{1}{2} K_n' \left(\frac{W}{L} \right) (V_{GS1} - V_T)^2$$

$$1 \text{ m} = \frac{1}{2} \times 8 \times 10^{-3} (V_{GS1} - 0.5)^2$$

$$2 \text{ m} = 8 \times 10^{-3} (V_{GS1} - 0.5)^2$$

$$\boxed{1 \text{ V} = V_{GS1}}$$

Using KVL,

V_S is wrt
gnd. so 2V
won't come.

$$+ V_S + V_{GS1} - V_G = 0$$

$$+ V_S + 1 = 0$$

$$\boxed{V_S = -1 \text{ V}}$$

$$V_D = V_{DD} - I_D R_D$$

$$= 2V - (1m)(500)$$

$$V_{D1} = 1.5V$$

$$V_{DS} = V_D - V_S$$

$$= 2.5V //$$

Case 2: When $V_G = 1V$

$$I_D = \frac{1}{2} K_n \left(\frac{W}{L} \right) (V_{GS1} - V_t)^2$$

$$1m = \frac{1}{2} (8 \times 10^{-3}) (V_{GS1} - 0.5)^2$$

$$V_{GS1} = 1V$$

$$V_{GS1} = 1$$

$$V_G - V_S = 1$$

$$1 - V_S = 1$$


$$V_S = 0$$

$$V_D = V_{DD} - I_D R_D$$

$$V_D = 1.5V$$

$$V_{DS} = 1.5V$$

Diode load :-

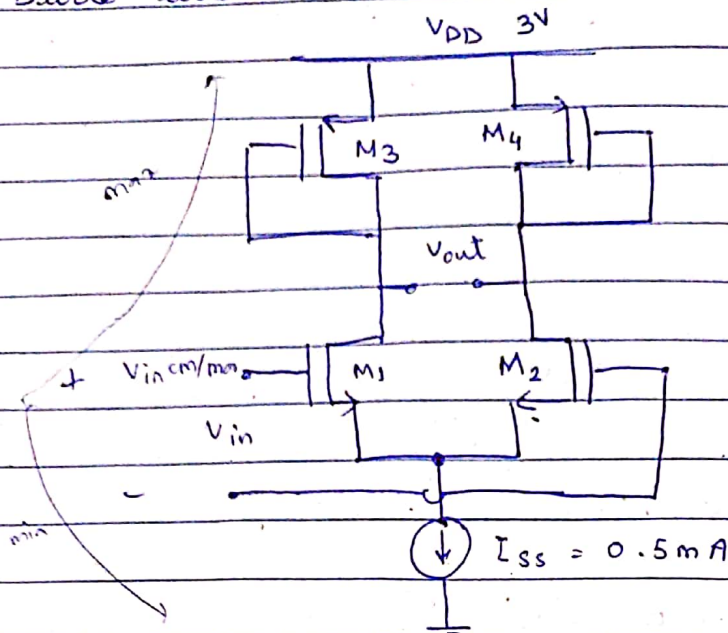

$$\left(\frac{W}{L}\right)_{1,2} = \frac{50}{0.5}$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{10}{0.5}$$

I_{ss} is implemented using NMOS of

$$\left(\frac{W}{L}\right)_{ss} = \frac{50}{0.5}$$

$$\textcircled{1} V_{in cm/min} = ?$$

If differential amplifier at

i/p & o/p are small.

$$\textcircled{2} V_{in cm/max} = ?$$

$$V_{THN} = 0.7V$$

$$V_{THP} = -0.8V$$

$$\mu_{n,ox} = 134 \mu A/V^2$$

$$\mu_{p,ox} = 38 \mu A/V^2$$

$$\rightarrow A_d = \frac{-g_{m1}}{g_{m3}} = - \frac{\sqrt{\frac{1}{2} \mu_{n,ox} \left(\frac{W}{L}\right)_1 I_{D1}}}{\sqrt{\frac{1}{2} \mu_{p,ox} \left(\frac{W}{L}\right)_3 I_{D1}}}$$

$$A_d = - \frac{\mu_n (W/L)_1}{\sqrt{\mu_p (W/L)_3}} //$$

$$I_{ss} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_{ss} (V_{GS(ss)} - V_{THN})^2$$

$$0.5m = \frac{1}{2} \times 134 \times 10^{-6} (V_{GS(ss)} - 0.7)^2$$

$$(V_{GS(ss)} - V_{THN}) = V_{OVSS} = 0.273V$$

$$I_{D1} = \frac{I_{SS}}{2} = 0.25 \text{ mA}$$

$$(V_{GS1} - V_{THN}) = \sqrt{\frac{2 \times I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \times 100}} \quad 134 \mu$$

$$V_{OV1} = 0.193 \text{ V}$$

$$\begin{aligned} V_{GS1} &= V_{OV1} + V_{THN} \\ &= 0.193 + 0.7 \\ &= 0.893 \text{ V} // \end{aligned}$$

$$\begin{aligned} V_{in,cm} \Big|_{min} &= V_{GS1} + V_{OVSS} \\ &= 0.893 + 0.273 \\ &= 1.17 \text{ V} // \end{aligned}$$

$$V_{in,cm} \Big|_{max} = 2.09 \text{ V}$$

HW

$$A_d = \frac{-g_{m2}}{g_{m4}} = - \frac{\sqrt{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (I_{D2})}}{\sqrt{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_4 (I_{D4})}}$$

$$A_d = - \sqrt{\frac{\mu_n \left(\frac{W}{L}\right)_2}{\mu_p \left(\frac{W}{L}\right)_4}} //$$

$$I_d = - \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_4 (V_{GS4} - V_{THP})^2$$

$$0.25 \text{ mA} = - \frac{1}{2} \times 38 \times 10^{-6} \times \frac{10}{0.5} (V_{GS4} + 0.8)^2$$

$$V_{GS4} = 0.346 \text{ V}$$

KVL ① across V_{in} & SS

$$+V_{DSS} + V_{GS1} - V_{in cm}|_{max} = 0$$

KVL ② across V_{DD}

$$V_{DSS} + V_{OV1} + V_{GS3} - V_{DD} = 0$$

$$\begin{aligned} V_{DSS} &= V_{DD} - V_{OV1} - V_{GS3} \\ &= V_{DD} - (V_{GS1} - V_{THN}) - V_{GS3} \\ &= V_{DD} - V_{GS1} + V_{THN} - V_{GS3} \end{aligned}$$

$$\begin{aligned} V_{in cm}|_{max} &= V_{DSS} + V_{GS1} \\ &= V_{DD} - V_{GS1} + V_{THN} - V_{GS3} + V_{GS1} \end{aligned}$$

$$V_{in cm}|_{max} = V_{DD} - |V_{GS}| + V_{THN}$$

$$\begin{aligned} V_{GS3} &= ? \\ &= V_{THP} + \sqrt{\frac{2I_{O3}}{\mu_p C_{ox}(W/L)_3}} \end{aligned}$$

$$= 0.8 + \sqrt{\frac{2 \times 0.25 \times 10^{-3}}{38 \times 10^{-6} \times 20}}$$

$$= 1.61 \text{ V}$$

$$V_{in cm}|_{max} = 3 - 1.61 + 0.7$$

$$= 2.08 \text{ V}$$

H.W

Part B :-

If $V_{in,cm} = 1.2V$, sketch the small signal differential voltage gain as V_{DD} goes from 0-3V.

Q9] In above problem, if M_1 and M_2 have V_t mismatch of 1mV, calc. the CMRR.

Suppose M_1 & M_2 have a threshold vol of 1mV, what is the CMRR.

→ Both currents are different; $g_{m1} \neq g_{m2}$
 $g_{m3} \neq g_{m4}$

$$i_{D1} = \frac{1}{2} K_n' \frac{W}{L} (V_{GS1} - V_t)^2$$

$$i_{D1} = \frac{1}{2} \times 134 \times 10^{-6} \times (0.893 - 0.699)^2$$

$$i_{D1} = 13.4 \mu A \quad 0.25 mA$$

$$i_{D2} = \frac{1}{2} \times K_n' \left(\frac{W}{L} \right) (V_{GS} - (V_t - 1))^2$$

$$= \frac{1}{2} \times 134 \times 10^{-6} (0.893 - 0.699)^2$$

$$i_{D1} = g_{m1} V_{gs1}$$

$$= g_m [V_{in,cm} - V_s]$$

$$i_{D2} = g_{m2} [V_{in,cm} - V_s]$$

$$V_{out1} = -i_{D1} \times \frac{1}{g_{m3}} = -\frac{g_{m1}}{g_{m3}} [V_{in,cm} - V_s]$$

$$v_{out2} = -i_{D2} \times \frac{1}{g_{m4}}$$

$$= -\frac{g_{m2}}{g_{m4}} (v_{inCM} - V_S)$$


$$\frac{g_{m1}}{g_{m3}} = \frac{\sqrt{2I_{D1} \mu_n (C_{ox} (W/L)_1)}}{\sqrt{2I_{D3} \mu_p (C_{ox} (W/L)_3)}} = \frac{\sqrt{\mu_n (W/L)_1}}{\sqrt{\mu_p (W/L)_3}}$$

$$\frac{g_{m2}}{g_{m4}} = \frac{\sqrt{\mu_n (W/L)_2}}{\sqrt{\mu_p (W/L)_4}}$$

Since μ_n & $\frac{W}{L}$ are same for $m1, m2$

μ_p & $\frac{W}{L}$ are same for $m3, m4$

$$v_{out1} = v_{out2}$$

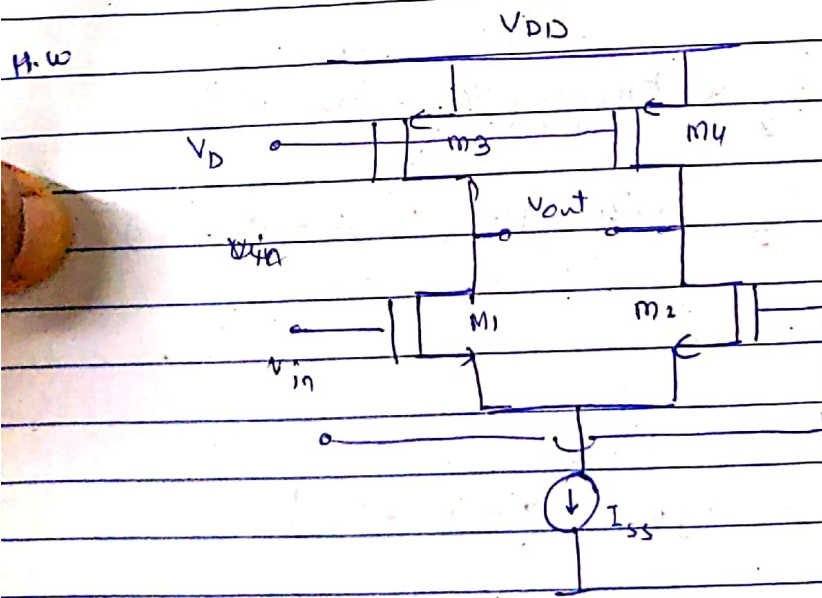

$$\left(\frac{W}{L}\right)_{m4} = \frac{50}{0.5}$$

$$I_{SS} = 1 \text{ mA}$$

① Calc. small signal P. Gain

$$\lambda_n = 0.1$$

$$\lambda_p = 0.2$$

② Find $v_{inCM} = 1.5V$
max o/p swing = ?

$$g_m = 3.66 \text{ mS}$$

$$\begin{aligned} \rightarrow r_{ds1} &= \frac{1}{\lambda_n \times I_{D1}} \\ &= \frac{1}{0.1 \times 0.5 \text{ mA}} \\ &= 20 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} r_{ds3} &= \frac{1}{\lambda_p I_{D3}} \\ &= \frac{1}{0.2 \times 0.5 \text{ mA}} = 10 \text{ k}\Omega // \end{aligned}$$

$$\begin{aligned} \text{Gain} = A_d &= -g_m (r_{ds1} \parallel r_{ds3}) \\ &= -3.66 \text{ m} \left[\frac{r_{ds1} \times r_{ds3}}{r_{ds1} + r_{ds3}} \right] \\ &= -3.66 \text{ m} \times \end{aligned}$$

$$\boxed{A_d = -24.5} //$$

$$\begin{aligned} \text{(b) Ans } V_{in} \text{ min o/p } V &= 0.8 \text{ V} \\ \text{max} &= 2.49 \text{ V} \end{aligned}$$

$$2(2.49 - 0.8) = 3.38 \text{ V} //$$


$$1.5 = (0.75 - 0.001)$$

KVL eq. to o/p min


$$\begin{aligned} +V_p + V_{ov1} - V_{out, \min} &= 0 \\ (V_p = V_{in, \min} - V_{GS}) \quad V_{out, \min} &= V_{in, \min} - V_{GS1} + (V_{GS1} - V_{THN}) \\ &= V_{in, \min} - V_{THN} \\ &= 1.5 - 0.7 \\ &= 0.8 \text{ V} // \end{aligned}$$

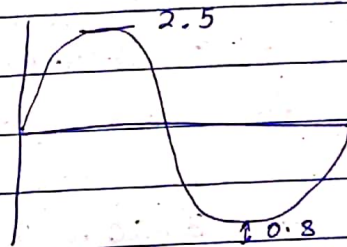18.2.19

$$\begin{aligned}
 * V_{out, max} &= V_{DD} - V_{SD3} (sat) \\
 &= V_{DD} - V_{OV3} \\
 &= V_{DD} - (V_{GS3} - V_{THP}) // \\
 &= V_{DD} - \left(\sqrt{\frac{2 I_{D3}}{\mu_p C_{ox} (W/L)}} + V_{THP} \right) \\
 &= 3 - \sqrt{\frac{2 \cdot 103}{38 \mu \times 100}} + 0.8 \\
 &= 3 - \sqrt{\frac{2 \cdot 103 (0.5 m)}{38 \mu \times 100}} \\
 &= 2.487 V //
 \end{aligned}$$


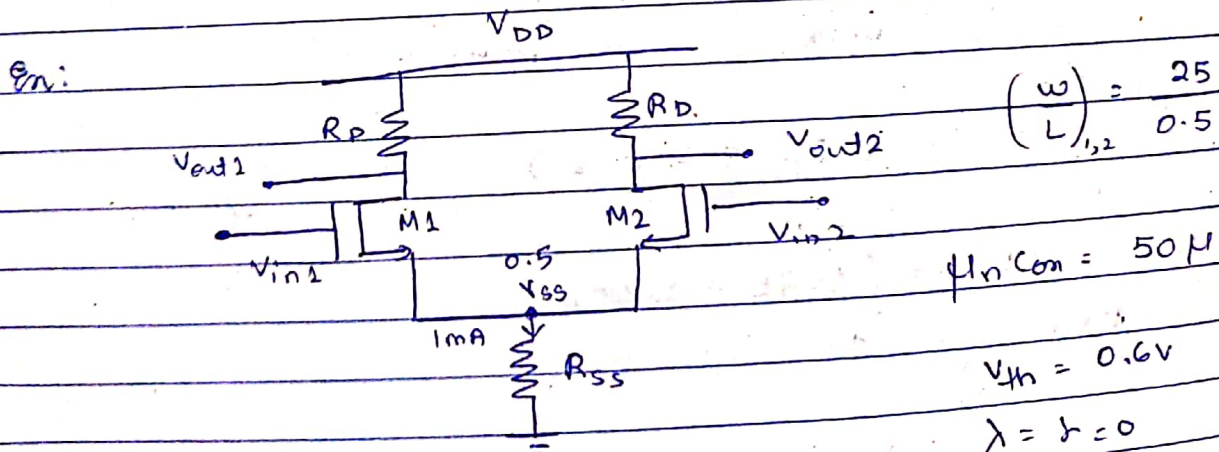
$$\begin{aligned}
 \text{max o/p swing} &= 2(2.5 - 0.8) \\
 &= 3.38V //
 \end{aligned}$$



@ what is the req. input cm voltage for which R_{ss} sustains 0.5V

$$\rightarrow R_{ss} = \frac{0.5}{I_m} = \frac{V_s}{I_{ss}} = 500 \Omega$$

Common mode voltage

$$V_{GS} = ?$$

$$I_d = \frac{1}{2} K_n' \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$0.5 \text{ mA} = \frac{1}{2} \times 50 \mu\text{A/V}^2 \times 50 (V_{GS1} - 0.6)^2$$

$$\boxed{V_{GS1} = 1.23 \text{ V}}$$

$$\begin{aligned} V_{in, cm} &= V_{GS1} + V_{SS} \\ &= 1.23 + 0.5 \\ &= 0.73 \text{ V} \end{aligned}$$


(b) calc. R_d for diff. gain of 5.

$$A_d = \frac{+g_m(R_d)}{2} + \frac{g_m R_d}{2}$$

$$\begin{aligned} &= g_m R_d \\ &= \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} \end{aligned}$$

$$5 = \sqrt{\frac{2 \times 0.5 \text{ mA}}{50 \mu\text{A/V}^2 \times 50}} ; R_D$$

$$\boxed{R_D = 3.16 \text{ k}\Omega}$$

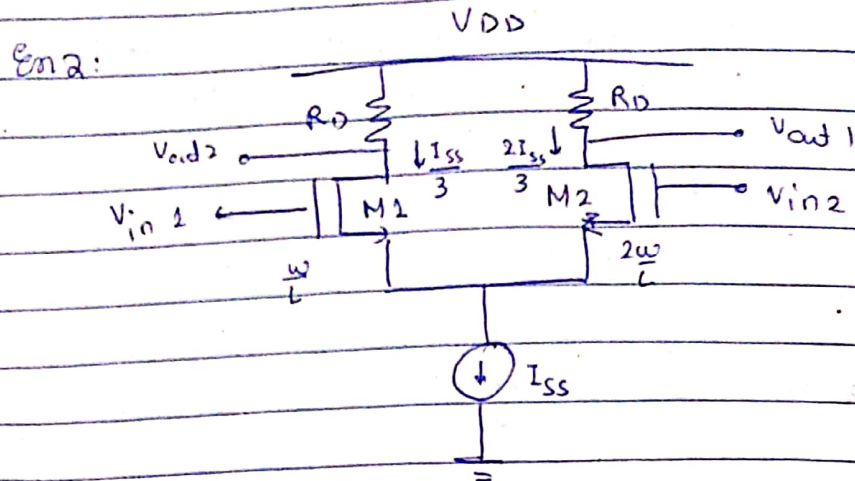

If $V_{in1} = V_{in2}$ find small signal gain

$$|A_V| = \frac{4}{3} g_{m1} R_D$$

→

$$g_{m1} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{w}{L}}} \rightarrow I_{SS}/3$$

$$g_{m2} = \sqrt{\frac{2 \cdot I_{D2}}{\mu_n C_{ox} \frac{w}{L}}}$$

$$g_{m1} = \sqrt{\frac{2 I_{D1}}{3} \mu_n C_{ox} \left(\frac{w}{L}\right)}$$


$$g_{m2} = \sqrt{\frac{2 \left(\frac{2I_{SS}}{3}\right) \mu_n C_{ox} \left(\frac{2w}{L}\right)}$$

$$g_{m2} = 2g_{m1}$$



consider, $V_{in1} \neq 0$ make $V_{in2} = 0$

$$V_{out2} = V_{DD} - (V_{in1} + V_{SS})$$

$$= 3 -$$

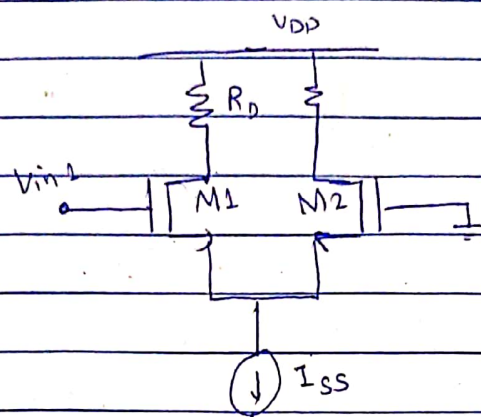

for small signal model -

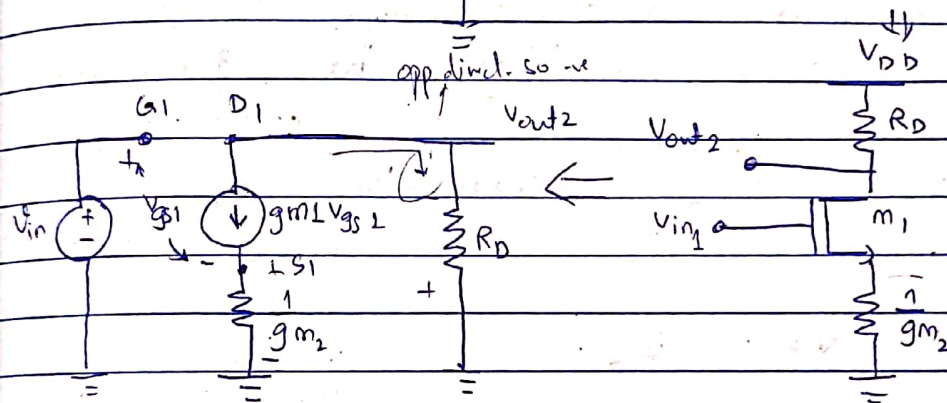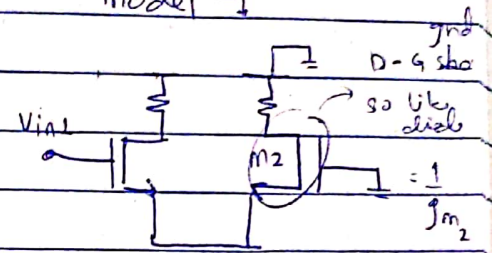

$$V_{gs1} = ?$$

$$V_S + V_{gs1} - V_{in1} = 0$$

$$g_{m1} V_{gs1} \times \frac{1}{g_{m2}} + V_{gs1} - V_{in1} = 0$$

$$V_{gs1} \left(\frac{g_{m1}}{g_{m2}} + 1 \right) = V_{in1}$$


$$V_{gs1} = \frac{V_{in1}}{1 + \frac{g_{m1}}{g_{m2}}}$$

$$V_{out2} = -g_{m1} V_{gs1} R_D$$

$$= -g_{m1} \left(\frac{V_{in1}}{1 + \frac{g_{m1}}{g_{m2}}} \right) R_D$$

$$\frac{V_{out2}}{V_{in1}} = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$


(b) Take V_{out1}
Let $V_{in2} = 0$

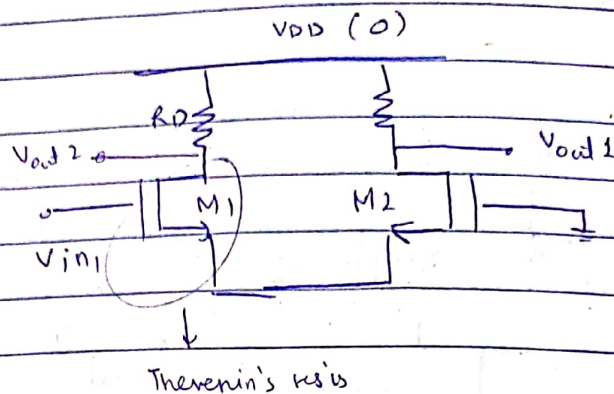


Thevenin's testis (small signal analysis, $P_1 - \text{gnd}$
 $V_{in1} \rightarrow \text{gnd} \therefore$ we want to find R_T
(inactive d_1)

$$R_T = \frac{1}{g_m} \quad (\text{Everything is } 0 \text{ except } m_1)$$

$$V_{th} = V_{in2}$$

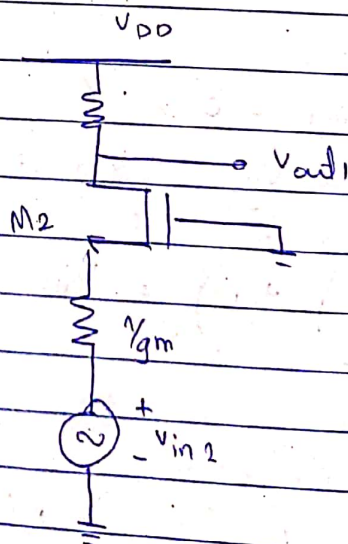

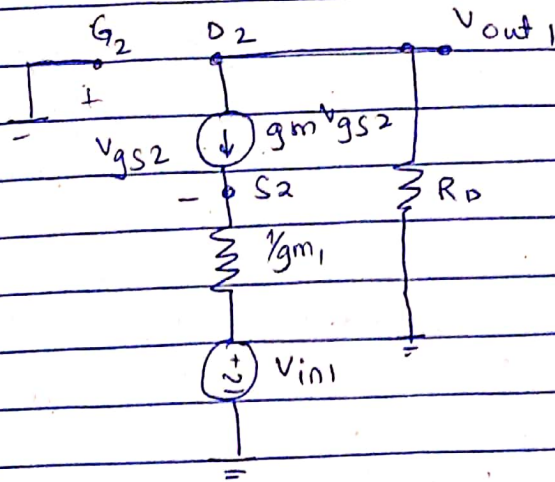

$$+V_{in1} + g_{m2} V_{gs2} \times \frac{1}{g_{m2}} + V_{gs2} = 0$$

$$V_{gs2} = \frac{-V_{in1}}{1 + \frac{g_{m2}}{g_{m1}}}$$

$$V_{out1} = -R_D g_{m2} V_{gs2}$$

$$= -R_D g_{m2} \left(\frac{-V_{in1}}{1 + \frac{g_{m2}}{g_{m1}}} \right)$$

$\frac{V_{out1}}{V_{in1}} = \frac{R_D}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$
--

$$\therefore \frac{V_{out1}}{V_{in1}} = \frac{V_{out2}}{V_{in2}}$$

$$= \frac{2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$\frac{1}{g_{m1}} + \frac{1}{g_{m2}}$$

$$11y \quad V_{out1} - V_{out2} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

phase change.

$$A_d = \frac{V_{out1}}{V_{in1}}$$

$$= \frac{V_{out1} - V_{out2}}{V_{in1}}$$

$$A_d = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}}$$

$$= \frac{V_{out1}}{V_{in1} - V_{in2}} - \frac{V_{out2}}{V_{in1} - V_{in2}}$$

$$1/A_d = \frac{V_{in1} - V_{in2}}{V_{out1} - V_{out2}}$$

$$= \frac{V_{in1}}{V_{out1} - V_{out2}} - \frac{V_{in2}}{V_{out1} - V_{out2}}$$

$$= \frac{\frac{1}{2R_D}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} + \frac{\frac{1}{2R_D}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$= \frac{1}{\frac{2R_D}{g_{m1} + g_{m2}}} + \frac{1}{\frac{2R_D}{g_{m1} + g_{m2}}}$$



* (not back)
Done using
superposition
in gmp

$$= \frac{2g_{m1}g_{m2}}{2R_D(g_{m1} + g_{m2})}$$

$$= \frac{R_D (g_{m1} + g_{m2})}{g_{m1} g_{m2}}$$

$$= \frac{R_D g_{m1} + R_D g_{m2}}{g_{m2} g_{m1}}$$

CM Range = ?

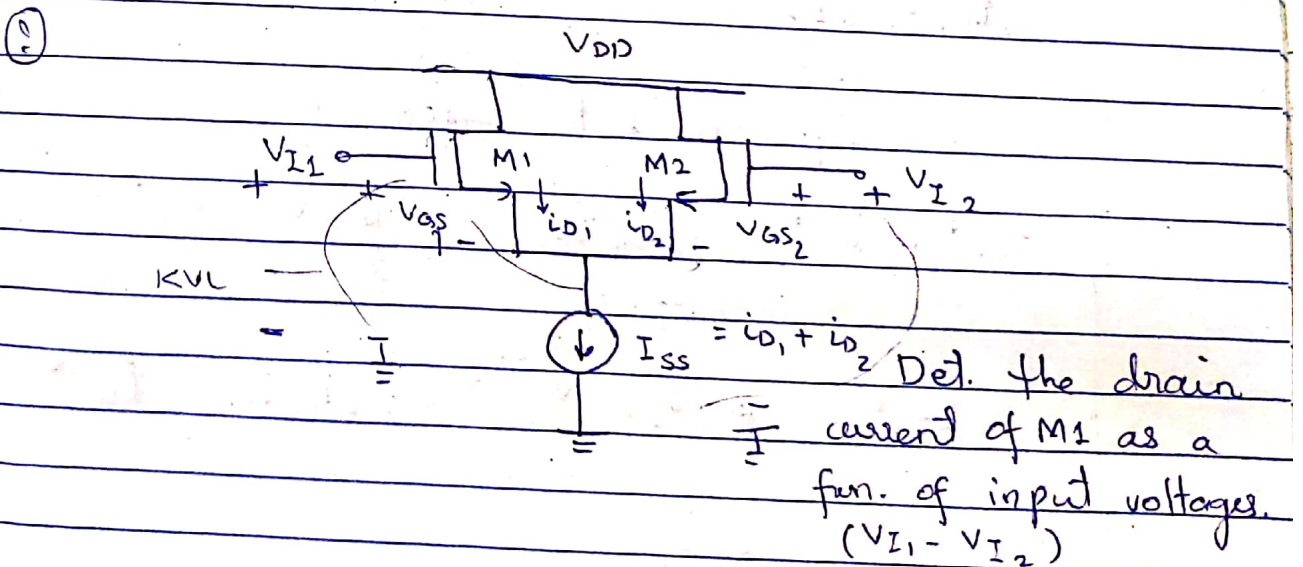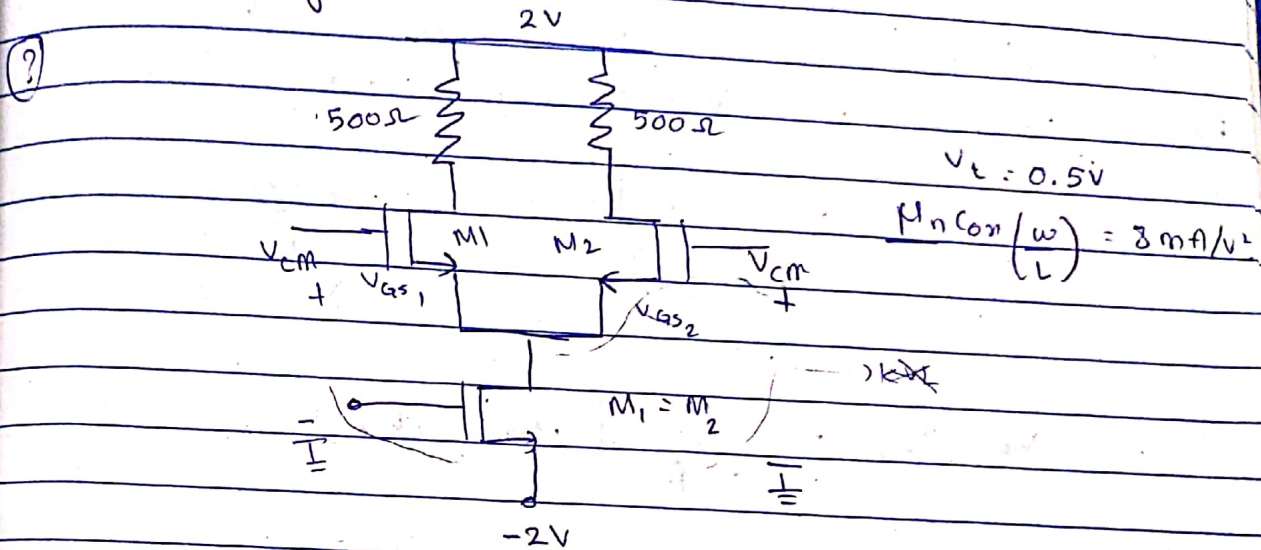

KVL for $M1$ & $M2$

$$V_{I2} - V_{GS2} + V_{GS1} - V_{I1} = 0$$

$$V_{GS1} - V_{GS2} = V_{I1} - V_{I2}$$

M_1 & M_2 - sat.

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$V_{GS} = \sqrt{\frac{2 i_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{th}$$

$$V_{I1} - V_{I2} = \sqrt{\frac{2 i_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{th} - \left[\sqrt{\frac{2 i_{D2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} + V_{th} \right]$$

matched

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$$

$$= \sqrt{\frac{2 i_{D1}}{\beta}} - \sqrt{\frac{2 i_{D2}}{\beta}}$$

$$V_{I1} - V_{I2} = \sqrt{\frac{2}{\beta}} (\sqrt{i_{D1}} - \sqrt{i_{D2}})$$

$$\sqrt{i_{D1}} - \sqrt{i_{D2}} = V_{I1} - V_{I2} \sqrt{\frac{\beta}{2}}$$

Sq. on both sides

$$i_{D1} + i_{D2} - 2\sqrt{i_{D1} i_{D2}} = \frac{\beta}{2} (V_{I1} - V_{I2})^2$$

$$i_{D1} = \frac{\beta}{2} (V_{I1} - V_{I2})^2 + 2\sqrt{i_{D1} i_{D2}} - i_{D2}$$

$$I_{SS} - 2\sqrt{i_{D1} i_{D2}} = \frac{\beta}{2} (V_{I1} - V_{I2})^2$$

$$I_{SS} - \frac{\beta}{2} (V_{I1} - V_{I2})^2 = 2\sqrt{i_{D1} i_{D2}}$$

SOBS

$$I_{SS}^2 + \left[\frac{\beta}{2} (V_{I1}^2 + V_{I2}^2 - 2V_{I1}V_{I2}) \right]^2 = 4i_{D1}i_{D2}$$

$$I_{SS}^2 + \left[\frac{\beta V_{I1}^2}{2} + \frac{\beta V_{I2}^2}{2} - \frac{\beta 2V_{I1}V_{I2}}{2} \right]^2 = 4i_{D1}i_{D2}$$

$$I_{SS}^2 + \frac{\beta^2 V_{I1}^4}{4} + \frac{\beta^2 V_{I2}^4}{4} + \frac{\beta^2 4 V_{I1}^2 V_{I2}^2}{4} - 2\beta^2 V_{I1}^2 V_{I2}^2$$

$$I_{SS}^2 + \frac{\beta^2 (V_{I1} - V_{I2})^4}{4} - 2 \times I_{SS} \times \frac{\beta}{2} (V_{I1} - V_{I2})^2 = 4i_{D1}i_{D2}$$

$$= 4i_{D1}(I_{SS} - i_{D1})$$

$$i_{D1}^2 = -\frac{I_{SS}^2}{4} + \frac{I_{SS} \beta (V_{I1} - V_{I2})^2}{4} - \frac{\beta^2 (V_{I1} - V_{I2})^4}{16} + i_{D1} I_{SS}$$

⑥ what does derivation give to i_{D1} when $V_{I1} \gg V_{I2}$


$$V_{I1} \gg V_{I2}$$

$$I_{SS} = i_{D1} + i_{D2}$$

$$I_{SS} \approx i_{D1}$$

$$\therefore i_{D1} = \sqrt{\frac{I_{SS}^2}{4} + \frac{I_{SS} \beta (V_{I1} - V_{I2})^2}{4} - \frac{\beta^2 (V_{I1} - V_{I2})^4}{16}}$$

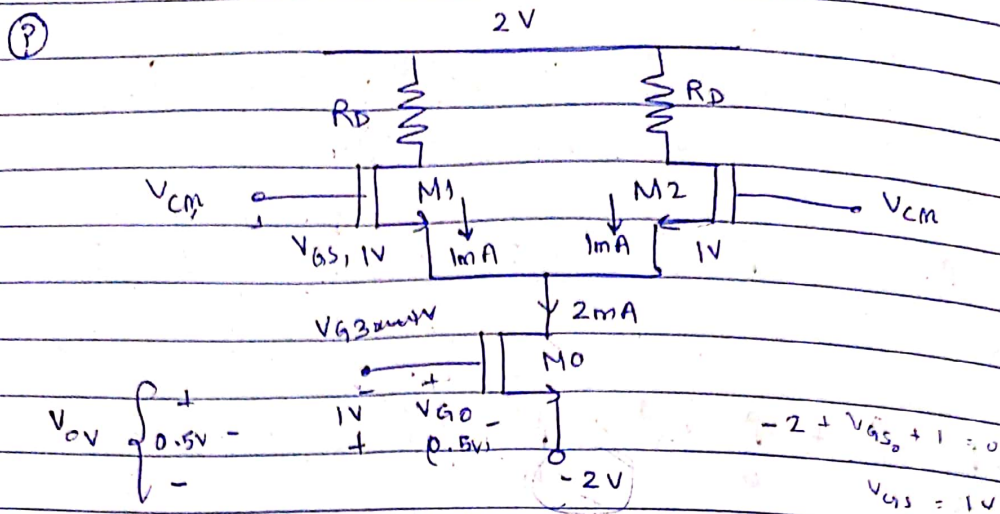Here although -ve 1V is supplied cal. V_{GS} it is +ve



M1 & M2 identical

$$R_D = 500 \Omega$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right) = 8 \text{ mA/V}^2$$

$$V_T = 0.5 \text{ V}$$

Calc. V_{CM} range

min max

→ cal. V_{GS_0} using KVL

$$-2 + V_{GS_0} + 1 = 0$$

$$V_{GS_0} = 1 \text{ V}$$

V_{CM} min, KVL →

$$(V_{GS_0} - V_T)^2$$

$$V_{CM} + 1 \text{ mA}$$

$$i_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS_0} - V_T)^2$$

$$1 \text{ mA} = \frac{1}{2} \times 8 \text{ m} (1 - 0.5)^2$$

$$= 4 \text{ m} (0.5)^2$$

$$= 1 \text{ mA} //$$

$$-2 - 1 + 1 + 1 - V_{cm} = 0$$

$$-1V + V_{cm, min} + \cancel{1} - 1V + 2V + 1 = 0$$

$$+0.5 + 1$$

$$-2 - 1 + 1 + 1 - V_{cm, min} = 0$$

$$V_{cm, min} = 1V - 0.5$$

$V_{cm, max}$:-

$$+2 - 2 - 1 + 1 + 1 + V_{cm, max} + 500(1m) = 0$$

$$V_{cm, max} = 1.5V$$

$$+2 - 2 + 0.5 + 1 - V_{cm, max} + 500(1m) = 0$$

$$V_{cm, max} = -2V$$

Mam's

$$-2 + V_{ov, 3} + V_{GS1} - V_{cm, min} = 0$$

$$V_{cm, min} = V_{GS1} + V_{ov, 3} - 2$$

For max

$$-2 + V_{DS1} + V_{GS1} - V_{cm, max}$$

$$-2 + V_{DS1} + V_{ov, 1} + I_{D1} R_D - V_{DD} = 0$$


$$V_{D1} = V_{DD} - I_{D1} R_D - V_{ov, 1} + 2$$

$$(V_{GS1} - V_T)$$

28.02.19

Unit II

MOS Characteristics

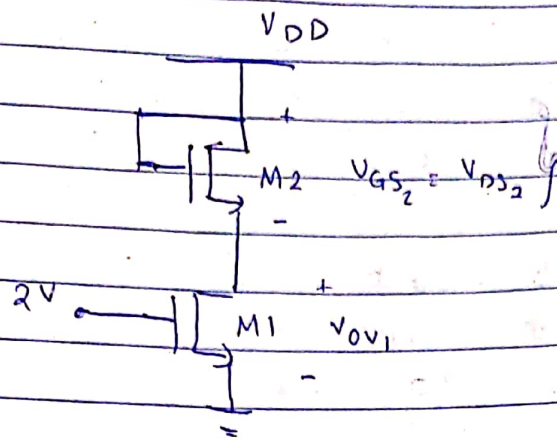

$$V_{DD_{min}} = V_{GS2} + V_{ov1} + 1$$

Assume $\frac{W}{L} = 1$

$$i_{D1} = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS1} - V_t)^2$$

$$i_{D1} = 0.5 \text{ mA}$$

$$i_{D1} = i_{D2}$$

$$0.5 \text{ m} = \frac{1}{2} (1 \text{ mA}) (V_{GS2} - 1)^2$$



$$V_{ov2} = 1 \text{ V}$$

$$V_{GS2} - 1 = 1 \text{ V}$$

$$V_{GS2} = 2 \text{ V}$$

$$V_{DD_{min}} = 2 + 1 = 3 \text{ V}_{//}$$

5 pack

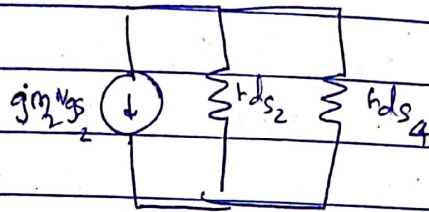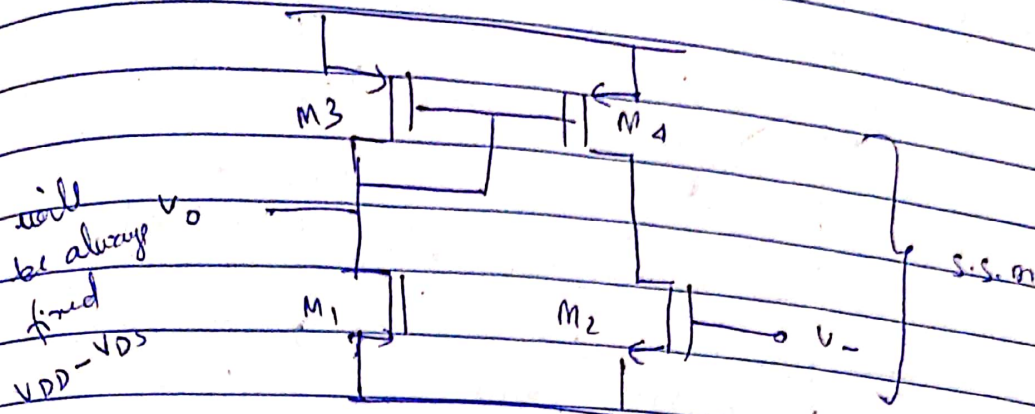



If m_2 & m_4 are matched


$$A_d = -g_m(r_{ds2} || r_{ds4})$$

Current Mirror.


$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$
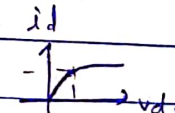
$$I_D \propto \frac{W}{L} \quad \text{— linear relation}$$

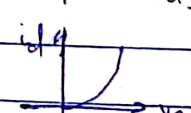
$$I_D \propto (V_{GS} - V_t)^2 \quad \text{— parabolic}$$

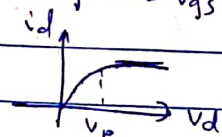
$$I_D \propto (1 + \lambda V_{DS}) \quad \text{— small signal}$$


MOS characteristic

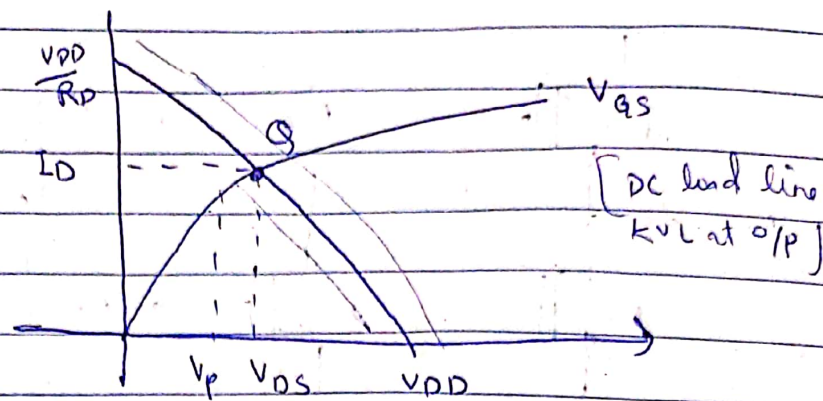

$$V_{DS} = V_{DD} - I_D R_D$$


load line

$$V_{DS} \Big|_{I_D=0} = V_{DD}$$


$$I_D \Big|_{V_{DS}=0} = \frac{V_{DD}}{R_D}$$

'Q' should always be to the right of V_p point.
So we have to design OpAmp in such way

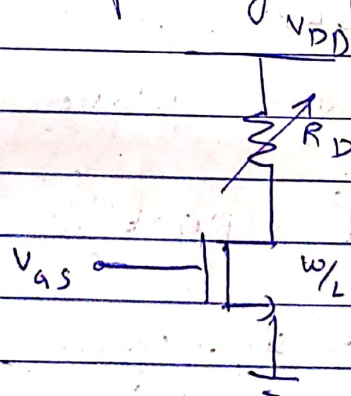If R_D value is different, we get different operating points



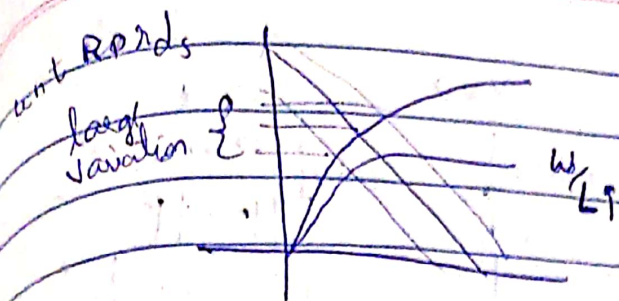So the intersection of load line & characteristic curve depends on your device & R_D value.



So to build current mirror, we need a flatter curve.
So if we used a large channel device, curve is flatter.


Current Mirror

17.03.19

- Biasing the MOS using current
- Used as active load; facilitates high gain.

Why?

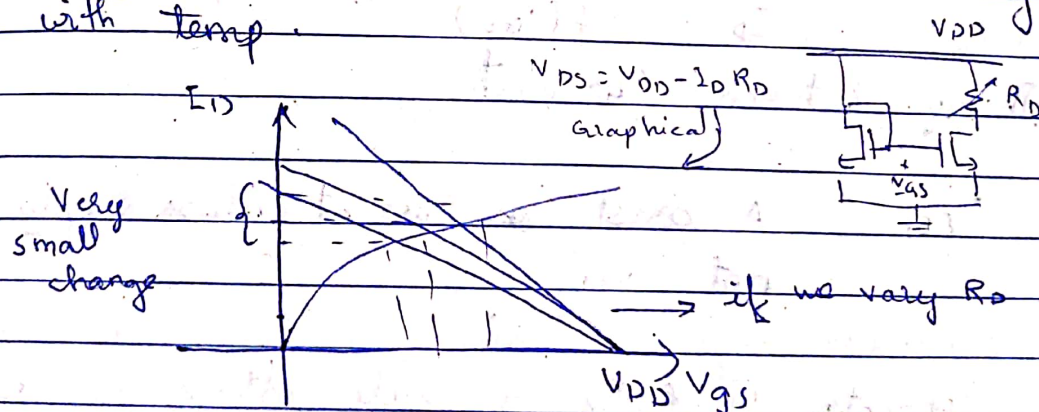
→ It gives a const. current, doesn't vary with temp.



- Using this mirror we can generate a current source - active load.

amp
CS source

active load

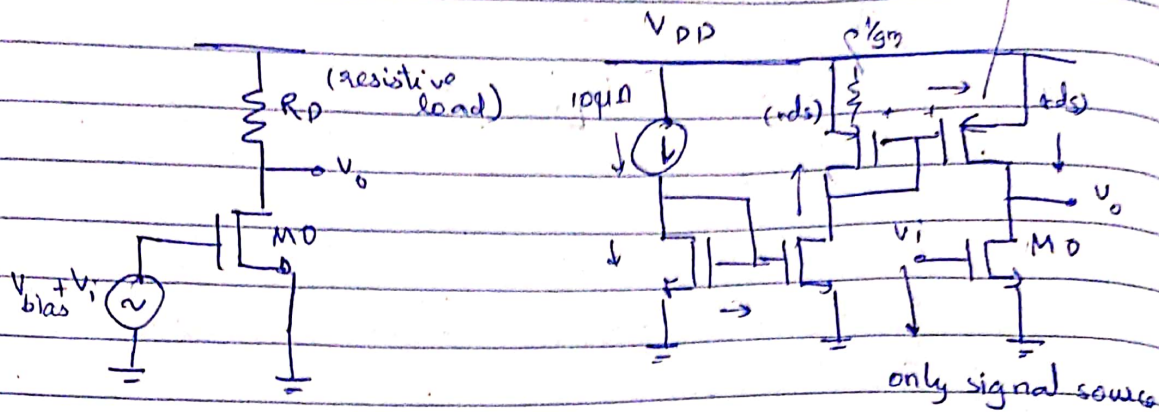

voltage biasing

$$A = -g_m R_D$$

current biasing

$$\frac{v_o}{v_i} = -g_m (r_{ds1} || r_{ds2})$$

$$\frac{v_o}{v_i} = -g_m r_{ds} \uparrow$$

I_D is made function of V_{GS}

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$


const

$$I_D = f(V_{GS})$$

Theory between Current

I_{REF} : A const current whose supply is not varying.

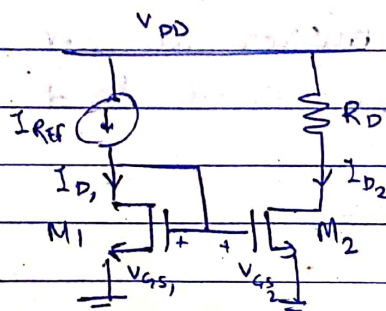Connect M_1 & M_2 gate voltages are same
Connect a R_D , then we have I_{D1} & I_{D2}



$$I_{D1} = f(V_{GS1})$$

$$V_{GS2} = V_{GS1}$$

$$I_{D2} = f(V_{GS2})$$

$$= f(V_{GS1})$$

$$V_{GS1} = f^{-1}(I_{D1})$$

$$I_{D2} = f[f^{-1}(I_{D1})]$$

$$I_{D2} = I_{D1} \rightarrow \text{* } \mu_n \text{ con} \left(\frac{W}{L} \right) \text{ \& } V_T \text{ of } M_1 \text{ \& } M_2$$

Mismatching - the current, are same

* If ~~parameters~~ $\left(\frac{W}{L} \right)$ are not ~~same~~ same.

$$\frac{I_{D2}}{I_{D1}} = \frac{\frac{1}{2} K_n' \left(\frac{W}{L} \right)_2 (V_{GS} - V_T)^2}{\frac{1}{2} K_n' \left(\frac{W}{L} \right)_1 (V_{GS} - V_T)^2}$$


$$\frac{I_{D2}}{I_{D1}} = \frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1}$$

$$I_{D2} = K I_{D1} ; K > 1 \rightarrow \text{current amplification}$$


$K < 1 \rightarrow \text{attenuation}$

~~Difficulties encountered~~

We can mirror into multiple branches

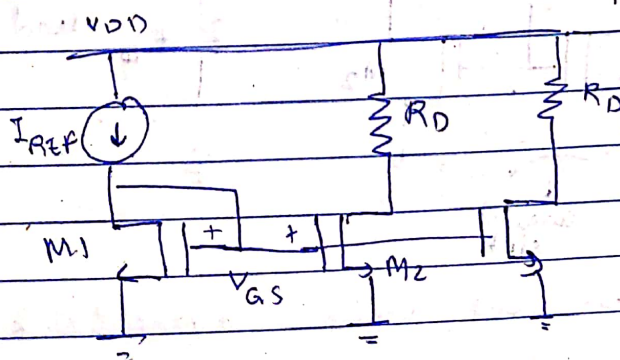


But instead we with only 1 R_D .

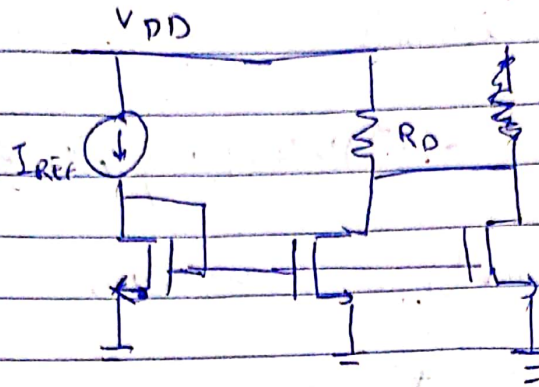


Here there will be minute change in current as there is only 1 R_D , but it is neglected.

Sink

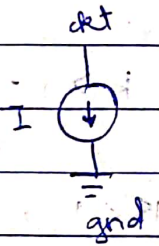

Source

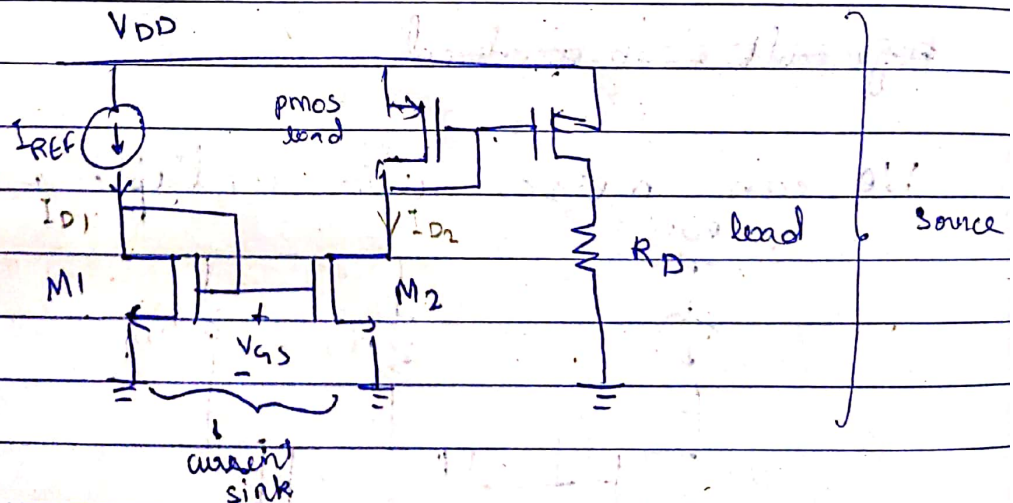

In this ckt which is source & sink

$$\frac{\partial \phi}{\partial x} = \frac{\partial \phi}{\partial y} + \frac{\partial \phi}{\partial z}$$

Merits of current source

- 1) o/p swing of current source.
(be high)
- 2) output resistance = ∞


MOS is a non linear device

$$I_{D2} = K I_{D1} \rightarrow \text{linear eqn.}$$

$$I_{D2} = \frac{(w/L)_2}{(w/L)_1} \times I_{D1}$$


So either you have a high o/p resistance a small swing a vice versa. So based on these combination we have 4 types of current mirror.

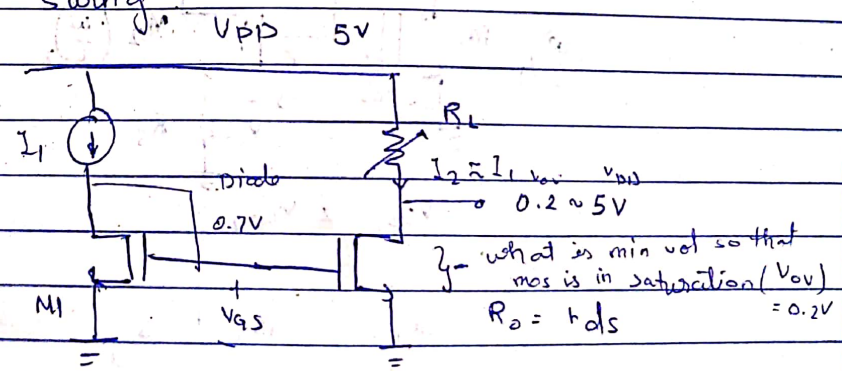We have to understand what is o/p resistance & o/p swing.



So o/p voltage can be 0.2 to 5V

O/p Resistance

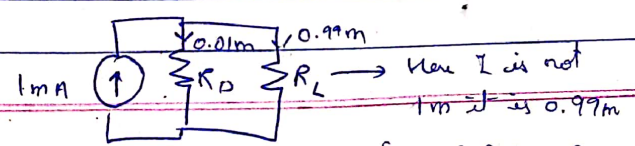

$$\text{So } R_o \gg R_L$$

Here I is not 1mA it is 0.99mA
So we assume a small current in R_o .


The higher the output resistance, better the opAmp.

So the different topologies are -

- Widlar
- Cascode
- Wilson (Regulated cascode)

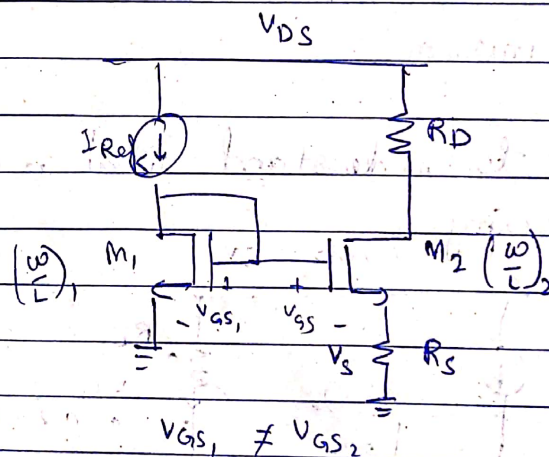1) Widlar current Mirror

In the source branch of 2nd MOS, a resistor is brought





$$V_{GS1} = V_{GS2} + V_S$$

So currents are not same
To make them equal, we adjust $\frac{W_2}{L_2}$
of 2nd transistor.

$\frac{\partial \phi}{\partial u} \cdot \frac{\partial u}{\partial x} = \frac{\partial \phi}{\partial x}$ $1 + \beta$

(i) O/P resistance

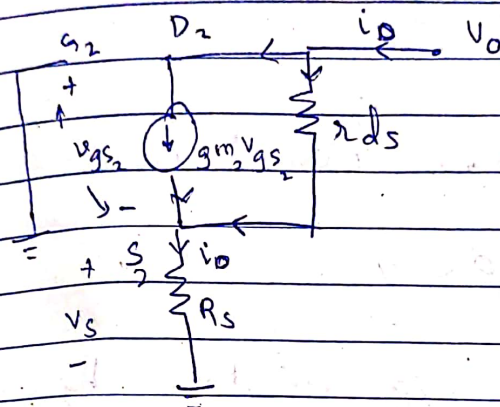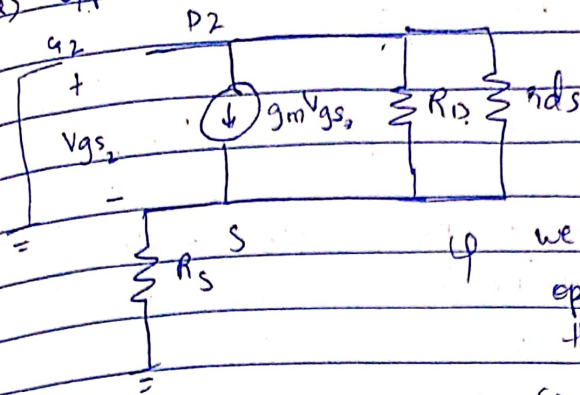

$$R_o \uparrow = r_{ds2} + R_S + g_{m2} R_S r_{ds2}$$


$V_{o \text{ swing}} \downarrow$

test source $V_o = R_o$

test current i_o

$$V_{gs2} = -V_S$$

$$= -i_o \times R_S$$

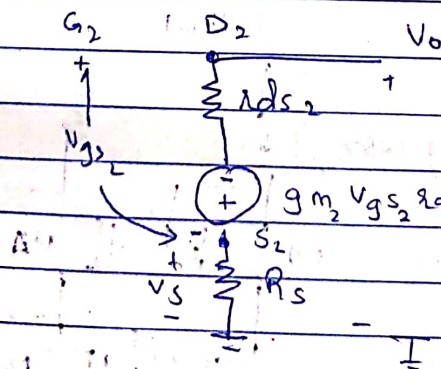

KVL eq. $\frac{V_o}{I_o}$

$$V_o = r_{ds2} I_o + g_{m2} V_{gs2} r_{ds2} + R_S I_o$$

if R_S was not connected

$$R_o = r_{ds2}$$

$$\frac{V_o}{I_o} = r_{ds2} + R_S + g_{m2} r_{ds2} R_S$$

B.C.M $R_{o1} = r_{ds}$
 $V_{oswing} \uparrow$


$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

En taking $R_S = 1K$
 $r_{ds2} = 100K$

$$R_o = r_{ds2} + R_S + g_m r_{ds2} R_S$$

$$= 100K + 1K + (1m) 100K \times 1K$$


$$= 201K //$$

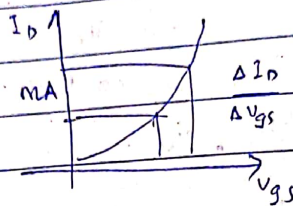

But with basic current mirror


$$R_o = 100K //$$

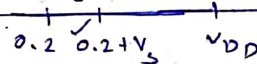So we increase o/p resistance by adding R_S . But with a very high R_S , the swing decreases



II Cascode


So instead of R_S we use active element

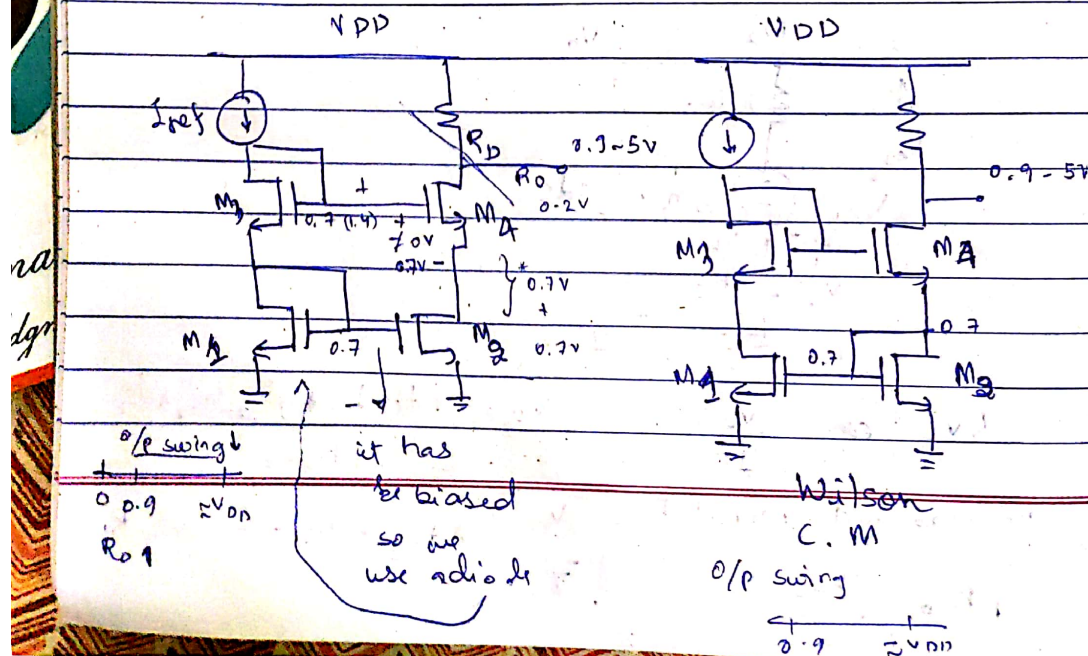

* 0.7 as there has to be some gate to source voltage

H.W Calc. R_o & V_{oswing} ?

Equivalent ckt

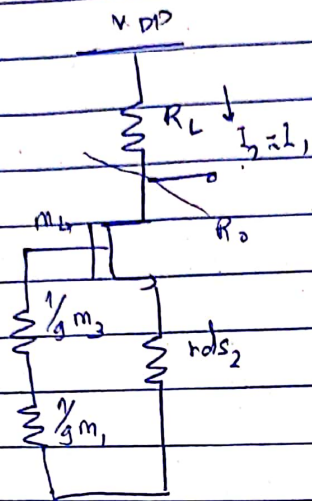


$$R_o = r_{ds4} + r_{ds2} + g_{m4} r_{ds4} r_{ds2}$$

o/p R_o is 1

$$R_o = (2 + \mu) r_{ds}$$

$\downarrow$
 $g_m r_{ds4}$

Equivalent ckt

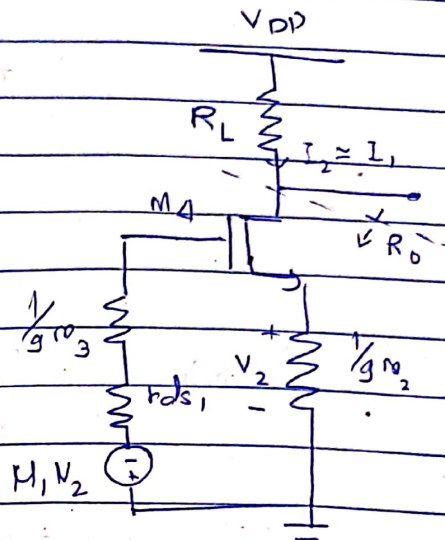

$$R_o = (2 + \mu) r_{ds}$$


Problems

i) For the above Widlar current mirror

$$V_{DD} = 5V; V_{GS1} = 0.7V \quad V_{GS2} = 0.4V \quad I_1 = I_2 = 10\mu A$$

$$V_t = 0.2V$$

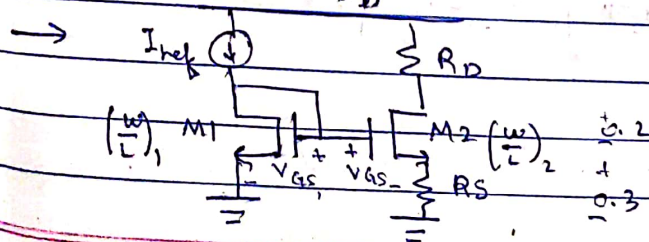Determine the value of R_s & Range of R_L & o/p voltage swing. Assume $V_{DS, min} = 0.2V$



$$V_{GS1} = V_{GS2} + I_2 R_S$$

$$R_S = \frac{V_{GS1} - V_{GS2}}{I_2}$$

$$= \frac{0.7 - 0.4}{10 \mu}$$

$$= 30 \text{ K}\Omega //$$

$$V_{O \min} = 0.3 + 0.2$$

$$= 0.5 \text{ V} //$$

$$\text{If } V_O = 0.5 \text{ V}$$

$$R_L = \frac{V_{DD} - V_O}{I_2}$$

$$= \frac{5 - 0.5}{10 \mu}$$

$$= 450 \text{ K}\Omega //$$


So R_L varies from 0 to 450 K Ω //

$$\text{if } V_O = 5 \text{ V}$$

$$R_L = 0 \Omega$$

$$\text{o/p voltage swing} = 0.5 - 5 \text{ V} //$$

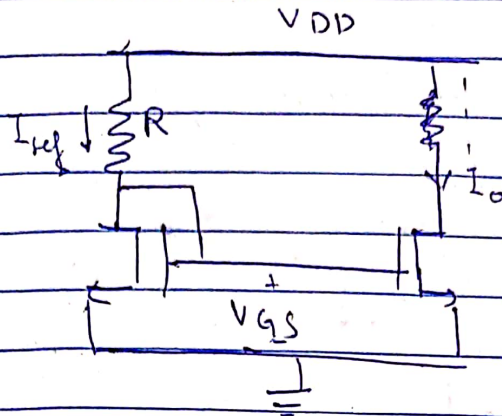2] Design the current mirror when $I_0 = 100 \mu A$,
 $V_{DD} = 3V$, $\lambda = 0$, $V_t = 1V$, $k'_n \frac{W}{L} = 90 \text{ mA/V}^2$



$$I_0 = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (V_{GS} - 1)^2$$

$$200 \mu A = 90 \text{ mA/V}^2 (V_{GS} - 1)^2$$

$$\sqrt{2.2 \text{ m}} = V_{GS} - 1$$

$$V_{GS1} = 10.047 \text{ V} = V_{GS2}$$

$$R = \frac{V_{DD} - V_{GS1}}{I_{ref}}$$


$$= \frac{3 - 0.047}{100 \mu A}$$

$$= 20 \text{ k}\Omega //$$

3] In a basic current mirror, let $V_{DD} = 5V$,
 $V_t = 1V$, $k_n' = 20 \mu A/V^2$, $R = 1K\Omega$,

(a) Find out $(\frac{w}{L})_1$ to create $I_{ref} = 1mA$

(b) $(\frac{w}{L})_2$ for $I_o = 7mA$

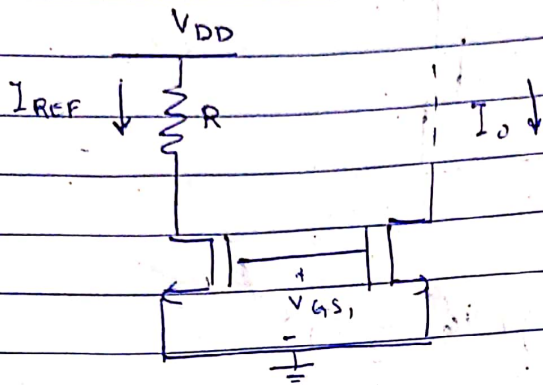

$$I_{REF} = \frac{V_{DD} - V_{DS1}}{R}$$

$$1mA = \frac{V_{DD} - V_{GS1}}{R}$$

$$V_{GS1} = \frac{V_{DD} - V_{GS1}}{R} (1 \times 10^{-3} \times 1 \times 10^3)$$

$$V_{GS1} = 5 - 1 = 4V$$

$$I_{ref} = \frac{1}{2} k_n' \left(\frac{w}{L}\right)_1 (V_{GS1} - V_t)^2$$

$$= \frac{1}{2} \times 20 \times 10^{-6} \left(\frac{w}{L}\right)_1 (4 - 1)^2$$

$$\left(\frac{w}{L}\right)_1 = 11.11$$


$$\frac{I_o}{I_{ref}} = \frac{(w/L)_2}{(w/L)_1}$$

$$\Rightarrow (w/L)_2 = \frac{I_o}{I_{ref}} \times (w/L)_1$$

$$= 11.11 \times 7$$

$$\left(\frac{w}{L}\right)_2 = 77.77 //$$

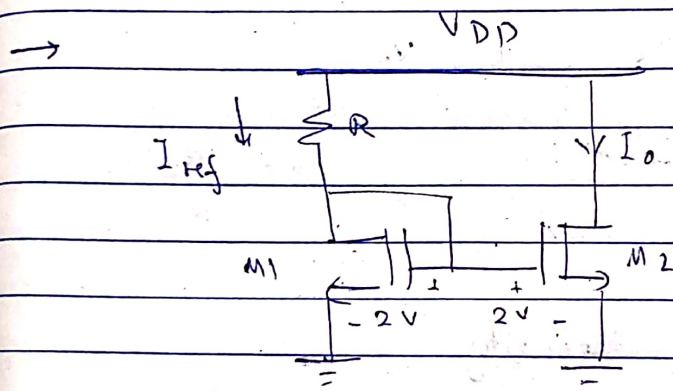4) Calculate the mirror ratio for MOS current mirror
for $V_{GS} = 2V$, $V_{DS} = 10V$, $\lambda = 0.02V^{-1}$
mirror ratio = ?



$$I_2 = \frac{1}{2} K_n' \left(\frac{w}{L}\right) (V_{GS} + \lambda V_{DS})^2$$

$$I_1 = \frac{1}{2} K_n' \left(\frac{w}{L}\right) (V_{GS} - V_t)^2$$

$$\frac{I_2}{I_1} = \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

$$\lambda = 0.02 V^{-1}, \quad 1 + 0.02(10)$$

$$V_{DS1} = \text{ratio} = 1.15 //$$

5] Calculate the output current I_o for the MOS current mirror if $V_{DD} = 10V$, $\mu_n C_{ox} \left(\frac{W}{L}\right) (1 + \lambda V_{DS}) = 250 \mu A/V^2$


$$V_t = 1V, \lambda = 0.0133 V^{-1}, I_{ref} = (150 \mu A),$$

$$V_{DS1} = 10V, \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$$

→

Linear Applications

1.4.19

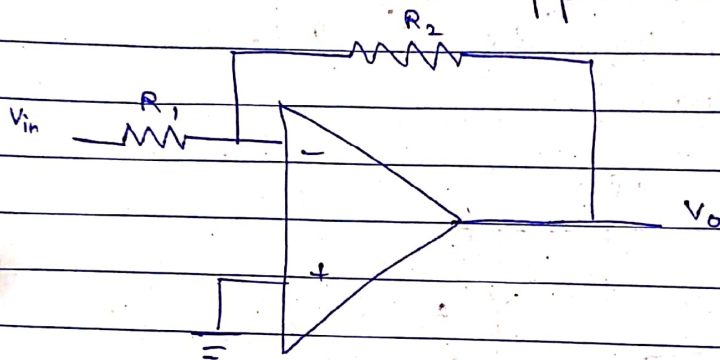

$$V_o = -\frac{R_2}{R_1} V_i$$


Condition for linearity

- Dominant negative feedback

$$V_d = \frac{V_o}{A}$$

$$V_+ = 0$$

- Output must be unsaturated

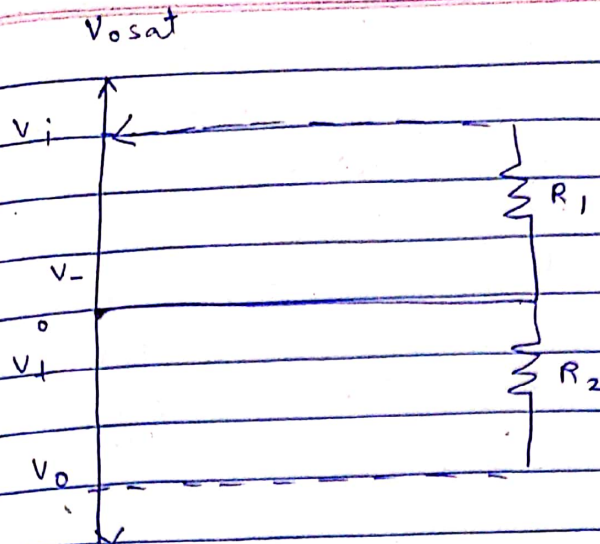


$$V_- = \frac{V_i R_2 + V_o R_1}{R_1 + R_2}$$

Noise:

$$V_{N\uparrow} = (V_d + V_{N\uparrow}) \Rightarrow V_d + AV_{N\downarrow} \Rightarrow (V_d + V_{N\uparrow} + AV_{N\downarrow})$$


Non-inverting amplifier

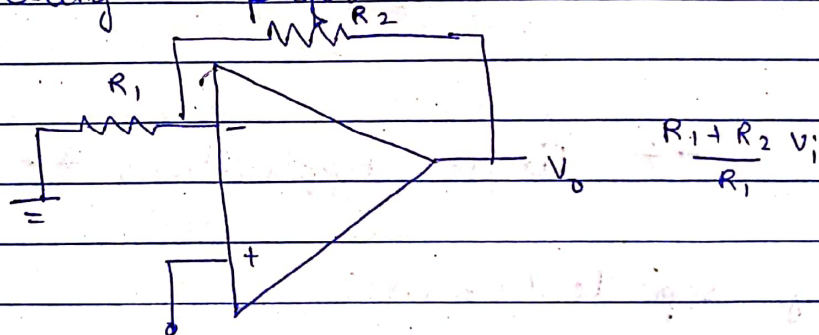

$$V_- = \frac{R_1}{R_1 + R_2} V_o$$

$$V_o = AV_d$$


3) Regenerative feedback

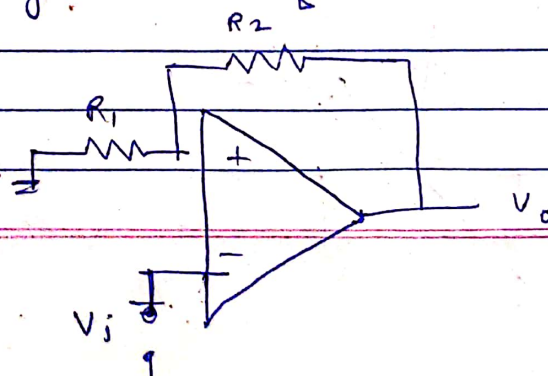

$$V_- = V_i; \quad V_+ = \frac{R_1}{R_1 + R_2} V_o$$

$$V_d = V_+ (\uparrow) : -V_- > + \frac{V_{o,sat}}{A}$$
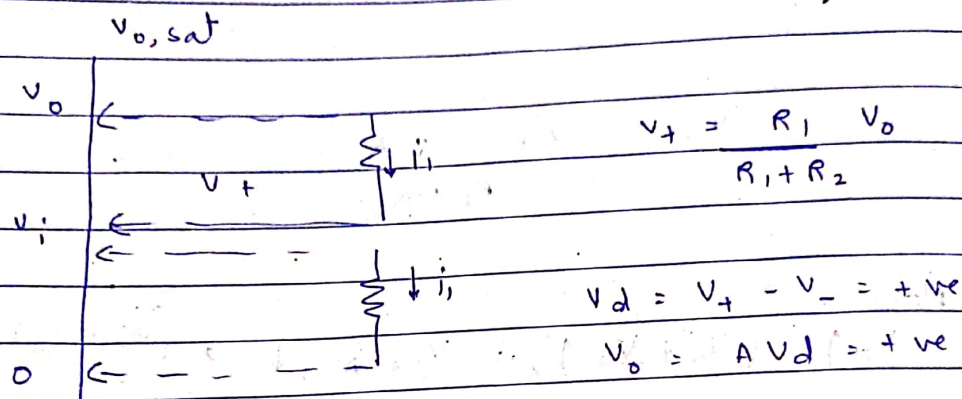
$$V_d = V_+ (\downarrow) : -V_- < - \frac{V_{o,sat}}{A}$$





$$V_N \uparrow = (V_d + V_N \uparrow) \Rightarrow (V_o + A V_N) \uparrow \Rightarrow (V_d + V_N \uparrow + A V_N)$$

** Linear Applications **

1.4.19

→ why separate (b.a.n.l)?

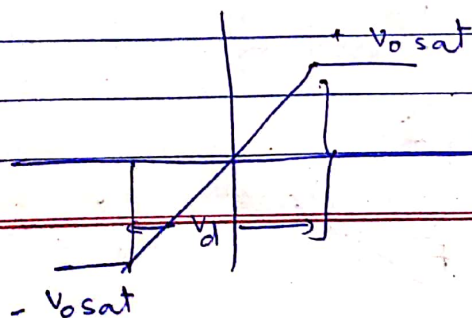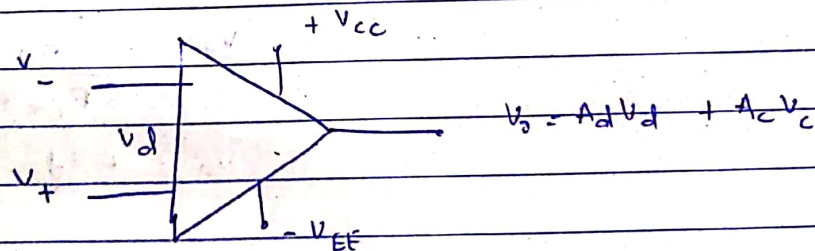

feedback $\begin{cases} +ve & \text{non linear} \\ -ve & \rightarrow \text{linear} \end{cases}$

unsaturated o/p -


$$V_d \approx 0$$

$$V_d = V_+ - V_-$$

$\Rightarrow$ virtual ground.

for any app to be in linear, the -ve feedback must be dominant.

Inverting Amplifier

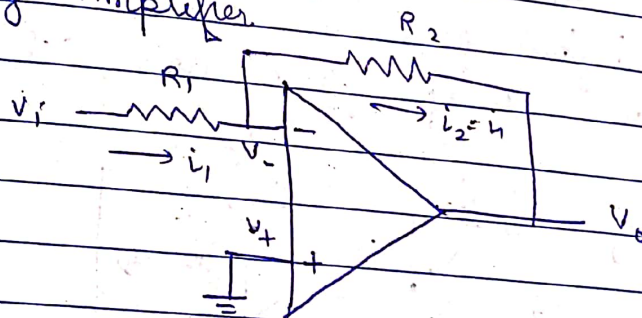

Difference $V_d = V_+ - V_-$

because o/p is unsaturated

$$i_1 = i_2$$

$$\frac{V_i - 0}{R_1} = \frac{0 - V_o}{R_2}$$

Gain of
inverting
amplifier


$$A_f = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

If $V_o = - \frac{R_2}{R_1}$ is this stable?

There are some factors which change the voltages & make change in o/p vol.


So we try to understand if there is a noise* which will alter the signal

* Noise is bidirectional signal

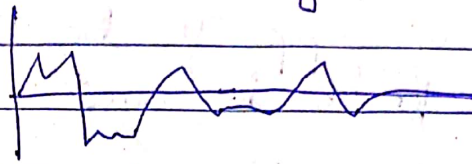

can affect at all frequencies but prominent at higher freq.

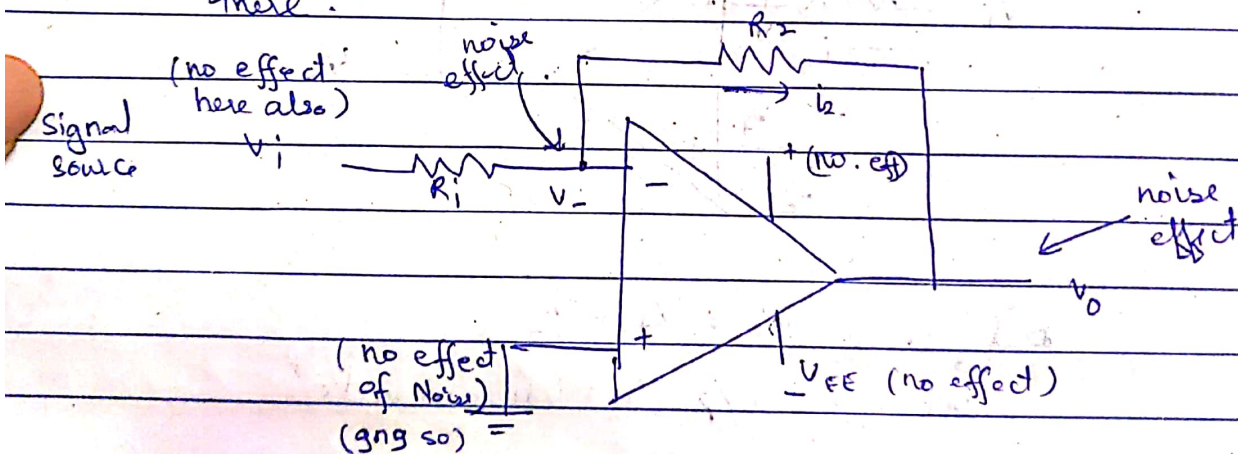We can't escape from noise, it is always there.



So remaining are V_o

We have few ohm of o/p impedance
So we have noise at inverting terminal & V_o

So using Superposition

$$V_i = 0$$

$$V_o = \frac{V_o R_1}{R_1 + R_2}$$

$$V_o = 0 \quad V_- = \frac{V_i R_2}{R_1 + R_2}$$

So Resultant

$$V_- = \frac{V_i R_2 + V_o R_1}{R_1 + R_2} //$$

V_N - Noise voltage.

Suppose $\Delta V_N \uparrow$ i.e. $V_- + V_N \uparrow$ (Noise getting added)

$$V_d = V_+ - V_-$$

$$= 0 - (V_- + V_N \uparrow)$$

$$V_d = -V_- - V_N \uparrow$$

$V_- \uparrow$ & $V_d \uparrow$ but in -ve direction.

$$\therefore \Delta V_N \uparrow \Rightarrow V_- \uparrow \Rightarrow |V_d| \uparrow \Rightarrow |V_o| \uparrow \Rightarrow V_- \downarrow$$


$$\downarrow V_- = \left(\frac{R_1}{R_1 + R_2} \right) V_i - \left(\frac{R_2}{R_1 + R_2} \right) \frac{V_o}{\%} \quad V_o(\text{noise})$$

considering the sign.

The feedback is countering on noise, its makes the output stable.


V_o is stable as linear mode signal.

2. Non inverting Amplifier

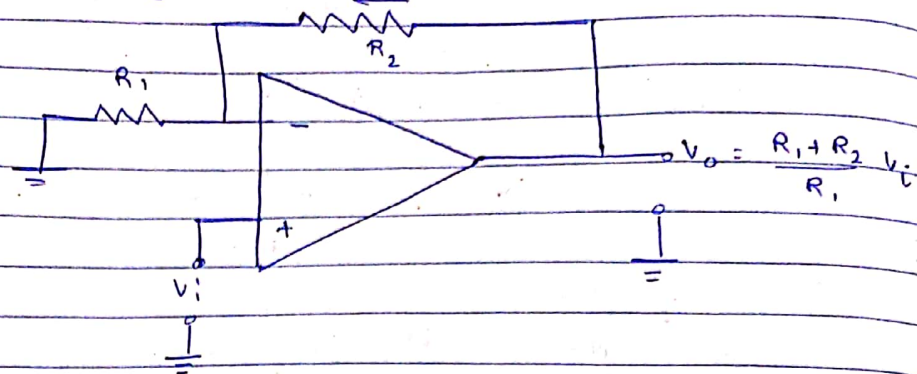

$$V_+ = V_i \quad \text{virtual short}$$

$$V_- = V_i$$

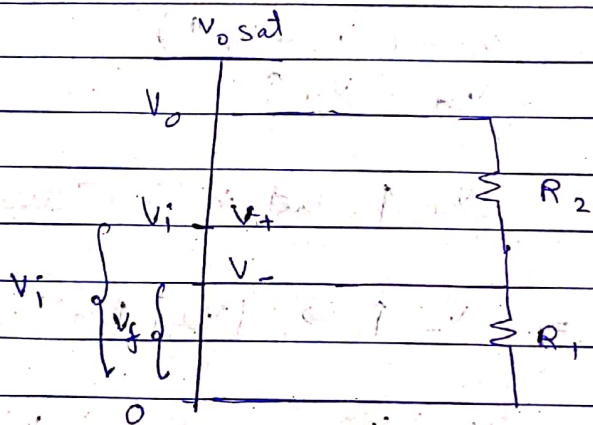

$$V_N \uparrow \Rightarrow V_d + V_N \uparrow \Rightarrow V_o + A V_N \downarrow \Rightarrow V_d + V_N \uparrow + A \beta V_N \downarrow$$

$$\Delta V_N \uparrow \Rightarrow V_- \uparrow \Rightarrow |V_d| \downarrow = |V_o| \downarrow = V_- \downarrow$$

$$V_d = V_+ - V_-$$

$$= V_+ - (V_- + \Delta V_N \uparrow)$$

$$V_d = V_+ - V_- - \Delta V_N \uparrow$$


$$|V_d| \text{ decreases} \Rightarrow |V_o| \downarrow \Rightarrow V_- \text{ decreases}$$

$$V_d = \frac{V_o}{A}$$

$$V_- = \frac{R_1}{R_1 + R_2} V_o$$

V_o - stable output.

Regenerative Feedback

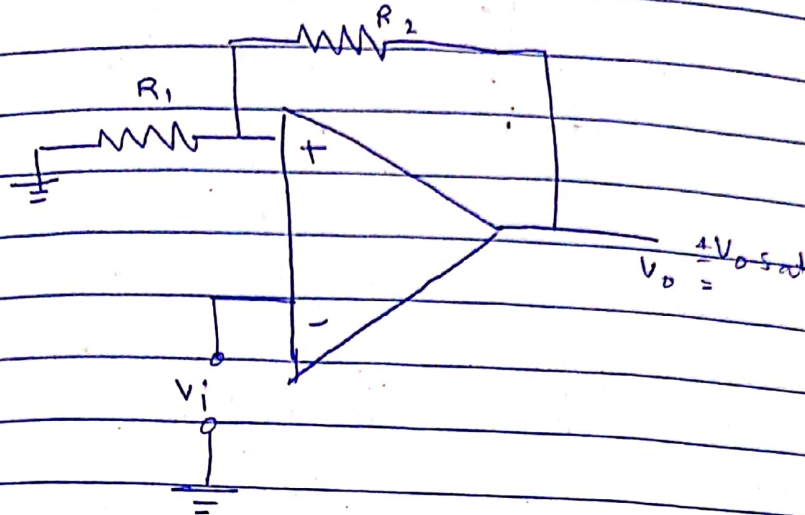

$$V_- = V_i \quad \text{but} \quad V_+ \neq V_i$$

$$V_+ = \frac{R_1}{R_1 + R_2} \cdot V_o$$

$$V_N \uparrow \Rightarrow (V_d + V_N \uparrow) \Rightarrow (V_o + A V_N \uparrow) \Rightarrow (V_d + V_N \uparrow + A \beta V_N \uparrow)$$

V_o = unstable as linear mode signal

$$V_o = \pm V_{o \text{ sat}} = \text{stable under saturation cond.}$$

$$\Delta V_N \uparrow \Rightarrow V_+ \uparrow \Rightarrow |V_d| \uparrow \Rightarrow |V_o| \uparrow \Rightarrow V_+ \uparrow \uparrow$$


$$V_d = V_+ - V_-$$

$$= V_+ + \Delta V_N \uparrow - V_i$$

fixed

= increases till it hits saturation.

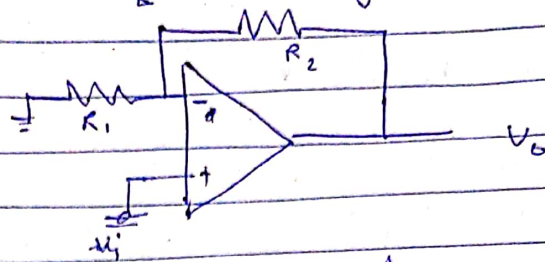
1) Draw ckt of inverting amp, & write gain.




$$A_f = -\frac{R_2}{R_1}$$

5) Draw an Op-amp circuit

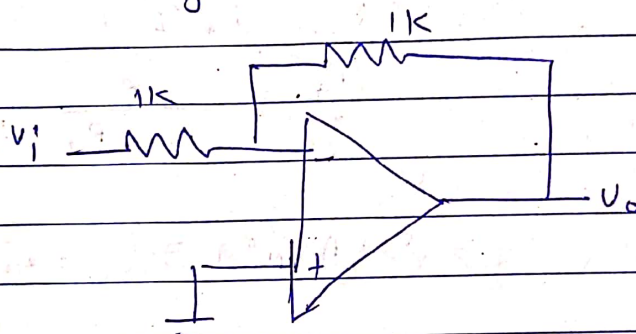
(i) Analog inverter - a inverting amp with gain 1




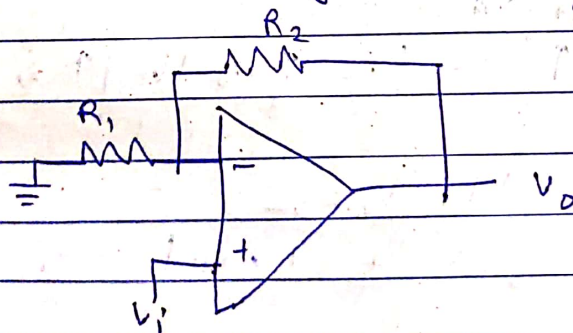(ii) Scale changer - non-inverting with some K gain



(iii) Buffer

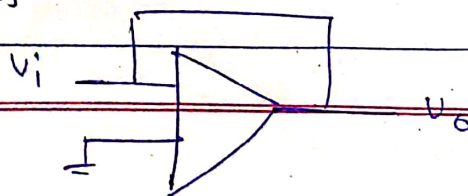

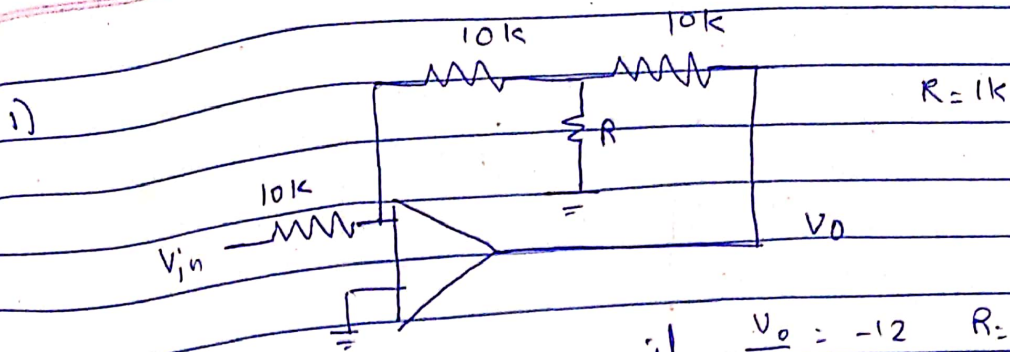

if $\frac{V_o}{V_{in}} = -12$ $R = ?$

$$A = -12$$

$$\frac{V_o}{V_{in}} = -12$$


$$V_{in}$$

$$V_o = -12 V_{in}$$

$$V_o = - \frac{R_2}{R_1} V_i$$

$$-12 V_i = - \frac{R_2}{10k} V_i$$

$$R_2 = 120k$$

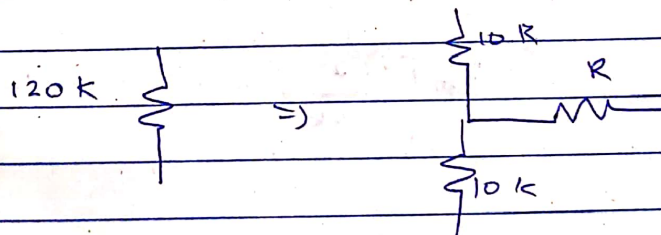

$$120k = 10k + \frac{10k R}{R + 10k}$$

$$110k = \frac{10k \cdot R}{R + 10k}$$

$$110R + 1100 = 10R$$

$$1100 = 100R$$

$$120k = 10k + (10k \parallel R)$$

$$110 = \frac{10R}{10+R}$$

$$\Rightarrow 1100 + 110R = 10R$$

$$1100 = 100R$$


$$-12V \times \frac{10k}{10k} = -\frac{R_2}{10k} \cdot V_{e3} 12V$$

$$5k + R$$

$$R_2 = 120k$$

Ans

$$i_1 = i_2$$

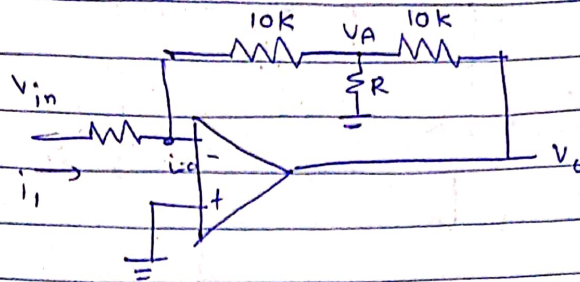

$$i_1 = i_2$$

$$\frac{V_{in}}{10k} = -\frac{V_A}{10k}$$

$$V_{in} = -V_A$$

$$i_2 = i_3 + i_4$$

$$\frac{V_A}{10k} = \frac{V_A}{R} + \frac{V_A - V_o}{10k}$$

$$\frac{V_{in}}{10k} = -\frac{V_{in}}{R} + \left(-\frac{V_{in} - V_o}{10k} \right)$$

$$V_{in} \left[\frac{2}{10k} + \frac{1}{R} \right] = -\frac{V_o}{10k}$$

$$V_d = V_+ - V_- = 1 - 0 = 1$$


Given $\frac{V_o}{V_{in}} = -12$

$$-\frac{V_o}{V_{in}} = 10k \left[\frac{2}{10k} + \frac{1}{R} \right]$$



$$12 = 10 \left[\frac{2}{10k} + \frac{1}{R} \right]$$

$$\boxed{R = 1k}$$

3] . calc. V_2

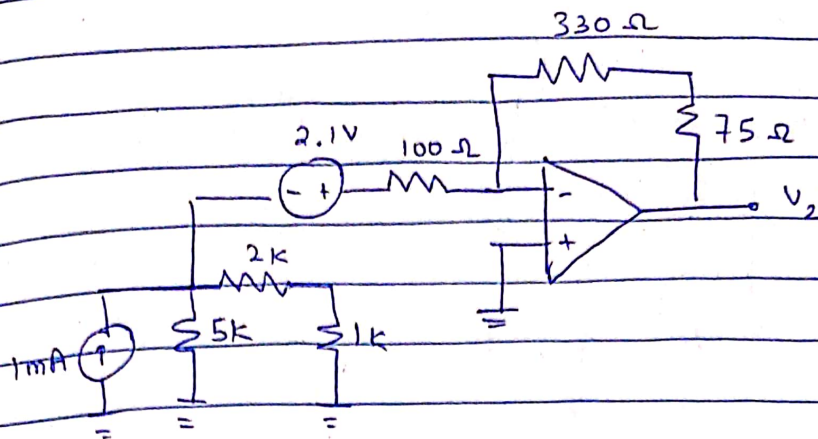



$$V = IR$$

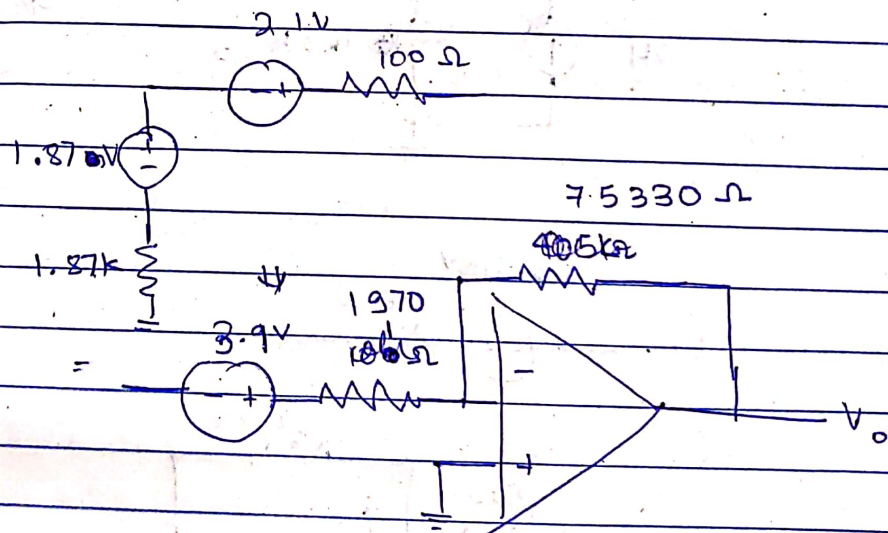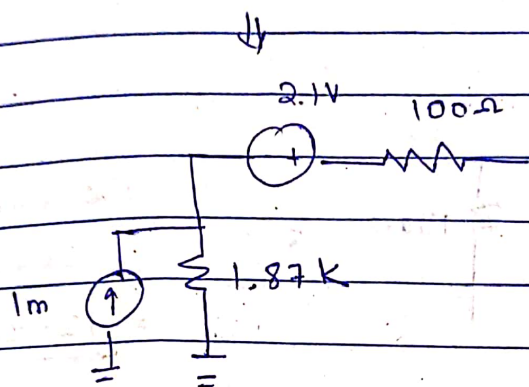


$$\frac{V_0}{3.9} = - \frac{405}{1001} - \frac{75330}{1970}$$

$$V_0 = 8.54V \parallel 149.1V //$$



5]

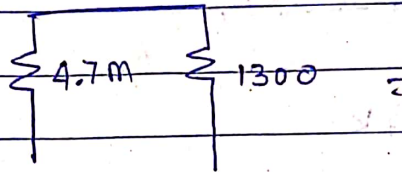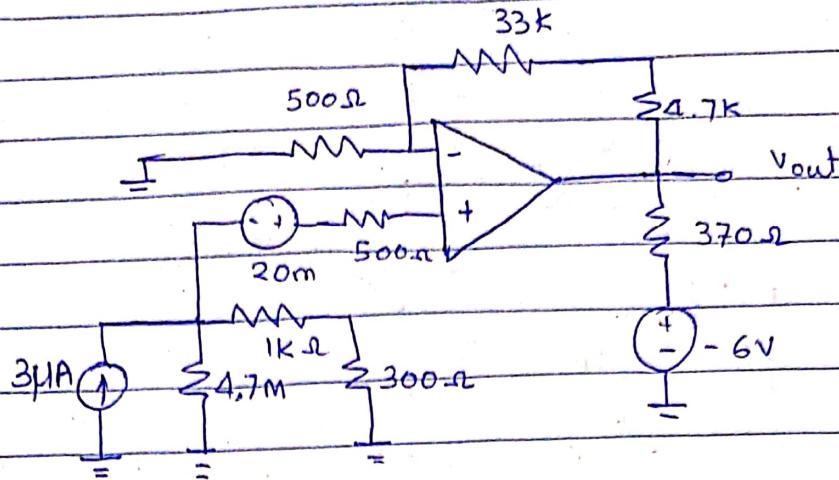
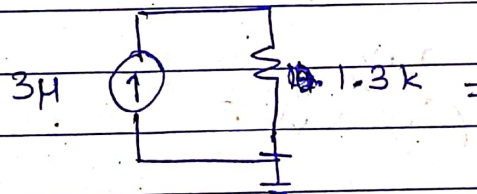
$$\frac{1300 \times 4700000}{1300 + 4700000} = 1299.6\Omega$$


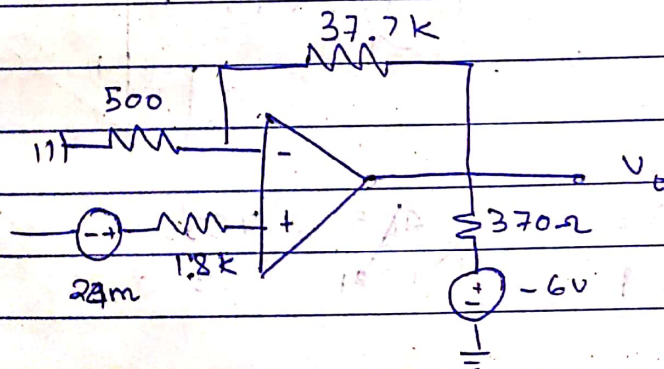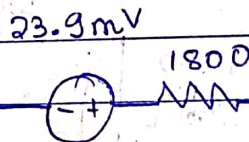
$$3\mu \times 1.3\text{k} = 3.9\text{mV}$$



$$\frac{V_o}{V_{in}} = 1 + \frac{R_2}{R_1}$$

$$\frac{24m}{V_{in}} = 1 + \frac{37.7k}{500}$$


$$\frac{24m}{V_{in}} = 76.4$$

$$V_{in} = 314 \mu V //$$

$$\frac{V_o}{24m} = 76.4$$

$$V_o = 1.826 V$$

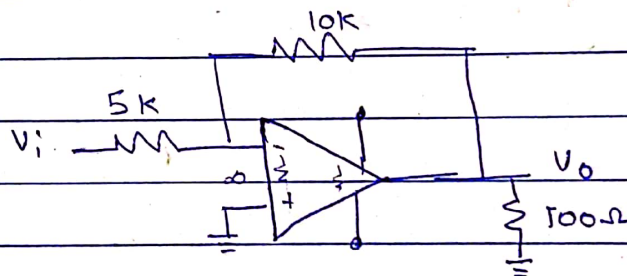HW. An inverting amplifier with load resistor
 $R_L = 100\Omega$, $R_1 = 5k$, $R_2 = 10k\Omega$. $A_v = 50k$, $R_o = 500\Omega$
 $R_i \rightarrow \infty$



- (a) Determine voltage across R_L for an rms input signal of $1.5V$
 (b) Repeat part a, consider ideal opamp.


Ans.

→ $V_i = 1.5V$ (c) $V_o = -2.99V$

$$\frac{V_o}{V_i} = -\frac{10k}{5k}$$

$$V_o = -3V$$

$$V_{RL} =$$

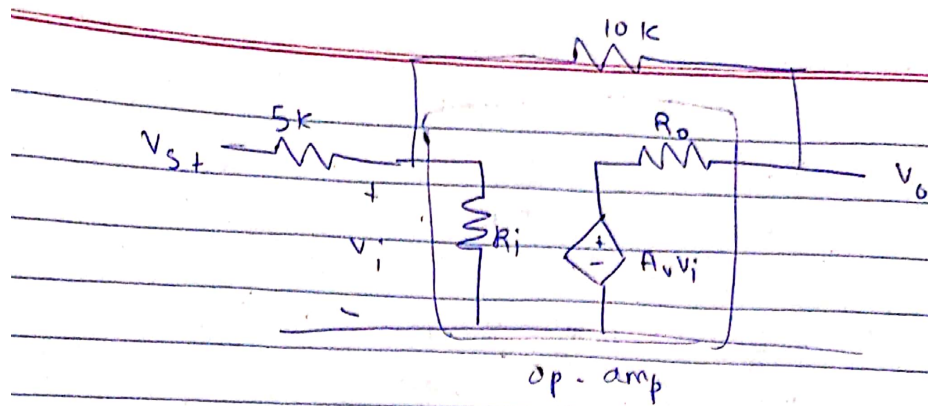


Theremin eqn.

11.10 2 different microphones are used in a recording studio, one for

11.10 A sinusoidal signal is riding on a $2V$ dc offset (in other words avg value of total signal is $2V$). Design a circuit to remove the dc offset and amplify the sinusoidal signal (without phase reversal) by a factor of 100.


5.9.19

Summing Amplifier

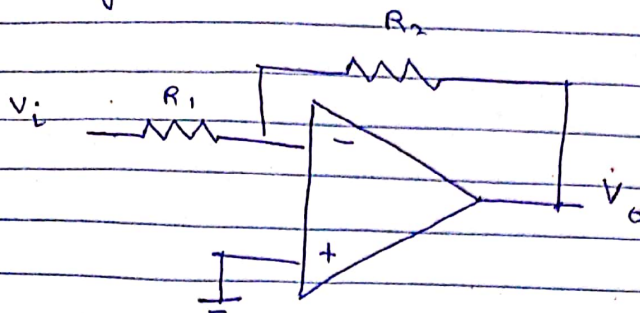

$$A_f = - \frac{R_2}{R_1}$$

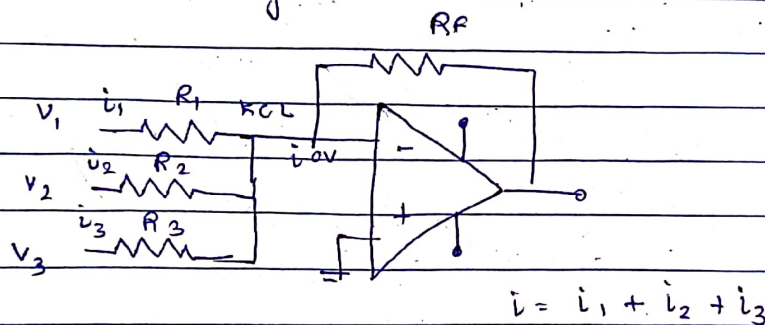Instead of one input, we can combine different input & then put to an amplifier with a gain



$$i = i_1 + i_2 + i_3$$

$$A_f = - \frac{R_f}{R_1 \parallel R_2 \parallel R_3}$$

$$- \frac{V_o}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$



$$-V_o = R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

$$= \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

Taking same resistances,

$$V_o = - [V_1 + V_2 + V_3]$$

Similarly for a non-inverting summer.

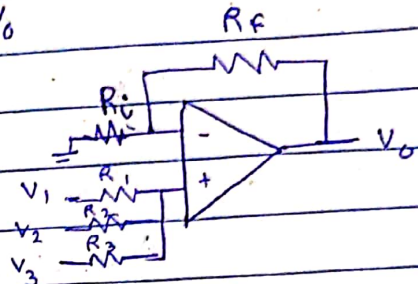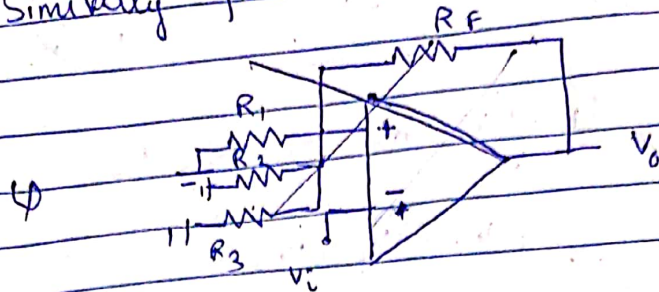


$$\frac{-V_o}{R_F} =$$

$$V_o = \left(1 + \frac{R_F}{R_i}\right) V_i + \left(\frac{R_F}{R_i}\right) V_1 + \left(\frac{R_F}{R_i}\right) V_2 + \left(\frac{R_F}{R_i}\right) V_3$$

$$V_o = 2 [V_1 + V_2 + V_3]$$


Non-inverting summer

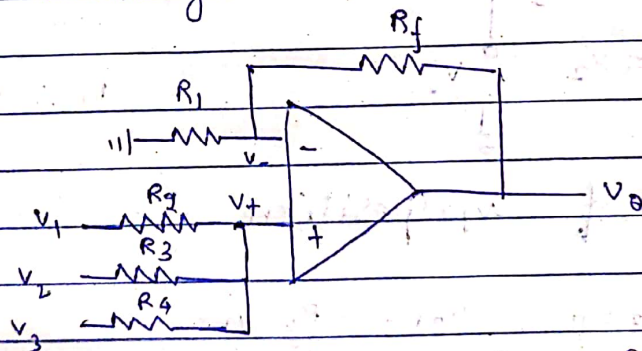

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_+$$

So $V_+ = ?$

Superposition

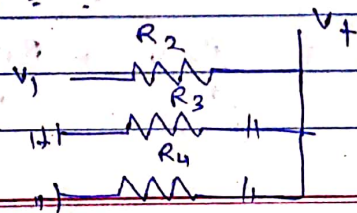

$$V_+ = \frac{R_3 R_4}{R_2 + R_3 R_4} V_1$$

* There will be no drop across R_3 as no current enters opamp.

$$V_+ = \frac{\left(\frac{R_2 R_4}{R_2 + R_4} \right) V_2}{R_3 + \frac{R_2 R_4}{R_2 + R_4}}$$


$$V_+ = \frac{\left(\frac{R_2 R_3}{R_2 + R_3} \right) V_3}{R_4 + \frac{R_2 R_3}{R_2 + R_3}}$$

So add all, assume $R_2 = R_3 = R_4$

$$V_+ = \frac{1}{3} \left(\frac{V_1}{3} + \frac{V_2}{3} + \frac{V_3}{3} \right)$$

$$V_+ = V_1 + V_2 + V_3 //$$

Dual input amplifier

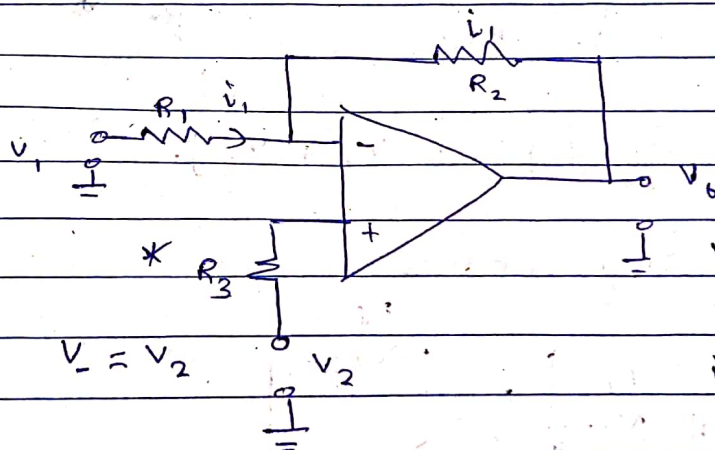

$$V_0 = \frac{-R_2 V_1}{R_1} + \frac{R_1 + R_2}{R_1} V_2$$

$$i_1 = \frac{V_1 - V_2}{R_1}$$

Principle of Superposition

Case 1 : $V_2 = 0$: $V_{01} = -\frac{R_2}{R_1} V_1$

Case 2 : $V_1 = 0$: $V_{02} = \frac{R_1 + R_2}{R_1} V_2$


Case 3 : $V_0 = V_{01} + V_{02} = -\frac{R_2}{R_1} V_1 + \frac{R_1 + R_2}{R_1} V_2$

dy $\frac{d\phi}{dx}$ sn
Whenever we come across more than one i/p
always use superposition



Basic Differential amplifier


Application built using opAmp

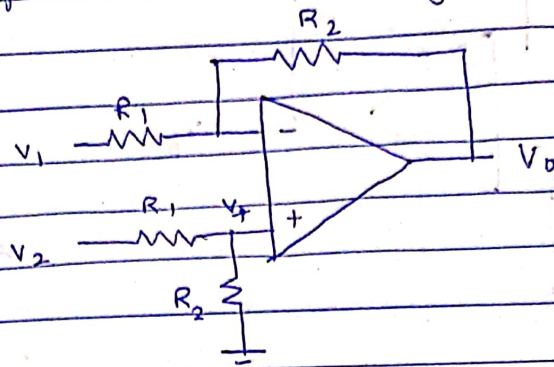

$$\text{when } V_2 = 0; \quad V_o = -\frac{R_2 \cdot V_1}{R_1}$$

$$V_1 = 0 \quad V_o = \left(1 + \frac{R_2}{R_1}\right) V_+$$

How do we find V_+

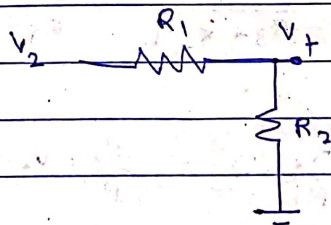

Thevenin's eq.
model


$$V_+ = \frac{R_2 \cdot V_2}{R_1 + R_2}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_o = -\frac{R_2}{R_1} V_1 + \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_2$$

$$V_o = -\frac{R_2}{R_1} V_1 + \frac{R_2}{R_1} V_2$$

Basic Differential Amplifier 2

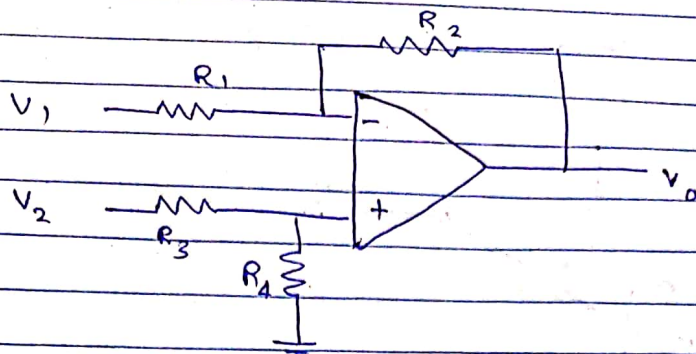

Condition $\frac{R_2}{R_1} = \frac{R_4}{R_3}$

$$\frac{R_1 + R_2}{R_1} = \frac{R_3 + R_4}{R_3}$$

inverting

non inverting

$$V_0 = -\frac{R_2}{R_1} V_1 + \frac{R_4}{R_3 + R_4} \left(\frac{R_1 + R_2}{R_1} \right) V_2$$

$$= -\frac{R_2}{R_1} V_1 + \frac{R_2}{R_1} V_2 = \frac{R_2}{R_1} (V_2 - V_1)$$

OpAmp is a Diff Amp with

High Gain $\{ A_d = 10^4 - 10^5 \}$

low bandwidth


Uncontrollable, unpredictable gain

Diff Amp using OpAmp with


low gain $\{ A_d = \frac{R_2}{R_1} = 5 \sim 50 \}$

High Bandwidth


controllable, predictable gain

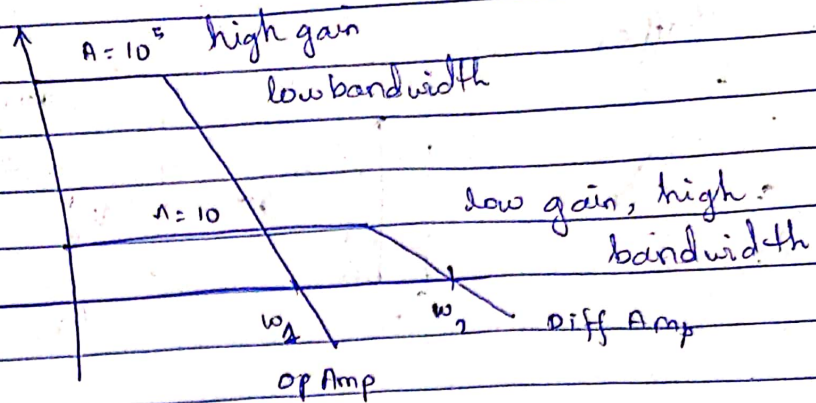

Differential Amplifier 3

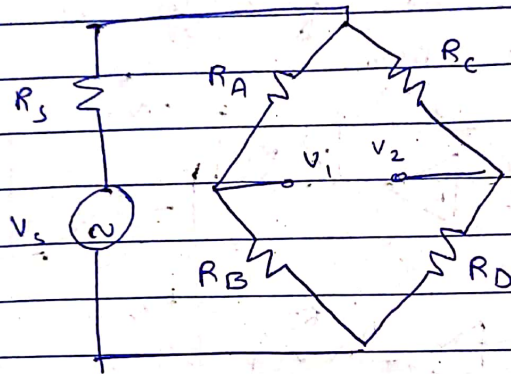

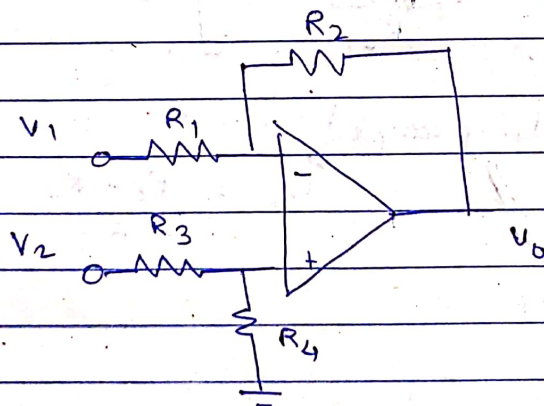When we connect an opAmp we do not get the correct voltage drop




This is due to loading effect
resistance R_A & R_B get loaded to R_1
& R_C & R_D get loaded to R_2

So we do not get the correct drop across V_1 & V_2


So to resolve this we connect a buffer

loading: drawing current

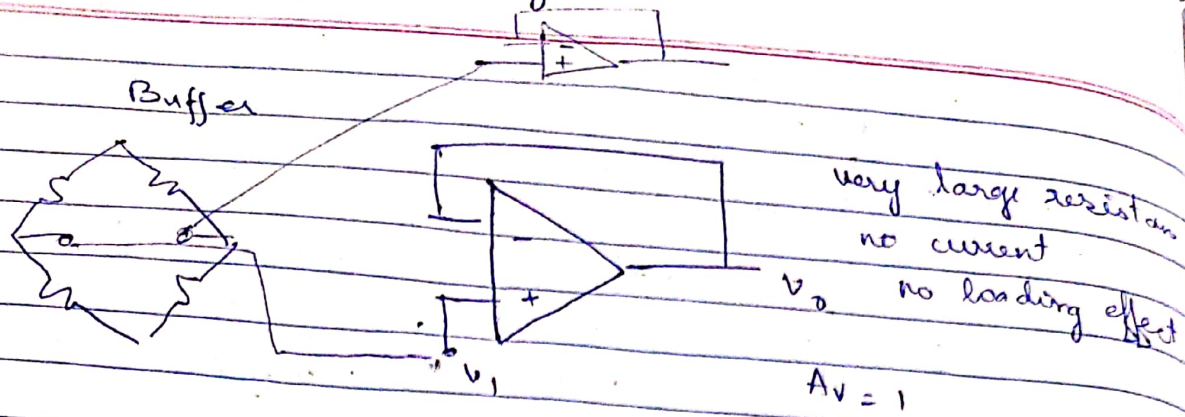

Differential Amplifier 5

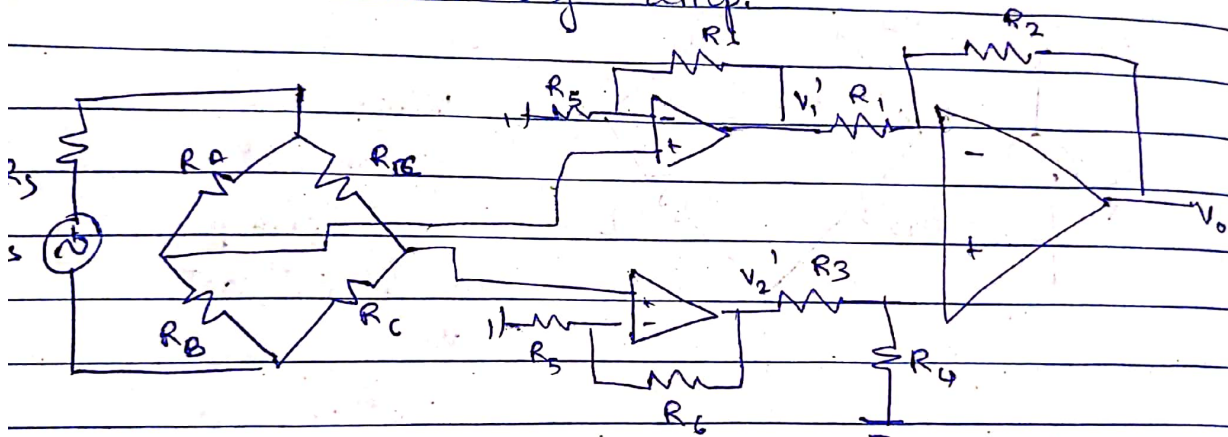For the previous ckt, if the i/p signals are weak, instead of buffer we use non-inverting amp.



Gain of non inverting amplifiers

$$G_1 = \frac{R_5 + R_6}{R_5}$$

$$G_2 = \frac{R_3 + R_4}{R_3}$$

$$\frac{V_1'}{V_1} = \frac{R_5 + R_6}{R_5}$$

$$\therefore V_1' = V_2' = \left(\frac{R_5 + R_6}{R_5} \right) V_1 \text{ or } V_2$$

Differential amplifier

$$\frac{\partial u}{\partial y} = x + 2x \frac{\partial x}{\partial y}$$

$$\frac{\partial v}{\partial y} = 1 +$$

$$\frac{R_2}{R_1} = \frac{R_4}{R_3}$$


$$V_0 = -\frac{R_2}{R_1} V_1' + \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_2'$$

$$V_0 = \frac{R_2}{R_1} (V_2' - V_1')$$

$$= \frac{R_2}{R_1} \cdot \left(\frac{R_5 + R_C}{R_5} \right) (V_2 - V_1) //$$

Using this concept we build

Instrumentation Amplifier

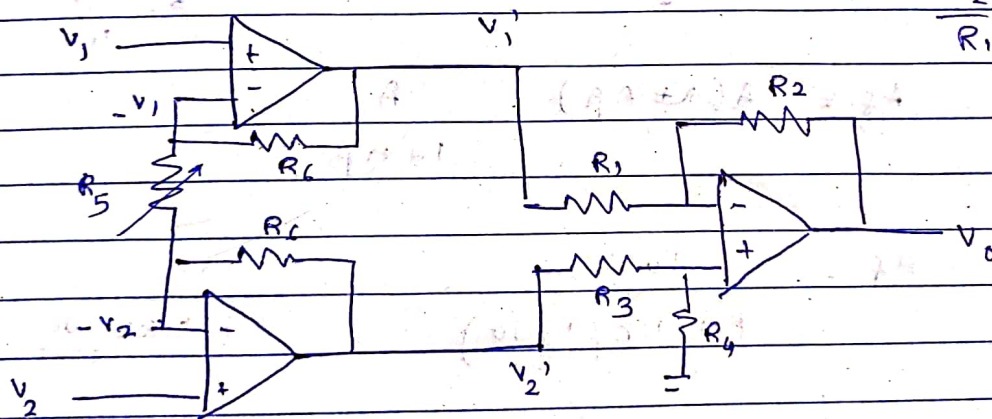


$$\frac{R_2}{R_1} = \frac{R_4}{R_3}$$

$$V_1' = \frac{R_5 + R_C}{R_5} V_1 - \frac{R_C}{R_5} V_2 \quad V_2' = -\frac{R_C}{R_5} V_1 + \frac{R_5 + R_C}{R_5} V_2$$

$$V_0 = \frac{R_2}{R_1} (V_2' - V_1') = \frac{R_2}{R_1} \cdot \frac{R_5 + 2R_C}{R_5} (V_2 - V_1) = A_d (V_2 - V_1)$$

$$A_d = G_1 G_2$$

②

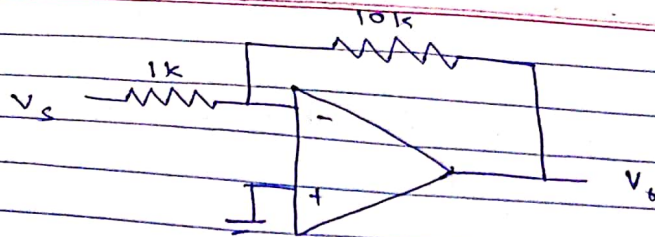

The inverting OpAmp shown has an open loop gain of 100.
Determine the closed loop gain $\frac{V_o}{V_s}$

→

$$A = 100$$

$$\frac{V_s}{V_o} = 100$$

$$V_s = 100 V_o$$

$$\beta = \frac{1k}{11k}$$

$$A_f = \frac{A}{1 + A\beta}$$

$$A$$

$$1 + A\beta$$

$$A_f = \frac{100}{1 + 100(1 + 10)}$$

$$100$$

$$1 + 100(1 + 10)$$

$$1 + 100 \frac{100}{11}$$

$$= 9.9 //$$

φ

β is wt 2 inputs

$$\beta = () V_s + () V_o$$

$$= \frac{R_1}{R_2} = \frac{1}{10}$$

δy

$\frac{\delta y}{\delta x}$

δy

$$A_f = \frac{100}{1 + 100(Y_0)}$$

$$z = -9.09 \checkmark$$


$$A_f = \frac{100}{1 + 100(V_o)}$$

$$z = -9.09 \checkmark$$

8.4.18

1. Construct summing, scaling & averaging amplifier using opamp.


→ (i) Summing

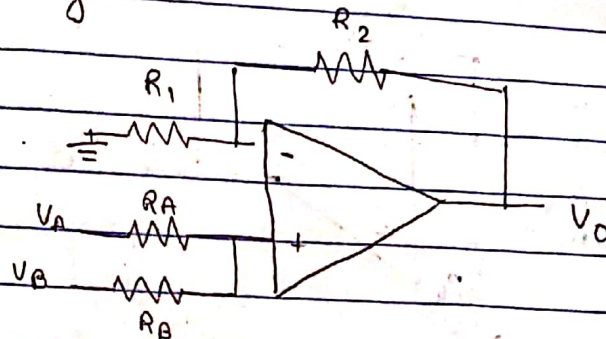

$$V_{in} = V_A + V_B$$

$$\frac{V_O}{V_{in}} = - \frac{R_2}{R_1}$$

(ii) Average

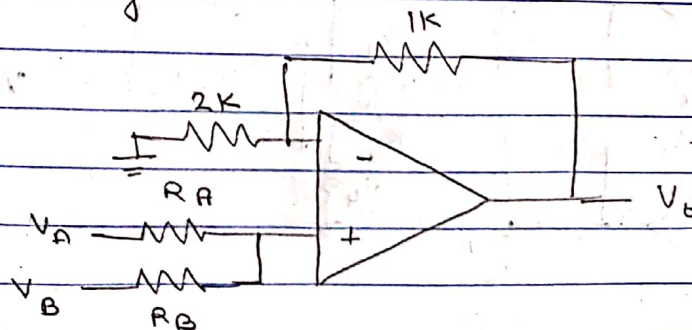


$$\frac{\sum n}{2}$$


$$\text{Gain} = \frac{1}{2} - \frac{R_2}{R_1}$$

$$\frac{R_2 + R_1}{R_1} = 1$$

(iii) Scaling

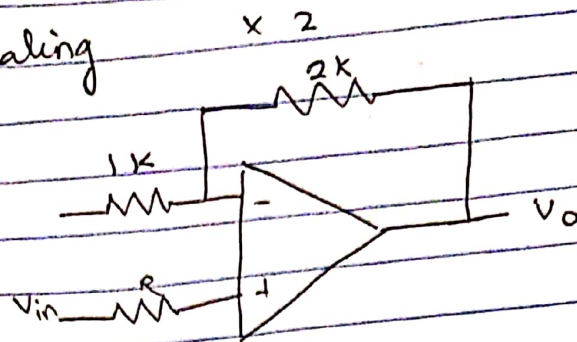


Diff. Amp built using Op Amp

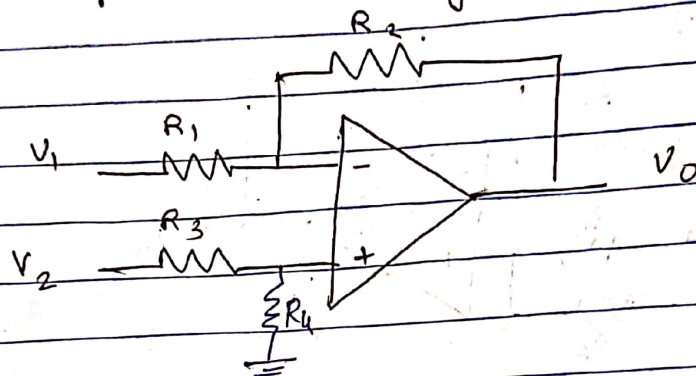

$$\text{Gain} = + \frac{R_2}{R_1}$$

4] Instrumentation Amp

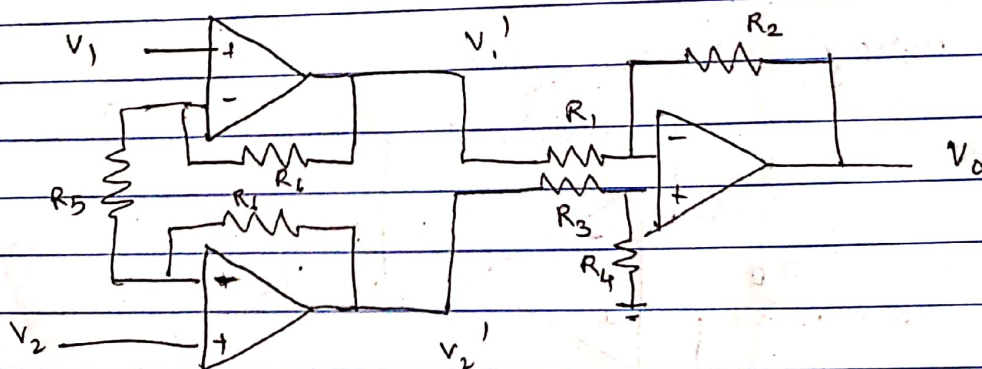

$$V_o = G_1 G_2 (V_1 - V_2)$$


Applications:

wherever small diff. in voltage has to be measured
strain gauge


Diff b/n diff-amp & instrumentation

I.A is meant to measure vol. b/n 2 points
whereas D.A will amplify the diff. signal.

Find o/p voltage.

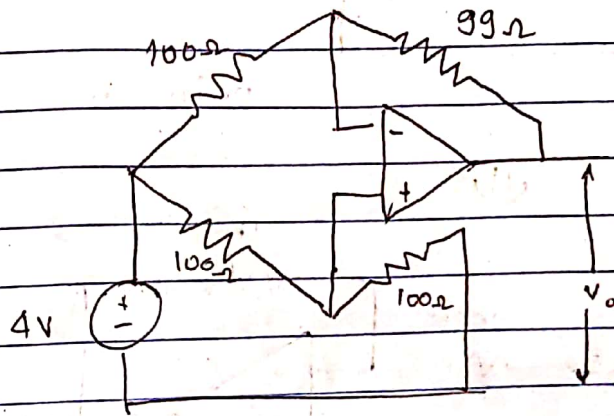

$$\frac{200 \times 4}{300} = 2.6$$

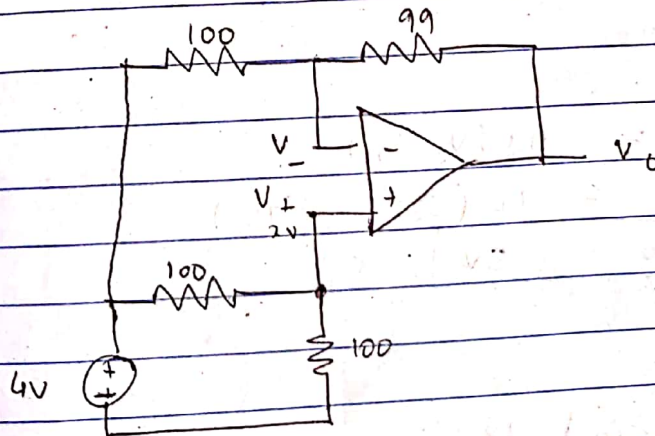

$$\frac{4 \times 100}{300} = 1.$$

$$\frac{V_+ - 4}{100} + \frac{V_+}{100} = 0$$

$$V_+ = 2V$$

$$\text{At } V_- \quad (V_+ = V_-)$$



$$\frac{V_+ - 4}{100} + \frac{V_+ - V_o}{99} = 0$$

$$V_o = -0.02V$$

? Determine V_o

$$V_- = \frac{10 \times 105}{200}$$

$$V_+ = \frac{10 \times 95}{200}$$

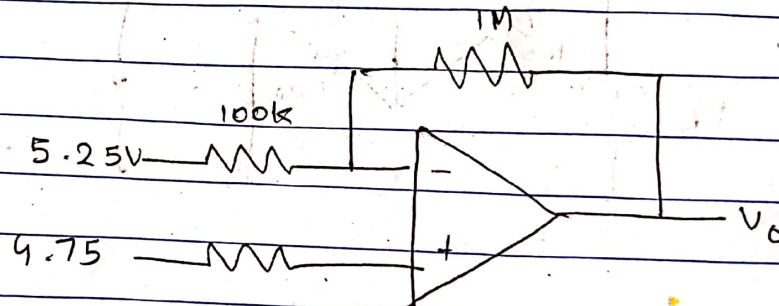
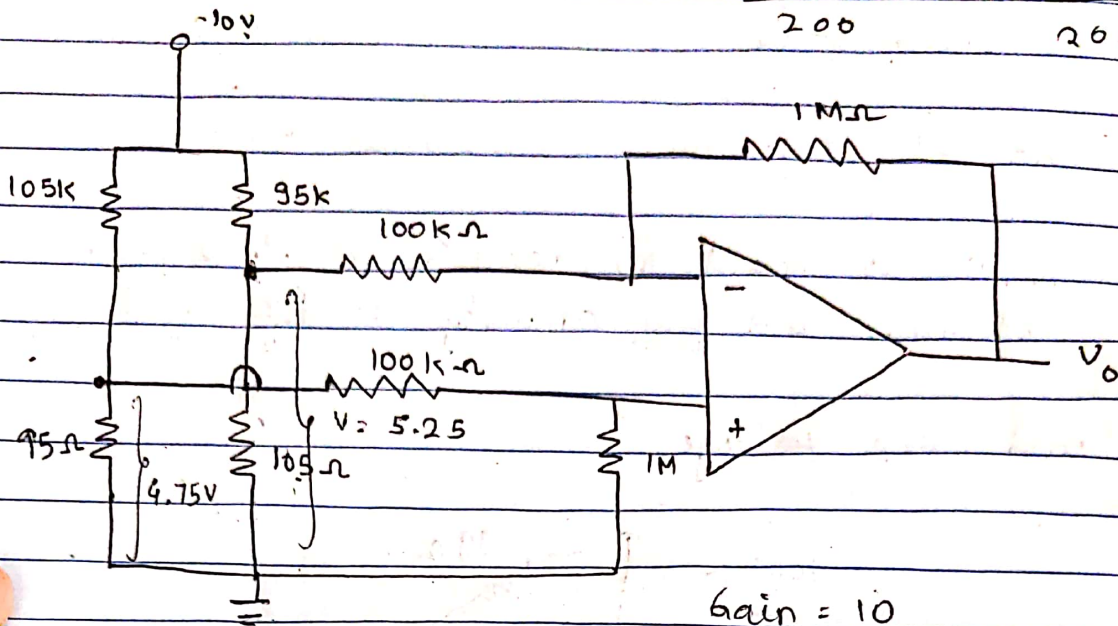


$$V_o = A_d (V_2 - V_1)$$

$$= 10 (5.25 - 4.75)$$

$$V_o = 5V$$

③ $S = 0.05$; Find V_o

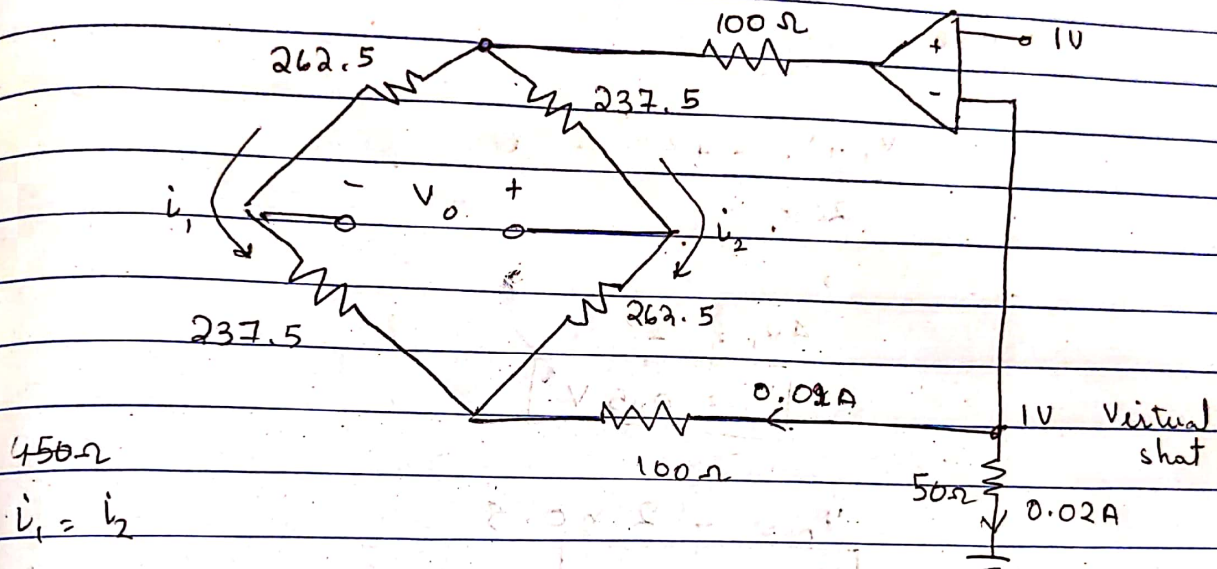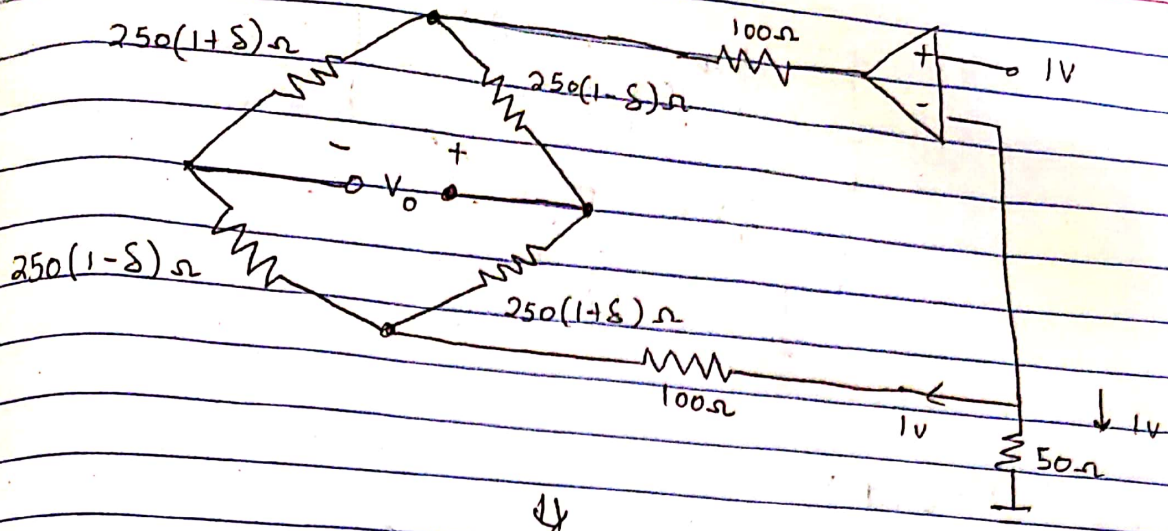

$$V_{out} = 250(1+\delta)0.01 - V_o - 250(1-\delta)0.01 = 0$$


$$V_o = 0.25V$$

$$= 250mV //$$

④ Calc. V_o assume ideal opAmp



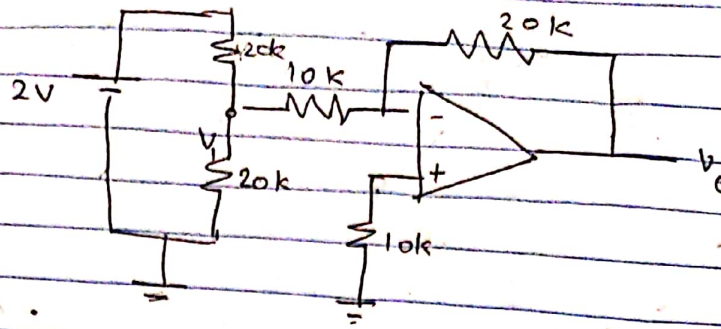-ve feedback $\therefore$ o/p unsaturated
So virtual gnd.



KVL at V_1

$$\frac{V_1}{20k} + \frac{V_1 - 2}{20k} + \frac{V_1}{10k} = 0$$

$$\frac{V_1 + V_1 - 2 + 2V_1}{20k} = 0$$


$$4V_1 = 2$$

$$V_1 = 0.5 \text{ V}$$

$$V_o = -2 \times 0.5$$

$$V_o = -1 \text{ V}$$

5. Calculate I_L

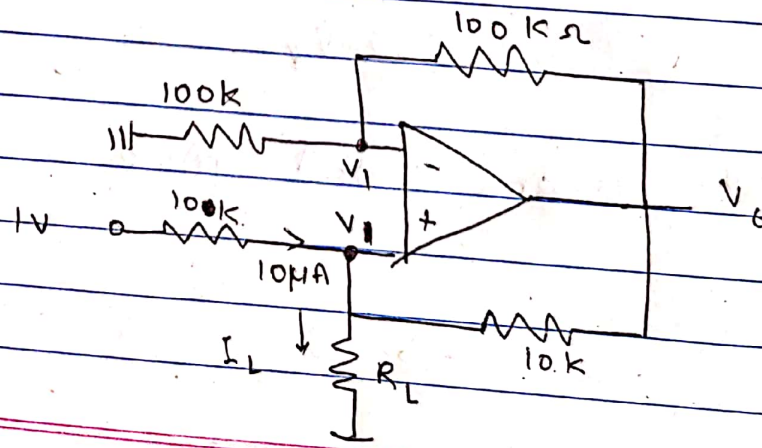

$$A = 1 + \frac{R_2}{R_1}$$

$$= 1 + \frac{100k}{100k}$$

$$= 2$$

$$\frac{V_1 - V_0}{10k} + \frac{V_1 - 1}{100k} + \frac{V_1}{R_L} = 0 \quad \text{--- (1)}$$

$$I_L = 10k \times 10\mu$$

$$\frac{V}{100k} + \frac{V - V_0}{100k} = 0$$

$$\boxed{2V_1 = V_0}$$

$$\frac{V_1}{100k} - \frac{2V_1}{100k} + \frac{V_1 - 1}{100k} + I_L = 0$$

$$\frac{10(-V_1)}{100k} + \frac{V_1 - 1}{100k} + \frac{100k I_L}{100k} = 0$$

$$-10V_1 + V_1 - 1 + 100k I_L = 0$$

$$-9V_1 - 1 + 100k I_L = 0$$

$$I_L = \frac{9V_1 + 1}{100k}$$

(1)

$$\frac{-1}{10k} = -I_L$$

$$\boxed{I_L = 100\mu A}$$